

Electronic Circuits Laboratory

EE462G

Lab #2

Characterizing Nonlinear Elements,
Semiconductor Analyzer, Transfer
Characteristics


Original slides prepared by Kevin D. Donohue (Spring 2007)

Modified by Zhi David Chen (Fall 2023)

Nonlinear Elements

Diodes

- *pn* junction
- Zener

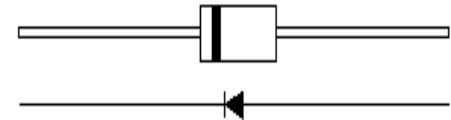


Transistors

- Field Effect Transistors – (FETs)

ZVN3306A -NMOSFET

ZVP3306A -PMOSFET

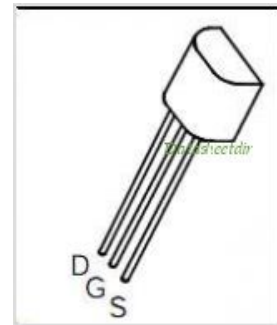

- Bipolar Junction Transistors – (BJTs)

PN2222 –NPN BJT




Instrumentation

Peak Electronics

DCA75 - Atlas DCA Pro Advanced Semiconductor Analyzer



Instrumentation

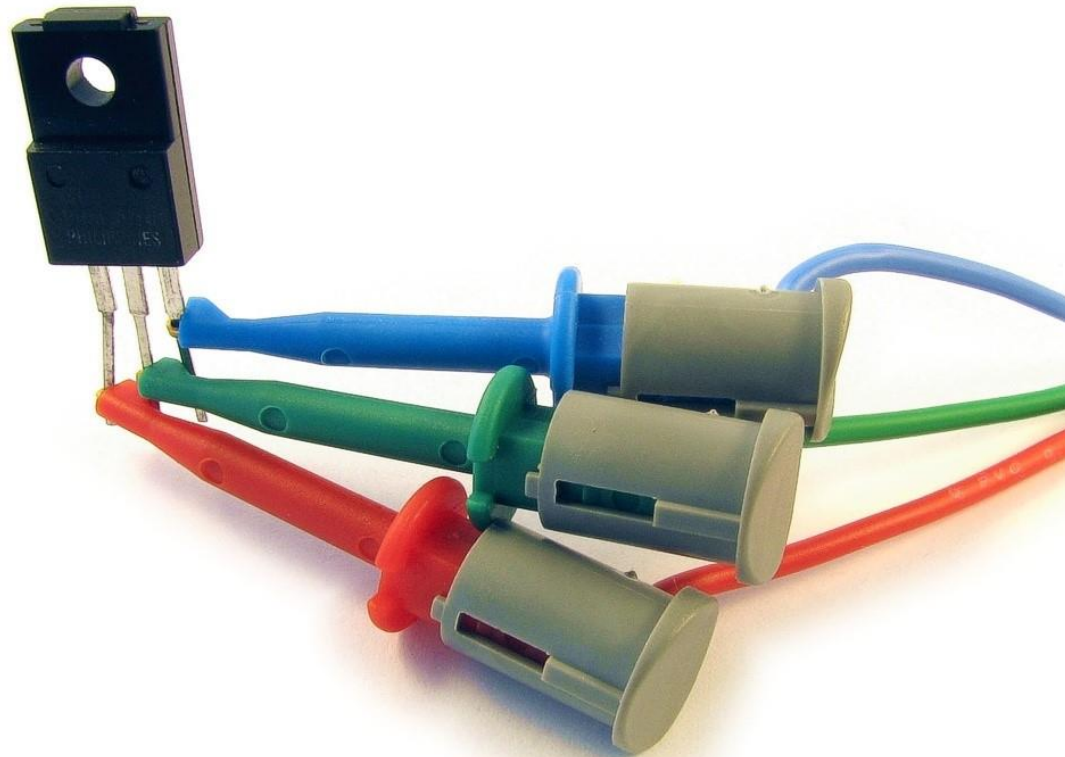

Instrumentation

Peak DCA Pro

DCA Pro Data Graph Help


Identify PN Junction BJT Ic / Vce BJT hFE / Vce BJT hFE / Ic BJT Ic / Vbe BJT Ic / Ib

Test

Diode junction
Red-A Blue-K
Vf=0.649V at 5.00mA

Anode(+) Cathode(-)

Diode




- Diode Junction is displayed for diodes or diode junctions (pn junctions).
- Forward voltage measured at a nominal test current of 5.0mA ± 0.25 mA.
- Voltage accuracy is typically $\pm 1\% \pm 0.006$ V.
- Valid forward voltage range is 0.15V-1.49V.
- Infra-red LEDs may fall within this voltage range.

DCA Pro connected New result received. Diode junction

Instrumentation

Find turn-on voltage V_f

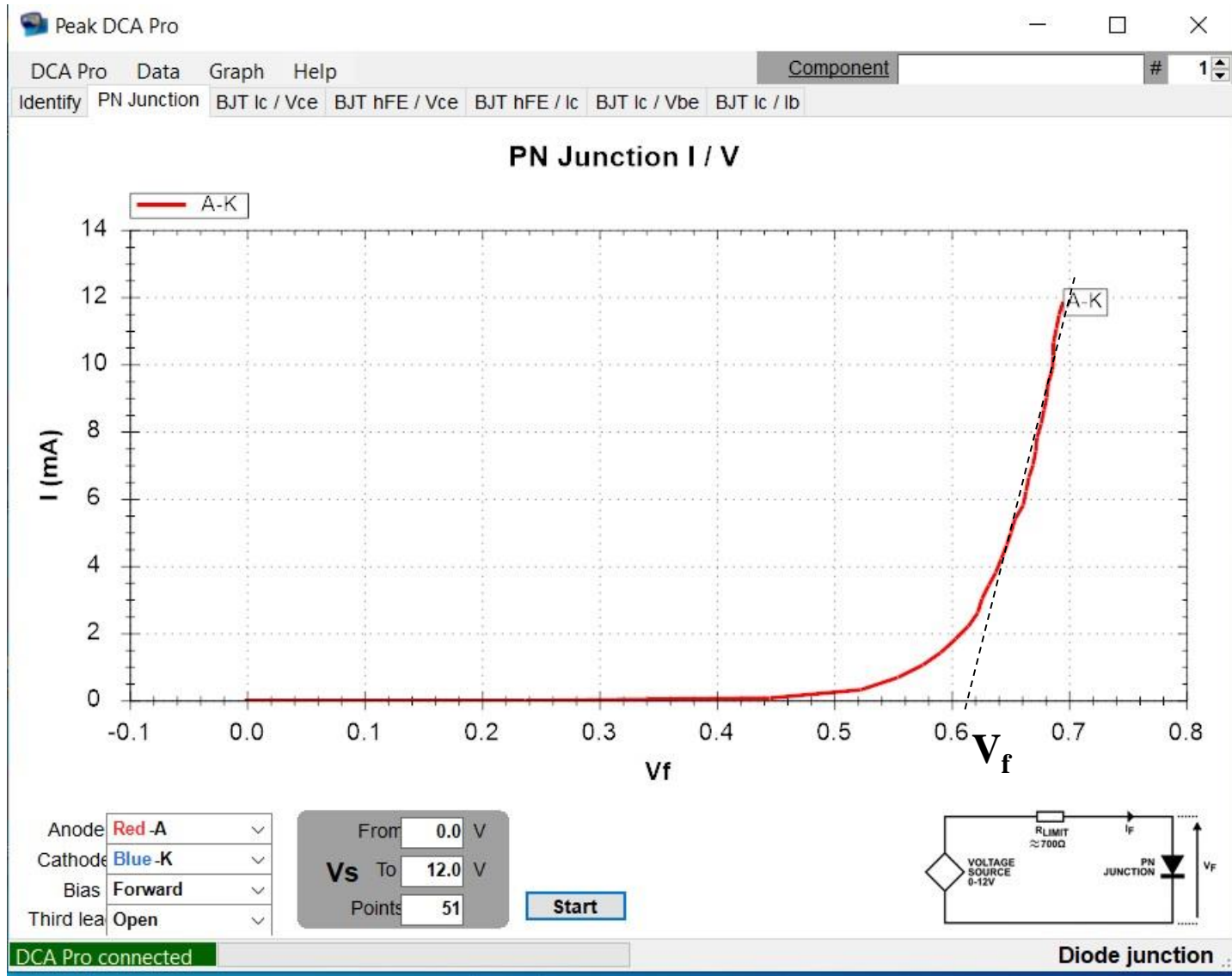

Instrumentation

Peak DCA Pro


DCA Pro Data Graph Help Component # 1

Identify PN Junction MOSFET Id / Vds MOSFET Id / Vgs

Test

N-Ch Enhancement mode MOSFET
Red-G Green-S Blue-D
Vgs(on)=2.290V at Id=5.05mA and Ig=2μA
Vgs(off)=1.631V at Id=5.2μA
gm=25.2mA/V at Id=3.0mA to 5.0mA
Rds(on)=4.5Ω at Id=5.0mA and Vgs=8.0V
with body diode


N-Ch Enhancement mode MOSFET

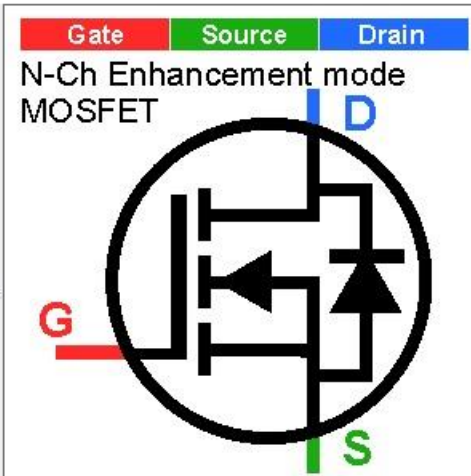

- The gate “on” threshold is determined when drain current is 5.0mA ±0.25mA.
- Gate threshold voltage accuracy is typically ±2% ± 0.01V.
- Transconductance is measured for a typical range of drain current from 3mA to 5mA.
- Transconductance is generally much larger at higher drain currents, particularly for power MOSFETs.
- Transconductance accuracy is typically ±5% ±2mA/V for values less than 20mA/V.
- Transconductance accuracy is typically ±10% ±5mA/V for values more than 20mA/V.
- Most MOSFETs have a “body diode” between the

DCA Pro connected New result received.

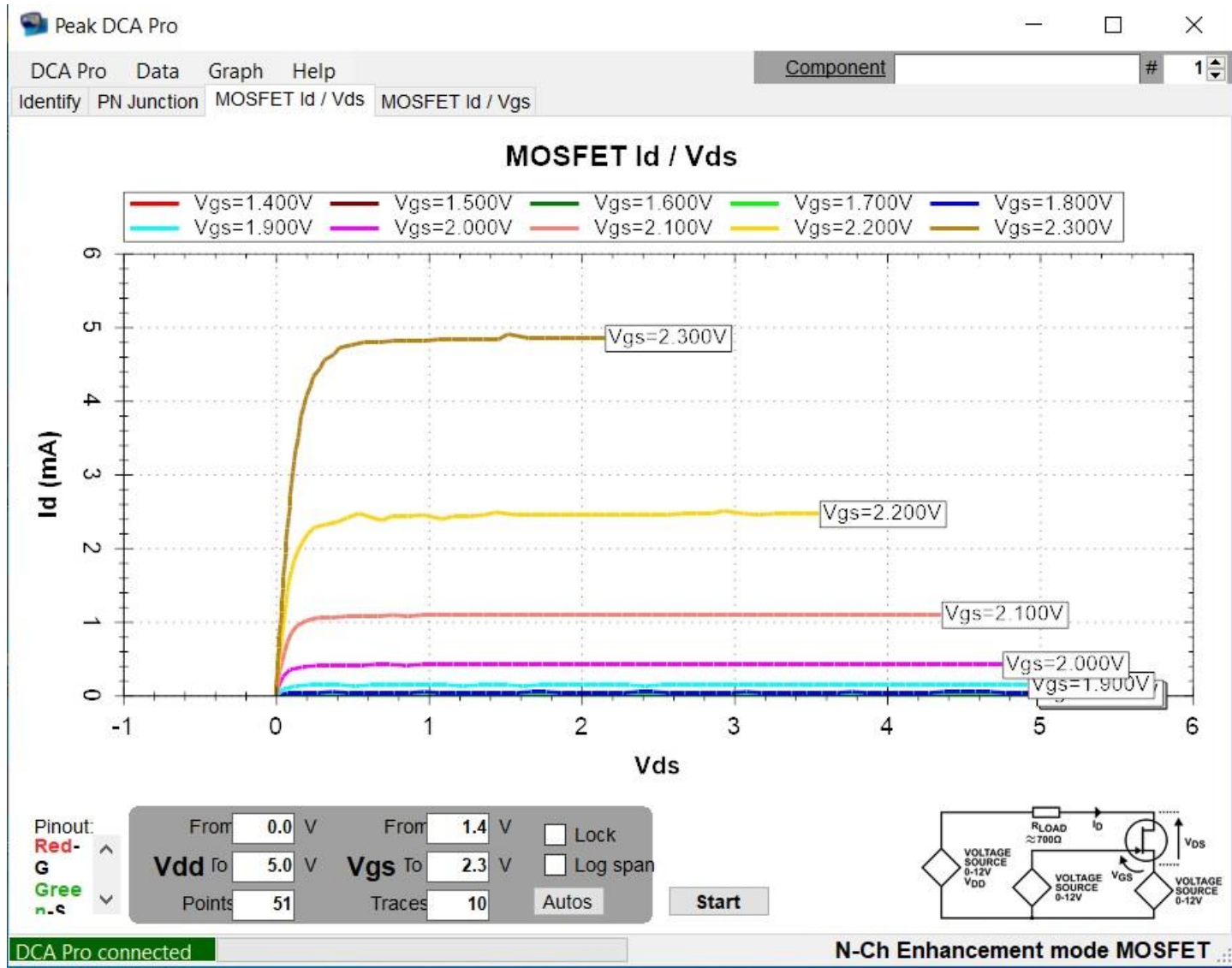Instrumentation Find threshold voltage V_{th}




Transfer Characteristics

Transfer Characteristics


- A relation describing the amplitude input-output relationship of a device (I-V curve).
- A sufficient characterization in most engineering problems for instantaneous systems (present output does not depend on future or previous values). These systems are sometimes referred to as memoryless and are typical of systems with no energy storage elements.

PN junction diode

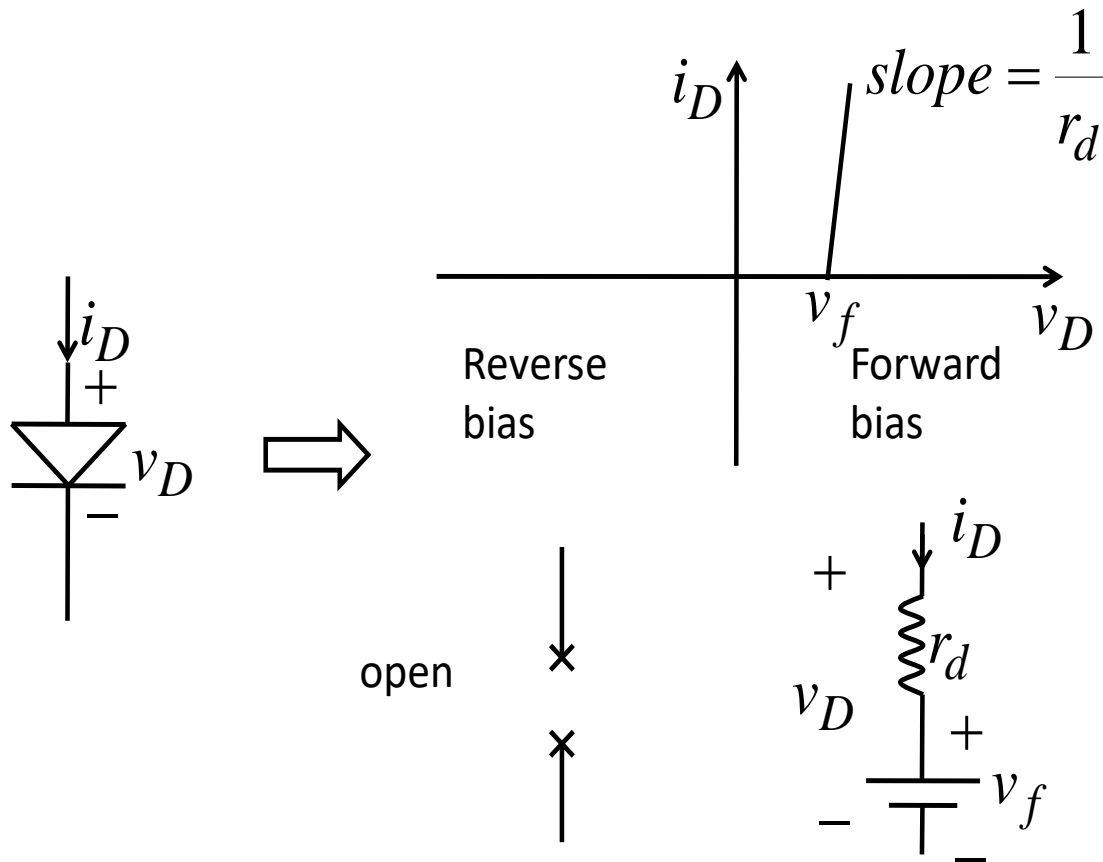

The band on the component usually denotes the cathode terminal



Zener diode

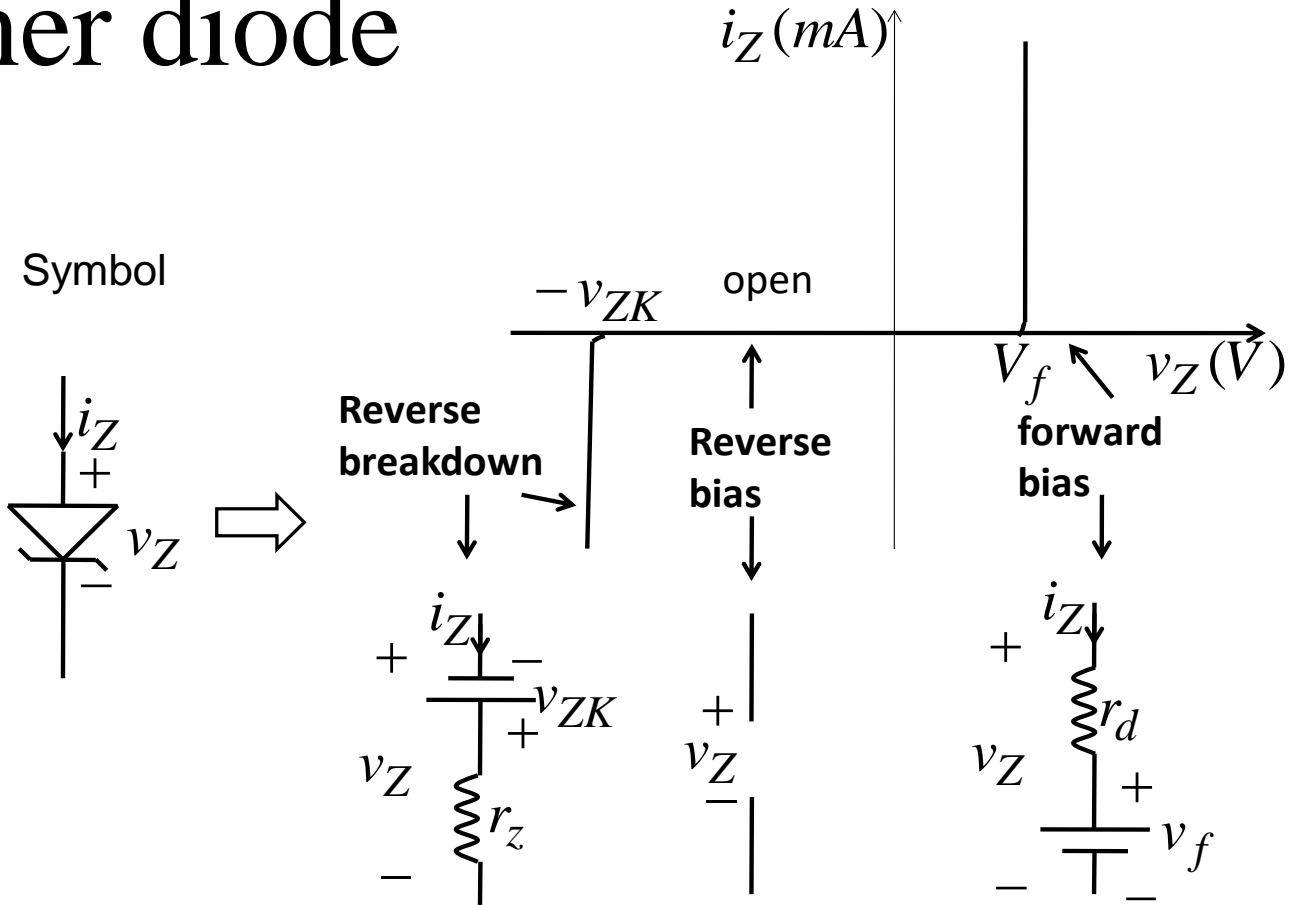

The band on the component usually denotes the cathode terminal

n-Channel MOSFET

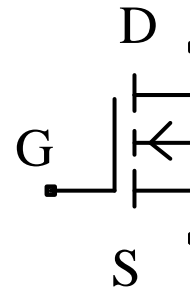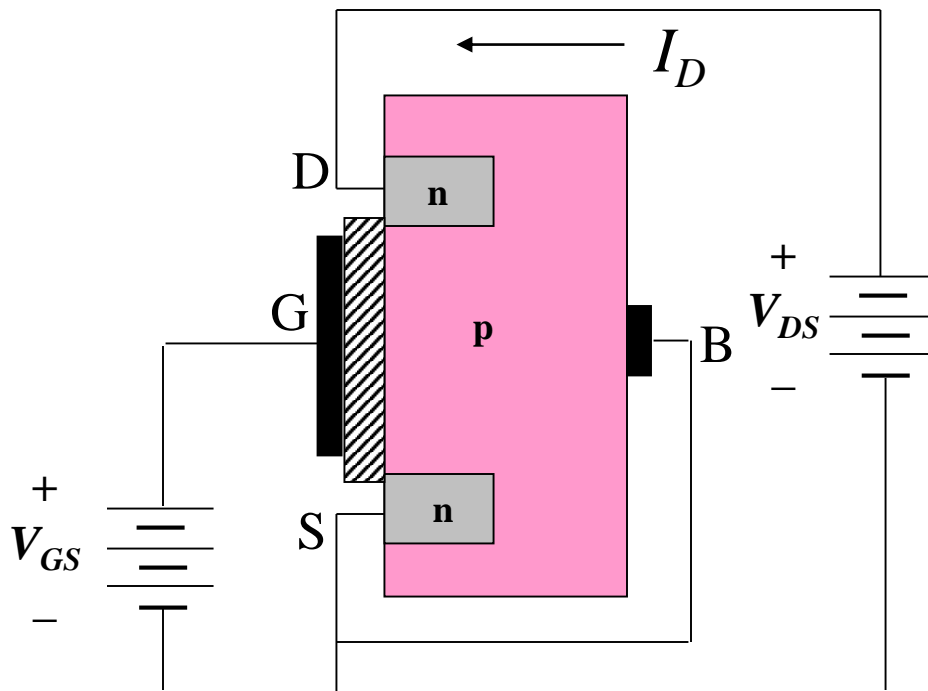A Metal-Oxide-Semiconductor field-effect transistor (MOSFET) is presented for charge flowing in an n-channel:




- B – Body or Substrate
- D – Drain
- G – Gate
- S – Source

For many applications the body is connected to the source and thus most FETs are packaged that way.


FET Operation

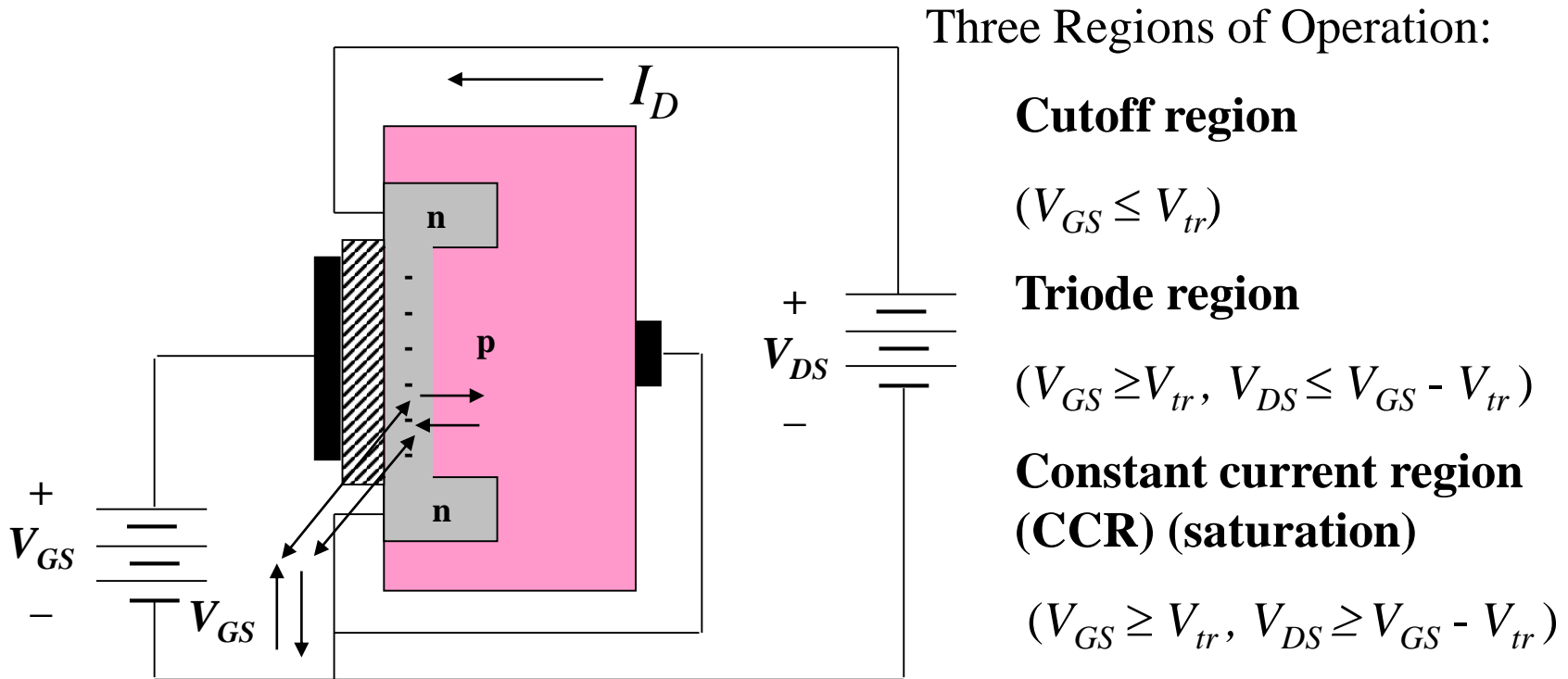The current flow between the drain and the source can be controlled by applying a positive gate voltage:



Cutoff Region

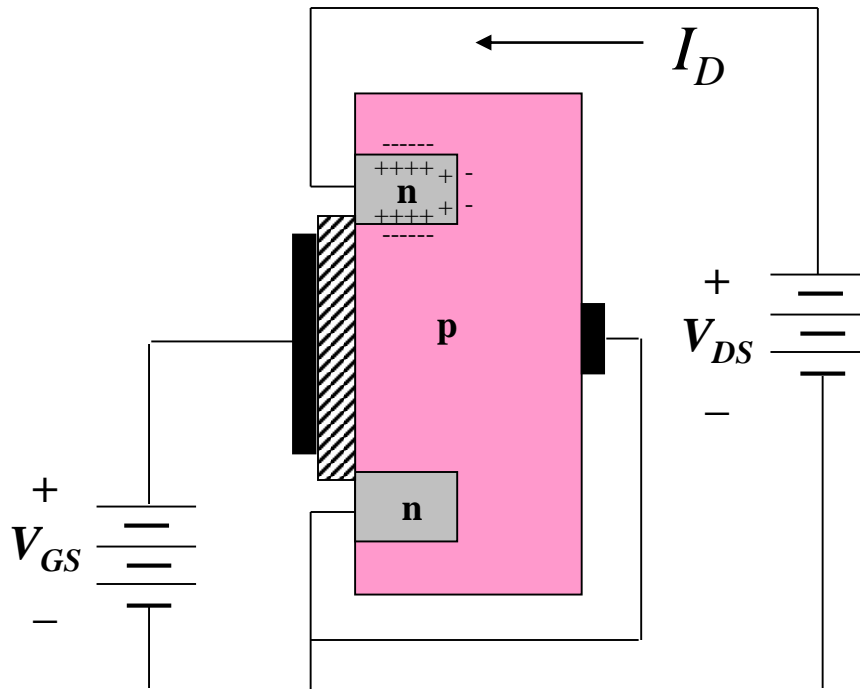In this region ($V_{GS} \leq V_{tr}$) the gate voltage is less than the threshold voltage and virtually no current flows through the reversed biased PN interface between the drain and body.




Typical values for V_{tr} (or V_{to}) range from 1 to several volts.

Cutoff region: $I_D=0$

Triode Region

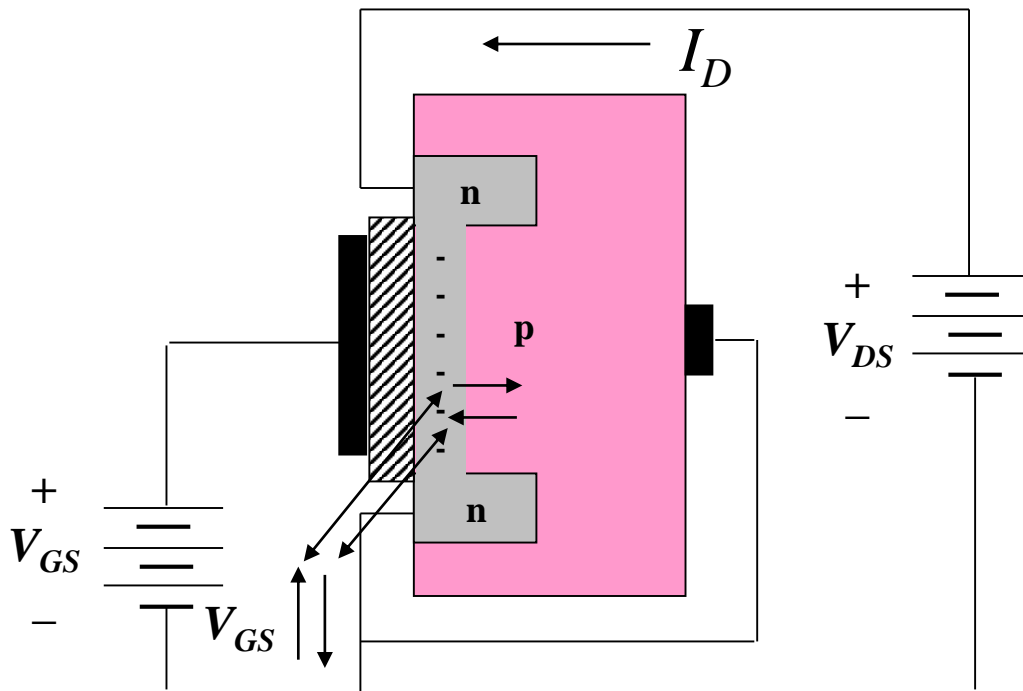In this region ($V_{GS} > V_{tr}$ and $V_{DS} \leq V_{GS} - V_{tr}$) the gate voltage exceeds the threshold voltage and pulls negative charges toward the gate. This results in an n -Channel whose width controls the current flow I_D between the drain and source.



Triode Region:


$$(V_{GS} > V_{tr}, V_{DS} \leq V_{GS} - V_{tr})$$

$$I_D = \left(\frac{W}{L}\right) \frac{K_p}{2} \left[2(V_{GS} - V_{tr})V_{DS} - V_{DS}^2 \right]$$

where: $K_p = \mu_n C_{ox}$
product of surface mobility of channel electrons μ_n and gate capacitance per unit area C_{ox} in units of amps per volts squared, W is the channel width, and L is channel length.

Constant Current Region (CCR)

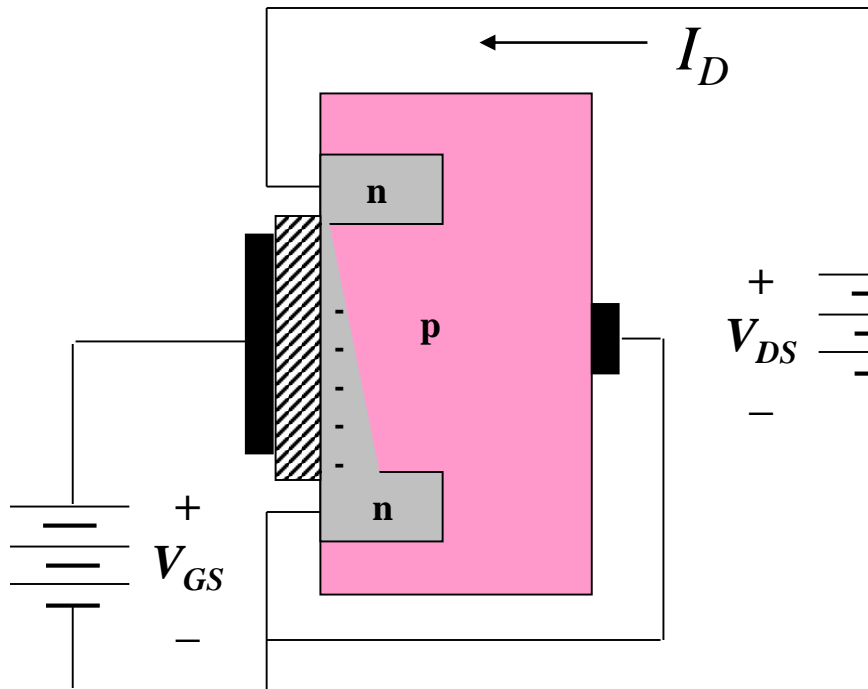In this region ($V_{GS} > V_{tr}$ and $V_{GS} - V_{tr} \leq V_{DS}$) the drain-source voltage exceeds the excess gate voltage and pulls negative charges toward the drain and reduces the channel area at the drain. This limits the current making it more insensitive/independent to changes in V_{DS} .



CCR: $V_{GS} > V_{tr}$, $V_{DS} \geq V_{GS} - V_{tr}$

$$I_D = \left(\frac{W}{L}\right) \frac{K_p}{2} (V_{GS} - V_{tr})^2$$

The material parameters can be combined into one constant:

$$I_D = K(V_{GS} - V_{tr})^2$$

At the point of beginning of CCR (Saturation), for a given V_{GS} , the following relation holds:

$$I_D = K V_{DS}^2$$

NMOS Transfer Characteristics

The relations between I_D and V_{DS} for the operational regions of the NMOS transistor can be used to generate its transfer characteristic. These can be conveniently coded in a Matlab function

```
function ids = nmos(vds,vgs,KP,W,L,vto)
```

```
% This function generates the drain-source current values "ids" for  
% and NMOS Transistor as a function of the drain-source voltage "vds".  
% ids = nmos(vds ,vgs,KP,W,L,vto)  
% where "vds" is a vector of drain-source values  
%     "vgs" is the gate voltage  
%     "KP" is the device parameter  
%     "W" is the channel width  
%     "L" is the channel length  
%     "vto" is the threshold voltage  
% and output "ids" is a vector of the same size of "vds"  
% containing the drain-source current values.
```


NMOS Transfer Characteristics

```
ids = zeros(size(vds)); % Initialize output array with all zeros
k = (W/L)*KP/2; % Combine devices material parameters
% For non-cutoff operation:
if vgs >= vto
    % Find points in vds that are in the triode region
    ktri = find(vds <= (vgs - vto) & vds >= 0); % Points less than (gate - threshold voltage)
    % If points are found in the triode region compute ids with proper formula
    if ~isempty(ktri)
        ids(ktri) = k*(2*(vgs - vto).*vds(ktri) - vds(ktri).^2);
    end
    % Find points in saturation region
    ksat = find(vds > (vgs - vto) & vds >= 0); % Points greater than the excess voltage
    % if points are found in the saturation regions compute ids with proper formula
    if ~isempty(ksat)
        ids(ksat) = k*((vgs - vto).^2);
    end
    % If points of vds are outside these ranges, then the ids values remain zero
end
end
```

NMOS Transfer Characteristics

Plot the transfer characteristics of an NMOS transistor where $K_P = 50 \mu\text{A}/\text{V}^2$, $W = 160 \mu\text{m}$, $L = 2 \mu\text{m}$, $V_{tr} = 2\text{V}$, and for $V_{GS} = [.5, 1, 2, 3, 4, 5, 6]$ volts
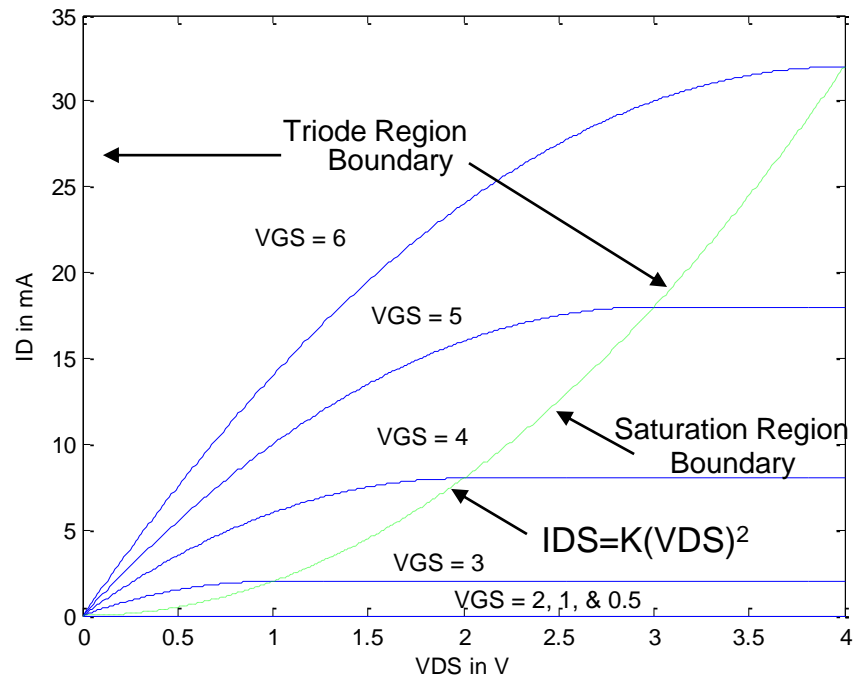
```
vgs = [.5, 1, 2, 3, 4, 5, 6]
vds = [0:.01:4];
for kc = 1:length(vgs)
ids = nmos(vds,vgs(kc),50e-6,160e-6,2e-6,2);
figure(1); plot(vds,ids*1000)
hold on
end
ids = (50e-6/2)*(160e-6/2e-6)*vds.^2;
figure(1); plot(vds,ids*1000,'g:')
hold off
xlabel('VDS in V')
ylabel('ID in mA')
```



Find K from Curves

Recall at the start of CCR the following holds: $I_D = KV_{DS}^2$

From graph: $I_D = KV_{DS}^2$


$$0.4 = K1.5^2$$

$$0.7 = K2.6^2$$

$$1.5 = K3.4^2$$

One way to estimate K is to compute it for each equation and take the average. In this case it becomes $K=0.137 \text{ A/V}^2$, which for $W=L=1$, implies:

$$K_p = K*2 = 0.274 \text{ A/V}^2$$

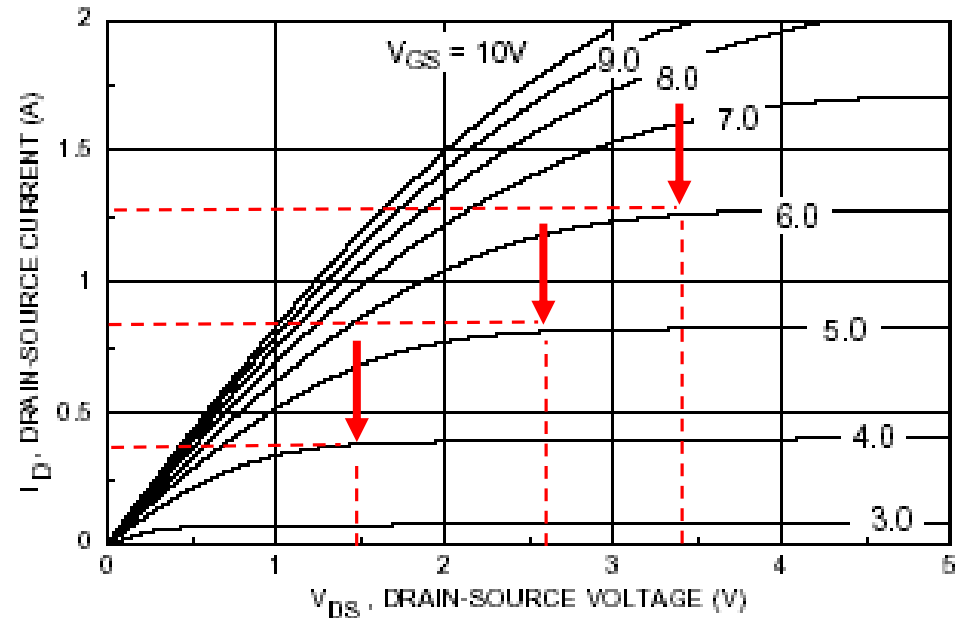

Find K from Curves

From graph:

$$I_D = KV_{DS}^2$$
$$0.4 = K1.5^2$$
$$0.7 = K2.6^2$$
$$1.5 = K3.4^2$$

A better approach uses a least-squares solution that gives the error in each equation equal weight. Find K to minimize mean square error for the measured data:

$$\langle E^2 \rangle = \frac{1}{M} \sum_{i=1}^M (I_{Di} - KV_{DSi}^2)^2$$


Take derivative with respect to K and set equal to 0 to obtain:

$$K_{LS} = \frac{\sum_{i=1}^M (V_{DSi}^2 I_{Di})}{\sum_{i=1}^M (V_{DSi}^2 V_{DSi}^2)} \quad K_{LS} = \frac{(.4 \times 1.5^2 + .7 \times 2.6^2 + 1.5 \times 3.4^2)}{(1.5^2 \times 1.5^2 + 2.6^2 \times 2.6^2 + 3.4^2 \times 3.4^2)} = .1246 \quad \frac{A}{V^2}$$

which for $W=L=1$, implies: $K_p = K_{LS} * 2 = 0.2492 \text{ A/V}^2$


Diode TC (I-V curve)

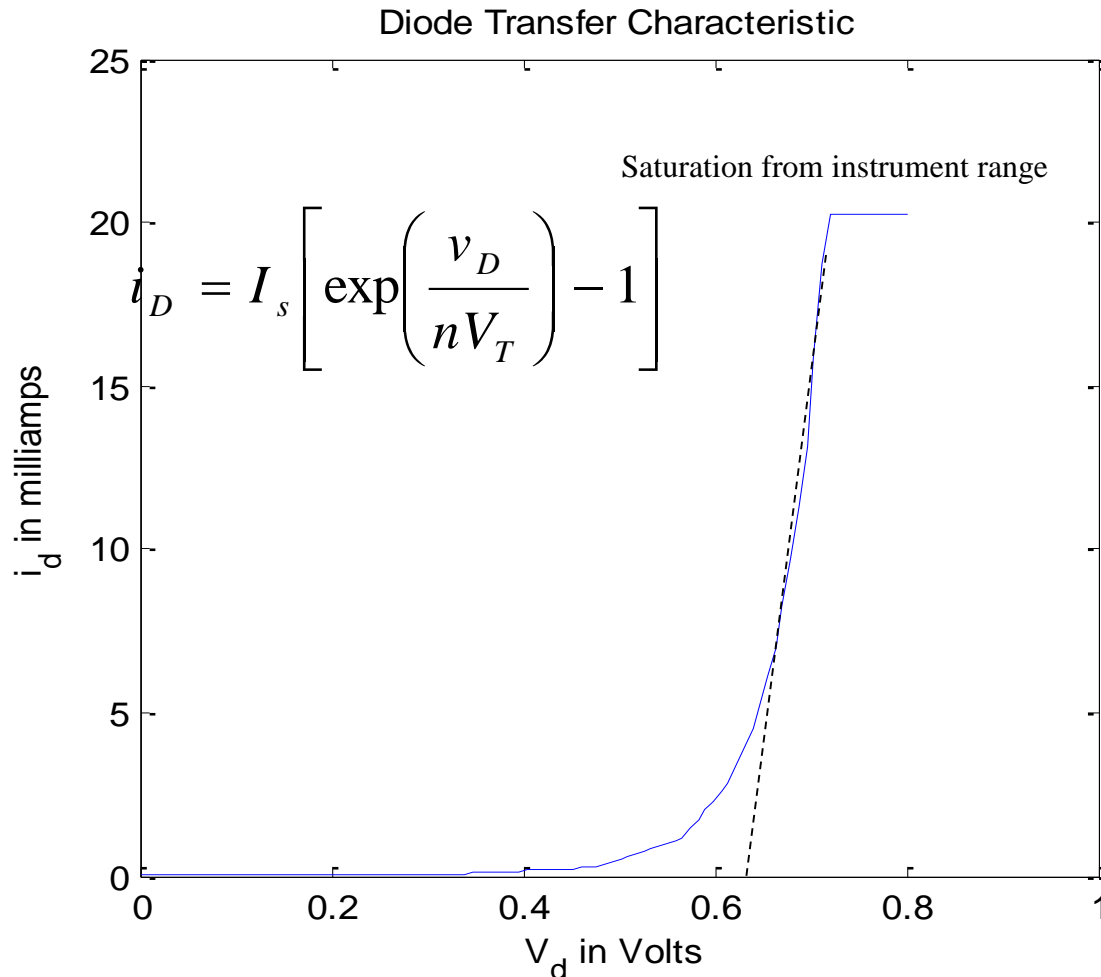Use Atlas DCA Pro Advanced Semiconductor Analyzer to obtain the diode I-V curve. Find the turn-on voltage V_f .



FET TC (I-V curve)

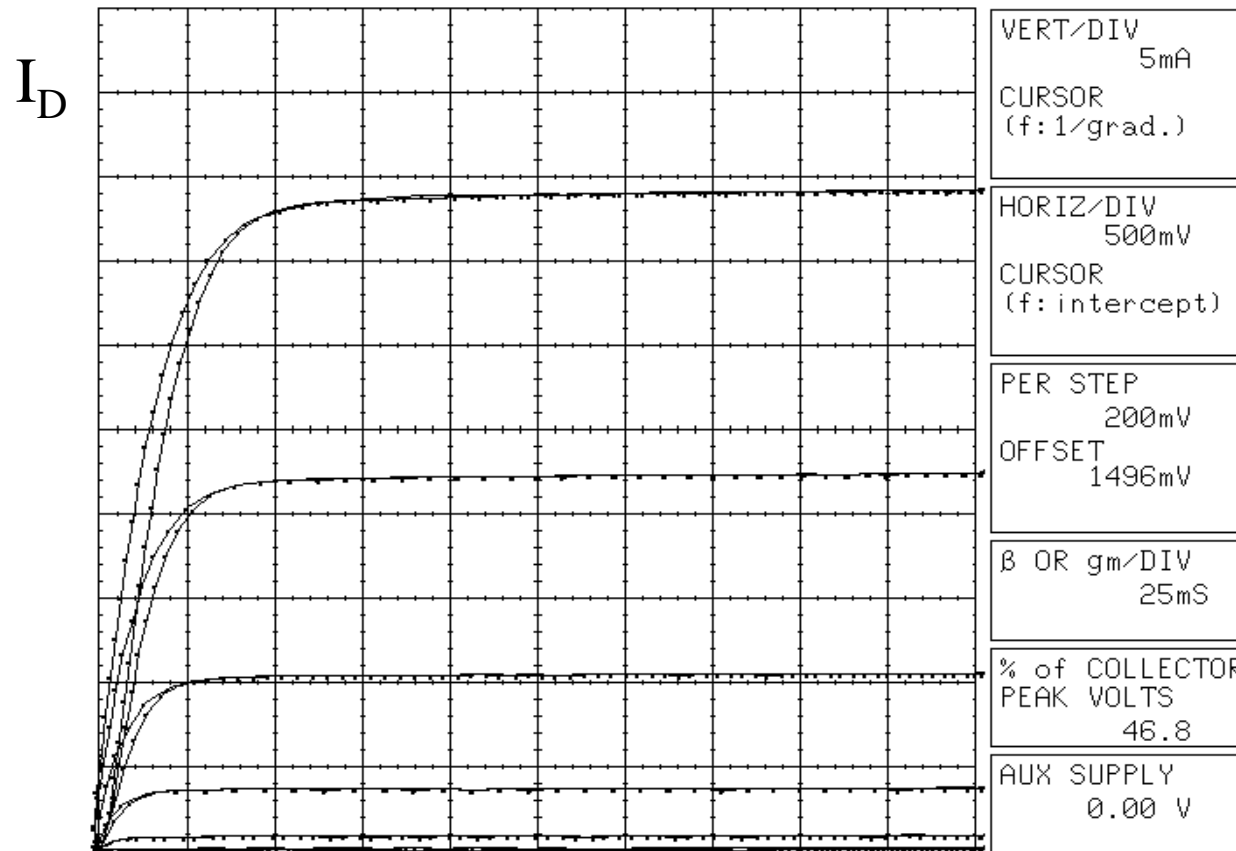Use Atlas DCA Pro Advanced Semiconductor Analyzer to obtain the FET I-V curves. Find the threshold voltage V_{th} .



V_{DS}