
 


Truth Tables

 


| V_{in} | V_{out} |
|----------|-----------|
| 0 | 1 |
| 1 | 0 |

Logic Inverter




| V_{in} | V_{out} |
|----------|-----------|
| 0 | 1 |
| 1 | 0 |

Logic Inverter

 


| V_{in1} | V_{in2} | V_{out} |
|-----------|-----------|-----------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

Logic Nor

 


| V_{in} | V_{out} |
|----------|-----------|
| 0 | 1 |
| 1 | 0 |

Logic Inverter

 

| V_{in} | V_{out} |
|----------|-----------|
| 0 | 1 |
| 1 | 0 |


Logic Inverter

 

| V_{in1} | V_{in2} | V_{out} |
|-----------|-----------|-----------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

Logic Nor

2.

 

$$I_D = 1\text{mA} \approx \frac{V_{DD}}{R_D} \quad \therefore R_D = \frac{V_{DD}}{I_D} = \frac{5\text{V}}{1\text{mA}} = 5\text{k}\Omega$$

Given: $k_p = .145 \text{ A/V}^2$, $V_{TP} = -2.8\text{V}$

For logic 1 output, $V_{in} = 0$
 $V_{SG} \approx V_{DD} \rightarrow V_{SD} < V_{SG} + V_{TP}$, Triode Region

$$I_D = k_p ((V_{SG} + V_{TP}) V_{SD} - \frac{V_{SD}^2}{2})$$

$$\frac{I_D}{k_p} = (V_{SG} + V_{TP}) V_{SD} - \frac{V_{SD}^2}{2}$$

$$\frac{V_{SD}^2}{2} - V_{SD} (V_{SG} + V_{TP}) + \frac{I_D}{k_p} = 0$$

$$V_{SD}^2 - 2(V_{SG} + V_{TP}) V_{SD} + \frac{2I_D}{k_p} = 0$$


$$V_{SD}^2 - 4.4 V_{SD} + .013793 = 0$$

$$\therefore V_{SD} = 4.3968, .0031, \quad V_{SD} = 3.1\text{mV}$$


not possible

V_{DD}

3)

 

4)

 


Load line

$$-V_{DD} + V_{SD} + i_D R_D = 0$$

$$i_D = \frac{V_{DD} - V_{SD}}{R_D}$$

$$\therefore i_D = 0, \quad V_{DD} = V_{SD}$$
 
$$V_{SD} = 0, \quad i_D = \frac{V_{DD}}{R_D}$$



Generate V_{out} vs V_{in} :

Find where load line intersects MOSFET curves to find i_D and thus V_{out} , where $V_{out} = i_D R_D$

MOSFET


$$V_{SG} = V_{DD} - V_{in}$$

$$V_{in} = 0 \text{ to } 5 \text{ V}$$

$$k_p = .145$$

$$V_{TP} = -2.8$$

 PMOS Logic Circuit Transfer Characteristic



```
% EE462 - Prelab 7 - Problem 4
% Stephen Maloney
```

```
clear all; close all; clc;
```

```
% Set up P-MOS Mosfet Parameters
```

```
KP = .145;
```

```
VTP = -2.8;
```

```
% Set up circuit values
```

```
RD = 5E3;
```

```

VDD = 5;

% A very fine VSD is required for accuracy
VSD = 0:1E-5:5;

% Load line generated by resistor RD
ILL = -1/RD*VSD + VDD/RD;

% Sweep input voltage from logic low (0) to logic high (5)
VIN = 0:.1:5;

% Run through all input voltages and find the Q points where the load
% line and MOSFET curve intersect. The smallest error point is the Q point,
% representing the particular current at that input voltage.

for K = 1 : length(VIN)
    VSG = VDD - VIN(K);

    % Use the NMOS routine to generate ID curve.
    % Note that the VSD and VSG must be used for the PMOS mosfet
    ID = nmos(VSD, VSG, KP, 1, 1, -1*VTP);
    [Error, Eindex] = min(abs(ID - ILL));
    IDMatch(K) = ID(Eindex(1));


end

% Calculate the output voltage
VOUT = IDMatch * RD;


% Plot transfer characteristic
plot(VIN, VOUT, 'k', 'LineWidth', 2); grid on;
title('PMOS Logic Circuit Transfer Characteristic'); xlabel('V_{In}');
ylabel('V_{Out}');

```

5.

 

 not possible
 $2K = K_p = .1233$, $V_{TN} = 1.8V$ (from previous values)
 At maximum i_D , $V_{in} = 5V = V_{GS}$
 $\therefore Q_1$ is in triode region
 Q_2 is an active load



$$i_D = \frac{K_p}{2} (V_{GS} - V_{TN})^2 \rightarrow Q_2, V_{GS} = V_{DD} - V_{out}$$

$$i_D = K_p \left((V_{GS} - V_{TN}) V_{DS} - \frac{V_{DS}^2}{2} \right) \rightarrow Q_1, V_{GS} = V_{in}, V_{DS} = V_{out}$$

$$\frac{K_p}{2} (V_{DD} - V_{out} - V_{TN})^2 = K_p \left((V_{in} - V_{TN}) V_{out} - \frac{V_{out}^2}{2} \right)$$

$$(V_{DD} - V_{out} - V_{TN})^2 = 2(V_{in} - V_{TN}) V_{out} - V_{out}^2$$

$$(3.2 - V_{out})^2 = 6.4 V_{out} - V_{out}^2$$

$$10.24 - 6.4 V_{out} + V_{out}^2 = 6.4 V_{out} - V_{out}^2$$

$$2 V_{out}^2 - 12.8 V_{out} + 10.24 = 0$$

$$V_{out}^2 - 6.4 V_{out} + 5.12 = 0$$


$$V_{out} = \frac{6.4 \pm \sqrt{40.96 - 4(5.12)}}{2}$$

SAT not possible


$$\therefore i_D = \frac{K_p}{2} (V_{DD} - V_{out} - V_{TN})^2$$

$$i_D = 316 \text{ mA}$$

6)

 

 Peak power can approximately found by moving the cursor on the graph into the switching event. As seen below, about 27mW is the peak power for this value of K_p and V_{tn} .



7)

Q_2 is an active load, thus $V_{DS} > V_{GS} - V_{TN}$ always.

$\therefore i_D = \frac{K_P}{2} (V_{GS} - V_{TN})^2$, where $V_{GS} = V_{GS} = V_{DD} - V_{out}$

$i_D = \frac{K_P}{2} (V_{GS} - V_{TN})^2$

$i_D = \frac{K_P}{2} (V_{DD} - V_{out} - V_{TN})^2$

$V_{out} = V_{DSQ_1} \rightarrow i_D = \frac{K_P}{2} (V_{DD} - V_{DSQ_1} - V_{TN})^2$

$\therefore V_{DSQ_1} = 0, i_D = \frac{K_P}{2} (V_{DD} - V_{TN})^2$


$i_D = 0, V_{DSQ_1} = V_{DD} - V_{TN}$

Load line

$i_D = \frac{K_P}{2} (V_{DD} - V_{TN} - V_{DSQ_1})^2$

MOSFET

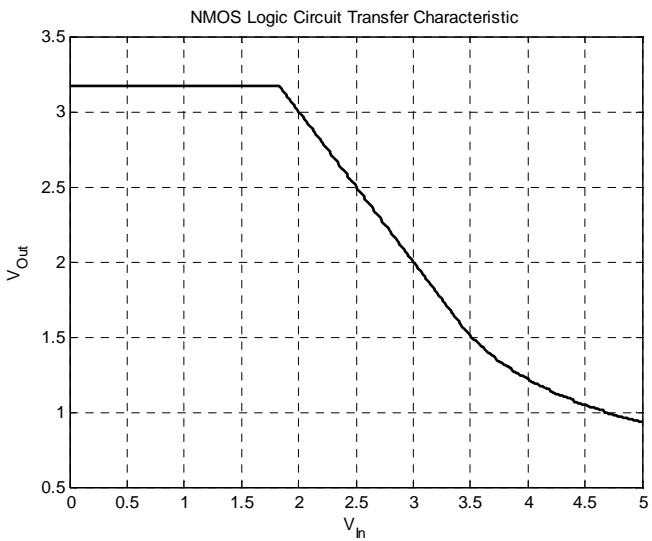- $V_{GS} = V_{in}$
- $K_P = .1233$
- $V_{TN} = 1.8$



% EE462 - Prelab 7 - Problem 7
 % Stephen Maloney

```
clear all; close all; clc;
```

```
% Set up N-MOS Mosfet Parameters
KP = .101;
VTN = 1.833;
```

```
% Set up circuit values
VDD = 5;
```

```
% Sweep input voltage from logic low (0) to logic high (5)
VIN = 0:.01:5;
```

```

VDS = 0:.01:5;

% Set up square law device load line
% It is zero on the far side of VDD-VTN
VOUTSP = 0:.01:VDD-VTN;
IDQ1GEN = KP/2*(VDD - VOUTSP - VTN).^2;
IDQ1 = [IDQ1GEN, zeros(1, length(VDS) - length(IDQ1GEN))];


disp('Generating TC...');


% Run through the input voltage values (VGS of the second mosfet)
% And see where the load line and the MOSFET curve intersect
for K = 1 : length(VIN)
    IDQ2 = nmos(VDS, VIN(K), KP, 1, 1, VTN);
    [Error, Eindex] = min(abs(IDQ1 - IDQ2));
    IDMatch(K) = IDQ2(Eindex(1));
    VDSMatch(K) = VDS(Eindex(1));
end

% Display final transfer characteristic
plot(VIN, VDSMatch, 'k', 'LineWidth', 2); grid on;
title('NMOS Logic Circuit Transfer Characteristic');
xlabel('V_{In}'); ylabel('V_{Out}');

```

8)

 

 


Generate two mosfet curves, find intersection for Q-point.

MOSFET

PMOS
 $K_p = .145$
 $V_{TP} = -2.8$
 $V_{SG} = V_{DD} - V_{in}$
 $V_{SD_{Q2}} = V_{DD} = V_{DS_{Q1}}$

NMOS
 $K_n = .1233$
 $V_{TN} = 1.8$
 $V_{GS} = V_{in}$
 $V_{DS} = 0 - V_{out}$

 CMOS Logic Circuit Transfer Characteristic



% EE462 - Prelab 7 - Problem 9
 % Stephen Maloney

clear all; close all; clc;

% Set up N-MOS Mosfet Parameters
 KP_N = .101;
 VTN = 1.833;

% Set up P-MOS Mosfet Parameters
 KP_P = .145;
 VTP = -2.8;

% Set up circuit values
 VDD = 5;


```

disp('Generating TC...');

% Sweep input voltage
VIN = 0:.01:5;
VDS = 0:.01:5;
VSD = VDD-VDS;

for K = 1 : length(VIN)
    % The PMOS can be treated as an NMOS by creative subscript use
    IDQ2 = nmos(VSD, VDD-VIN(K), KP_P, 1, 1, -1*VTP);
    IDQ1 = nmos(VDS, VIN(K), KP_N, 1, 1, VTN);

    % Find where the two curves intersect for the q-points
    [Error, Eindex] = min(abs(IDQ1 - IDQ2));
    IDMatch(K) = IDQ1(Eindex(1));
    VDSMatch(K) = VDS(Eindex(1));

    % DEBUG - Uncomment below to view intersection plot
    %plot(VDS, IDQ2, VDS, IDQ1, VDSMatch(K), IDMatch(K), 'o', 'LineWidth', 2);
    %title(['VIN = ' num2str(VIN(K))]);
    %pause(.0001);
    % END DEBUG
end

% Display final transfer characteristic
plot(VIN, VDSMatch, 'k', 'LineWidth', 2); grid on;
title('CMOS Logic Circuit Transfer Characteristic');
xlabel('V_{In}'); ylabel('V_{Out}');

```