
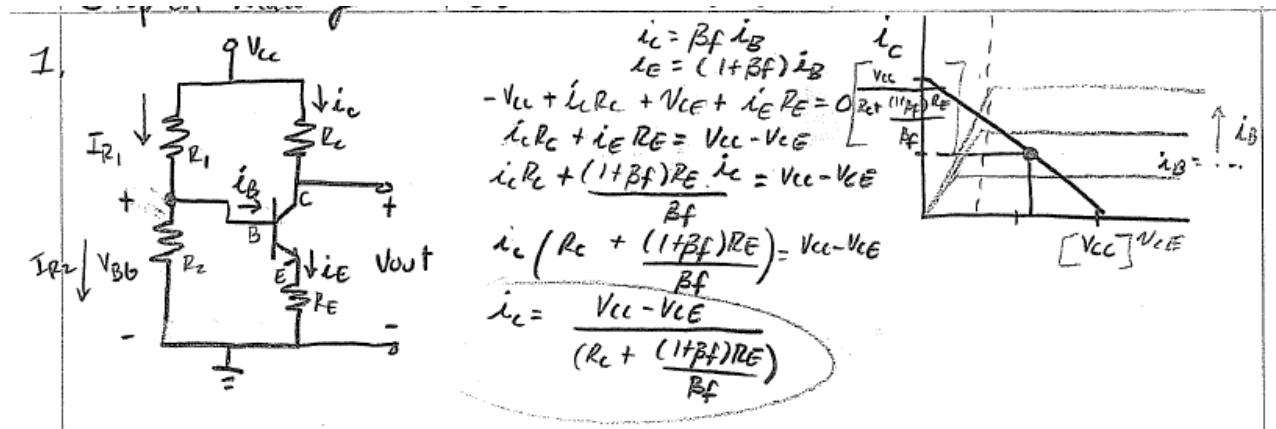


Prelab9 Solutions

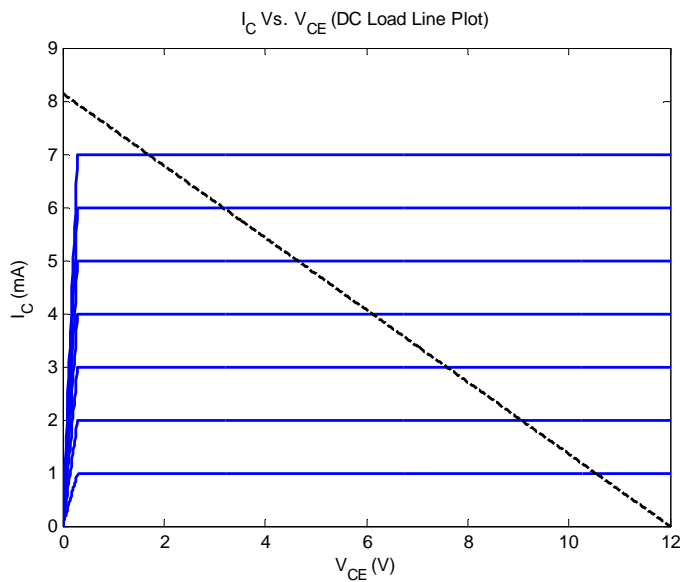

2)



% Prelab 8 - Problem 2
 % Stephen Maloney

clear all; clc; close all;

% Given parameters

Rc = 1e3;
 Re = 470;
 Vcc = 12;

% Set up the BJT curves

Bf = 200;
 Vce = linspace(0, 12, 1000);
 VceSat = .3;
 ibrange = linspace(5e-6, 35e-6, 7);

% Generate the load line

ill = (Vcc-Vce)/(Rc+((1+Bf)*Re)/Bf);

```

% Plot a range of ib values
for ib = ibrange
    ic = bjt(Vce, ib, Bf, VceSat);
    plot(Vce, ic*1e3, 'Linewidth', 2);
    hold on;
end

% Add load line
plot(Vce, ill*1e3, 'k--', 'LineWidth', 2);

% Label the graph
xlabel('V_C_E (V)'); ylabel('I_C (mA)');
title('I_C Vs. V_C_E (DC Load Line Plot)');

```

3.

$$V_{CE} = \frac{V_{CC}}{2} = 6V = V_{CEQ}$$

$$i_c = \left(\frac{V_{CC}}{R_C + \frac{(1+\beta_f)R_E}{\beta_f}} \right) \left(\frac{1}{2} \right) = 4.075 \text{ mA} = i_{cQ}$$

$$I_{R_1} = 100 I_B, \quad I_B = \frac{I_{cQ}}{\beta_f} = 20.375 \mu\text{A}$$

$$\therefore I_{R_1} = 2.0375 \text{ mA} \quad V_{BEF} = .6 \text{ V}$$

$$\frac{V_{CC} - V_{BB}}{R_1} = I_{R_1} \quad -V_{BB} + V_{BEF} + i_E R_E = 0 \quad i_E = \frac{(1+\beta_f) i_c}{\beta_f}$$



$$R_1 = \frac{V_{CC} - V_{BB}}{I_{R_1}} \quad V_{BB} = V_{BEF} + \frac{R_E (1+\beta_f) i_{cQ}}{\beta_f} = 2.5248 \text{ V}$$

$$R_1 = \frac{V_{CC} - \left[V_{BEF} + \frac{R_E (1+\beta_f) i_{cQ}}{\beta_f} \right]}{I_{R_1}} = 4.6504 \text{ k}\Omega = R_1$$

$$I_{R_2} = I_{R_1} - i_{BQ} \quad \frac{I_{R_1}}{V_{BB}} = R_2 = 1.2517 \text{ k}\Omega$$

$$I_{R_2} = 2.0171 \text{ mA}$$

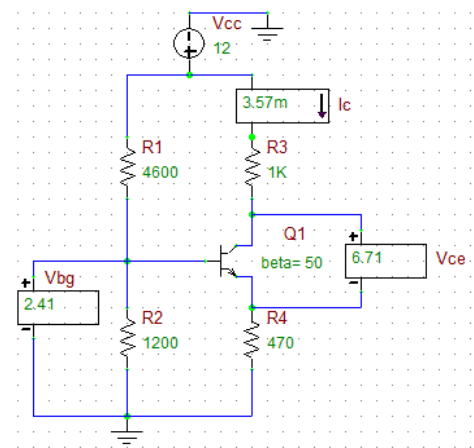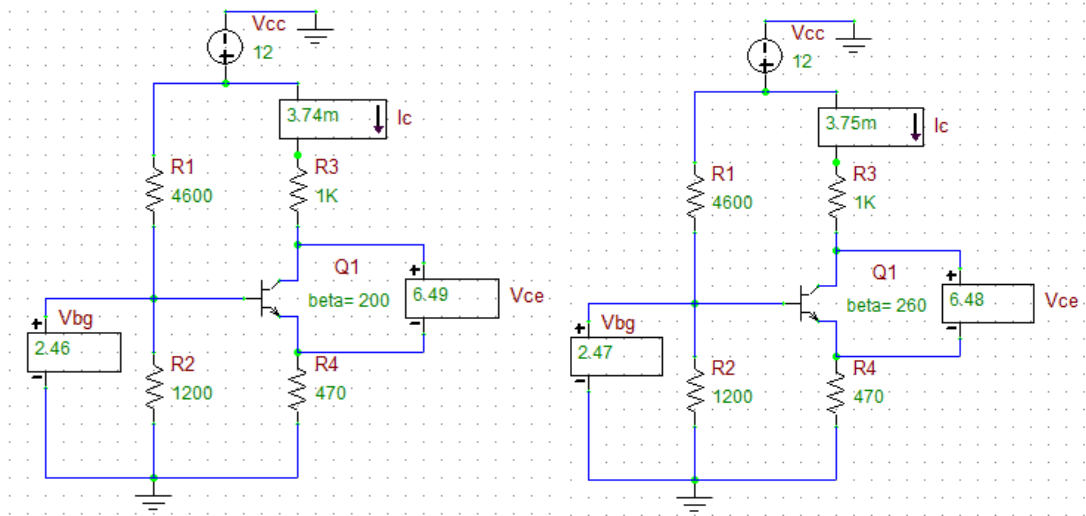4) As can be seen from the Spice DC-Operating point simulations below, β_f changing over quite a large range does not produce an extreme swing in operating point due to the feedback resistor, $R_E = R_4$.



5. a) $10 = e^{\frac{q}{kT} V_{BE}}$
 $\frac{kT}{q} \ln(10) = V_{BE} = .0576$

b) Taylor Series = $\sum_{n=0}^{\infty} \frac{f^{(n)}(a)(x-a)^n}{n!}$

$f(V_{BEQ}) = i_{BQ} = I_s e^{\frac{q V_{BEQ}}{kT}}$

$i_B(V_{BE}) = \frac{I_s e^{\frac{q V_{BEQ}}{kT}}}{i_{BQ}} + \frac{I_s \frac{q}{kT} e^{\frac{q V_{BEQ}}{kT}} (V_{BE} - V_{BEQ})}{kT} + \dots$

$i_B(V_{BE}) = i_{BQ} (1 + \frac{q}{kT} (V_{BE} - V_{BEQ}) + \dots)$

$r_{\pi} = \frac{kT}{q i_{BQ}}$

$\hat{i}_B = \frac{\hat{V}_{BE}}{r_{\pi}}$


$i_B(V_{BE}) = i_{BQ} + \frac{V_{BE} - V_{BEQ}}{r_{\pi}}$

$i_B(V_{BE}) = i_{BQ} + \frac{V_{BE} - V_{BEQ}}{r_{\pi}} \rightarrow y = mx + b \rightarrow i_b = \frac{1}{r_{\pi}} V_{BE} - \frac{V_{BEQ}}{r_{\pi}} + i_{BQ}$

To find \hat{i}_B , differentiate with respect to V_{BE} .

$\frac{d i_B}{d V_{BE}} = \frac{1}{r_{\pi}}, \frac{d i_B}{d V_{BE}} = \hat{i}_B \therefore \hat{i}_B = \frac{\hat{V}_{BE}}{r_{\pi}}$

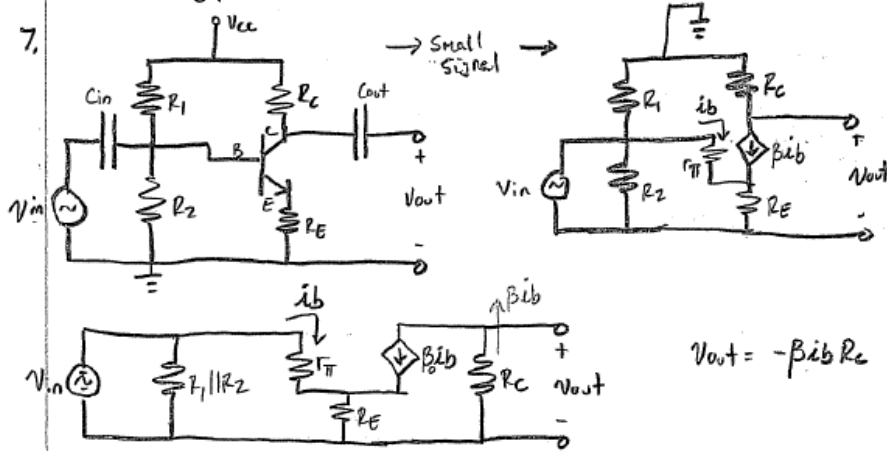6. $r_{\pi} = \frac{kT/q}{i_{BQ}} = \frac{(kT/q) \beta f}{i_{CQ}} = 1.227 k \Omega$




$-V_{in} + i_b r_{\pi} + (1 + \beta) i_b R_E = 0$
 $V_{in} = i_b (r_{\pi} + (1 + \beta) R_E)$
 $\frac{V_{in}}{r_{\pi} + (1 + \beta) R_E} = i_b$

$V_{out} = \frac{-\beta R_C V_{in}}{r_{\pi} + (1 + \beta) R_E}$

If $r_{\pi} \approx 0, \therefore \frac{V_{out}}{V_{in}} = \frac{-\beta_0 R_C}{(1 + \beta_0) R_E} \approx \frac{-R_C}{R_E}$

$\frac{V_{out}}{V_{in}} \approx -2$

8.

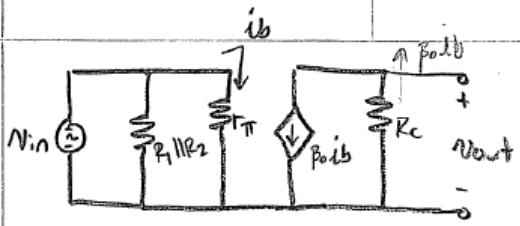

$$V_{out} = -\beta_0 i_b R_c \quad -V_{in} + i_b r_{\pi} = 0$$


$$i_b = \frac{V_{in}}{r_{\pi}}$$

$$V_{out} = -\beta_0 R_c \frac{V_{in}}{r_{\pi}}$$

$$\frac{V_{out}}{V_{in}} = -163$$

CAMERA

9.

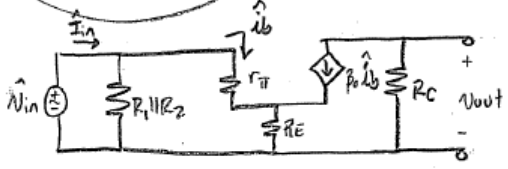

$$I_{in} = \frac{V_{in}}{R_1 || R_2} + i_b \quad V_{in} = i_b r_{\pi} + (1 + \beta_0) i_b R_E$$

$$V_{in} = i_b (r_{\pi} + (1 + \beta_0) R_E)$$

$$I_{in} = V_{in} \left(\frac{1}{R_1 || R_2} + \frac{1}{r_{\pi} + (1 + \beta_0) R_E} \right)$$

with RE

$$\therefore R_{in} |_{RE} = \frac{V_{in}}{I_{in}} = \frac{1}{\left(\frac{1}{R_1 || R_2} + \frac{1}{r_{\pi} + (1 + \beta_0) R_E} \right)} = 976.183 \Omega$$

$$V_{out} |_{loc} = -\beta_0 i_b R_c \quad I_{out} |_{sc} = -\beta_0 i_b \quad \therefore \frac{V_{out}}{I_{out}} = R_c = 1k\Omega = R_{out}$$

without RE

$$I_{in} = \frac{V_{in}}{R_1 || R_2} + \frac{V_{in}}{r_{\pi}} = V_{in} \left(\frac{1}{R_1 || R_2} + \frac{1}{r_{\pi}} \right)$$

$$\frac{V_{in}}{I_{in}} = \frac{1}{\left(\frac{1}{R_1 || R_2} + \frac{1}{r_{\pi}} \right)} = 546.763 \Omega = R_{in}$$

$$R_{out} = \text{same} = 1k\Omega$$

10.


$$\frac{1}{\omega R_{min} C} \ll C$$

$$\frac{1}{2\pi(8kHz)(50\Omega)} \ll C$$

$$.3\mu F \ll C$$

$$3\mu F \leq C \leq 30\mu F$$


11)

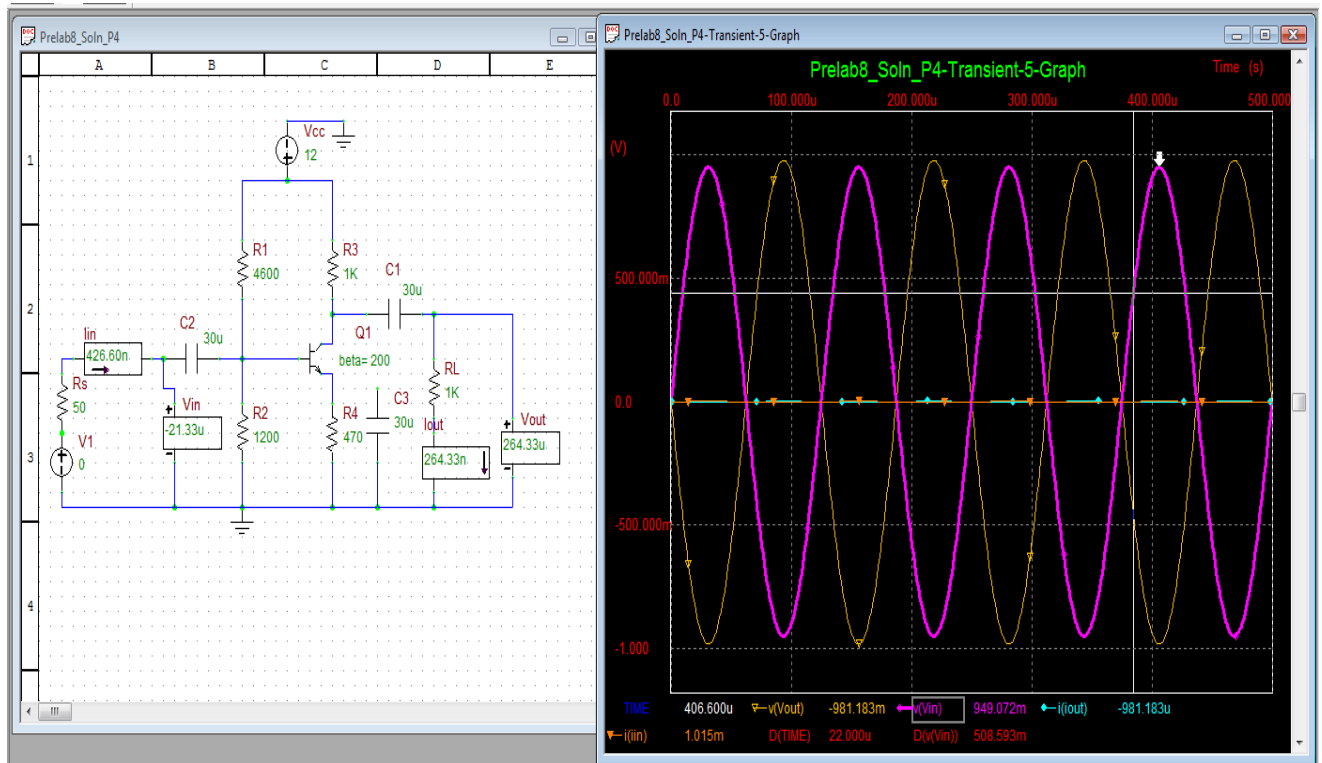

With $R_E = R_4$ in the circuit:

$$\frac{V_{Out}}{V_{In}} \approx -1.033 \quad \frac{I_{Out}}{I_{In}} \approx -0.967 \quad R_{In} \approx 935\Omega \quad \frac{V_{Out,Open}}{I_{Out,Short}} = R_{Out} \approx 1075.84\Omega$$

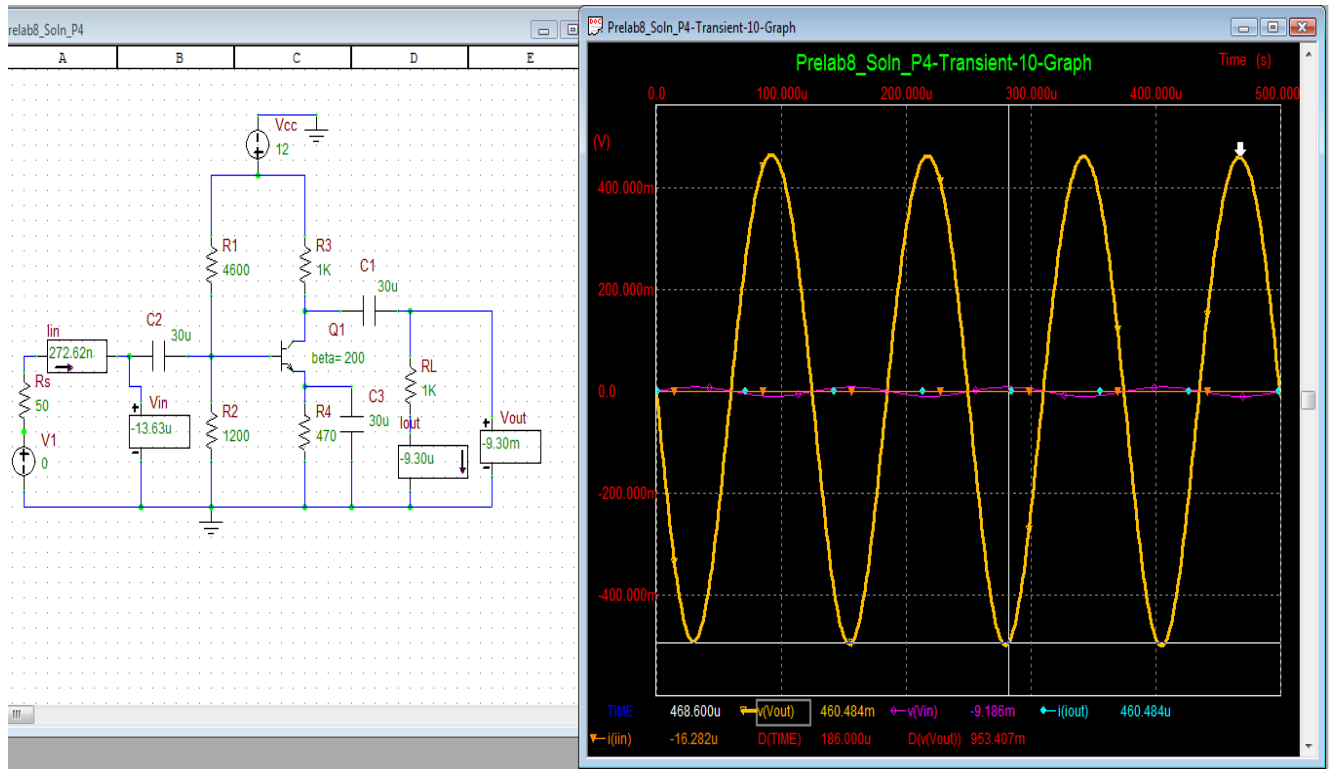Note - to measure R_{Out} you have to rerun the simulation first removing the load and measuring V_{out} to find the open circuit voltage output, then short the load and measure the short circuit current.



Without $R_E = R_4$ in the circuit:

$$\frac{V_{Out}}{V_{In}} \approx -50.13 \quad \frac{I_{Out}}{I_{In}} \approx -28.28 \quad \frac{V_{In}}{I_{In}} = R_{In} \approx 564.18\Omega \quad \frac{V_{Out,Open}}{I_{Out,Short}} = R_{Out} \approx 1065.69\Omega$$