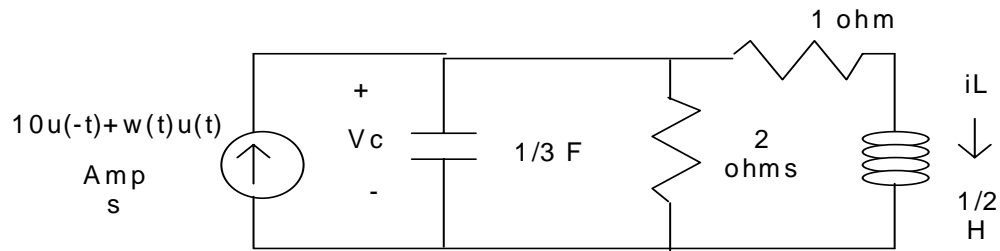


EE571 Solution to HW#1

1. a) Find the state variable model of the form  $\dot{x} = Ax + Bw$ ,  $x(0^+)$  for the following electrical network:



(Hint: Let  $x = \begin{bmatrix} v_c \\ i_L \end{bmatrix}$ ) ((make sure to include your initial conditions))

Solution: Let  $x = \begin{bmatrix} v_c \\ i_L \end{bmatrix}$ . Note that prior to  $t=0$ , the input is 10 amps and the capacitor acts like an open circuit while the inductor behaves as a short circuit. Thus,  $i_L(0^-)$  is 6.67 amps and  $V_c(0^-)$  is 6.67 volts. For  $t > 0$ , the input is  $w(t)$  and we can write a KCL and KVL to try to obtain our state equations:

$$\text{KCL at top node: } -w(t) + 1/3 \frac{dV_c}{dt} + \frac{V_c}{2} + i_L = 0$$

$$\text{Therefore, } \frac{dV_c}{dt} = -3/2 V_c - 3i_L + 3w(t)$$

KVL around loop:

$$1/2 \frac{di_L}{dt} - V_c + 2i_L = 0.$$

$$\text{Therefore, } \frac{di_L}{dt} = 2V_c - 4i_L$$

We can rearrange these two equations into the desired form:


$$\dot{x} = \begin{bmatrix} \dot{V}_c \\ \dot{i}_L \end{bmatrix} = \begin{bmatrix} -3/2 & -3 \\ 2 & -4 \end{bmatrix} \begin{bmatrix} V_c \\ i_L \end{bmatrix} + \begin{bmatrix} 3 \\ 0 \end{bmatrix} w(t), x(0) = \begin{bmatrix} 6.67 \\ 6.67 \end{bmatrix}$$

- b) English 101 Essay question: Briefly compare and contrast open-loop control versus closed-loop control

Solution: A closed-loop control utilizes feedback, that is process of returning a signal which occurs somewhere downstream in a process or system back to a point in the system before it was generated. Thus, the input which drives the system is a function of the output or states of the system and can therefore adapt to disturbances, etc.

An open-loop control implies that the input (control) is not a function of the output of the system (i.e., there is no *feedback* loop from output to input and thus the system is unable to adapt to any changes or disturbances which can be measured in the system output. However, open-loop control is generally much cheaper to implement as no sensors at the system output are needed nor comparators or subtractors at the system input.

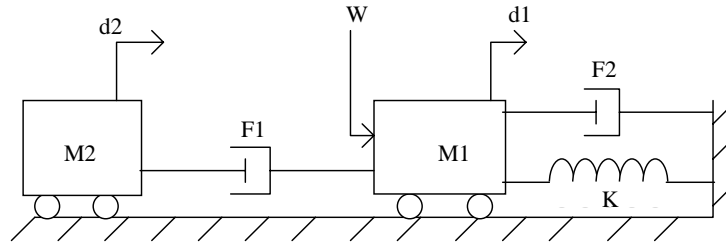- 2a) Write the state variable model for the following mechanical circuit



(Hint: Let  $x = [\dot{d}_1 \quad \dot{d}_2 \quad K(d_1)]^T$  where T means transpose)

Solution: Applying Newton's law at mass  $M_1$  we find:

$$\sum \text{Forces} = ma \Rightarrow w(t) - Kd_1 - F_2\dot{d}_1 - F_1(\dot{d}_1 - \dot{d}_2) = M_1\ddot{d}_1$$

or

$$\ddot{d}_1 = -(F_1 + F_2)/M_1\dot{d}_1 + F_1/M_1\dot{d}_2 - K/M_1d_1 + 1/M_1w$$

Similarly, we can apply Newton's law at mass  $M_2$  as follows:

$$\sum \text{Forces} = ma \Rightarrow -F_1(\dot{d}_2 - \dot{d}_1) = M_2\ddot{d}_2$$

or

$$\ddot{d}_2 = F_1/M_2\dot{d}_1 - F_1/M_2\dot{d}_2$$


Notice that these two equations involve the time derivatives of our first two state variables,  $\dot{d}_1$  and  $\dot{d}_2$ . To find an equation involving the time derivative of our last state variable,  $Kd_1$ , note that (obviously):

$$\frac{d}{dt}(Kd_1) = K(\dot{d}_1).$$

Or, putting all three equations together, we find:

$$\dot{x} = \begin{bmatrix} \ddot{d}_1 \\ \ddot{d}_2 \\ K(\dot{d}_1) \end{bmatrix} = \begin{bmatrix} -(F_1 + F_2)/M_1 & F_1/M_1 & -1/M_1 \\ F_1/M_2 & -F_1/M_2 & 0 \\ K & 0 & 0 \end{bmatrix} \begin{bmatrix} \dot{d}_1 \\ \dot{d}_2 \\ K(d_1) \end{bmatrix} + \begin{bmatrix} 0 \\ 1/M_2 \\ 0 \end{bmatrix} w$$

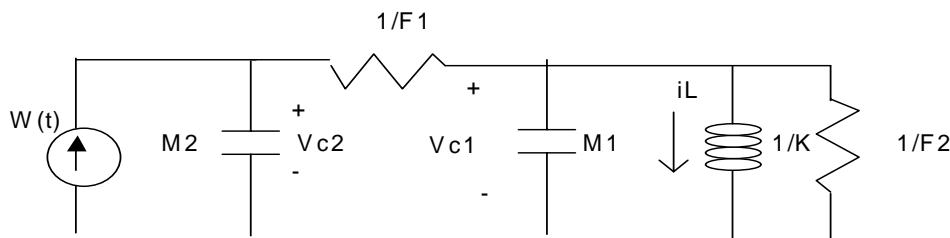b) Now write the state variable model for the following electrical circuit



(Hint: let  $x = [Vc_1 \quad Vc_2 \quad i_L]^T$ )

Solution: writing a KCL at the top rightmost node, produces:

$$-w(t) + F_1(Vc_1 - Vc_2) + M_2\dot{Vc}_1 = 0$$

or

$$\dot{Vc}_1 = -F_1/M_1Vc_1 + F_1/M_1Vc_2 + 1/M_1w$$

Similarly, we can apply a KCL at the top left node to find:

$$F_1(Vc_1 - Vc_2) + M_1 \dot{V}c_1 + i_L + F_2 Vc_1 = 0$$

or

$$\dot{V}c_2 = (F_2 + F_1) / M_1 Vc_1 - F_1 / M_1 Vc_2 - 1 / M_1 i_L$$

For our last equation, let's write a KVL involving the inductor voltage:

$$1 / K \frac{d}{dt}(i_L) = Vc_1.$$

Or, putting all three equations together, we find:

$$\dot{x} = \begin{bmatrix} \dot{V}c_1 \\ \dot{V}c_2 \\ \dot{i}_L \end{bmatrix} = \begin{bmatrix} -(F_1 + F_2) / M_1 & F_1 / M_1 & -1 / M_1 \\ F_1 / M_2 & -F_1 / M_2 & 0 \\ K & 0 & 0 \end{bmatrix} \begin{bmatrix} Vc_1 \\ Vc_2 \\ i_L \end{bmatrix} + \begin{bmatrix} 0 \\ 1 / M_2 \\ 0 \end{bmatrix} w$$

c) Do you see any similarities between your answers for part 2a) and 2b)?

Solution: They are the exact same equation! How can a mechanical and electrical circuit have the same model?! We'll find out on next lecture!