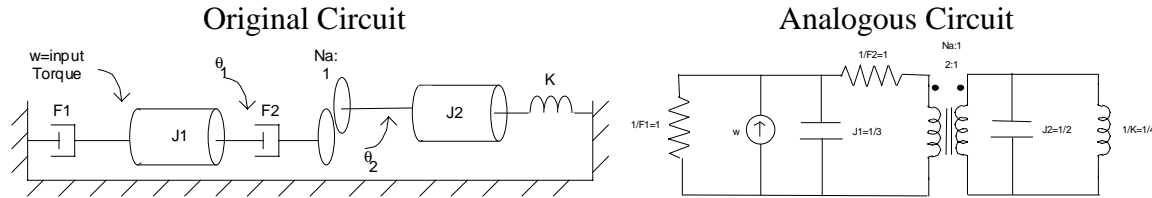



0. Have you picked a lab partner to work with you? Your first lab is coming soon!

1a) The analogous circuit for the first problem is:



where $F1=F2=1 \text{ Nms/rad}$, $K= 4 \text{ Nm/rad}$, $J1= 1/3 \text{ Nms}^2$, $J2= 1/2 \text{ Nms}^2$ and $Na=2$

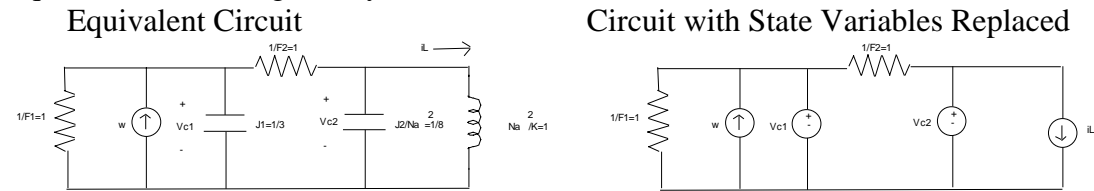The admittance seen to the left of the transformer is $Y=J2s+K/s$. Therefore, this admittance reflected across the transformer is: $Y_{eq}=Y/Na^2=(J2s+K/s)/Na^2$. This reflected admittance would come from a capacitor of $J2/Na^2$ in parallel with an inductor with a value of Na^2/K . Thus, the equivalent circuit is given by:




The state variable of the analogous electrical circuit is $x=[V_{c1} \ V_{c2} \ i_L]^T$. Thus:


$$\dot{x} = \begin{bmatrix} \dot{V}_{c1} \\ \dot{V}_{c2} \\ \dot{i}_L \end{bmatrix} = \begin{bmatrix} 1/C_1(i_{c1}) \\ 1/C_2(i_{c2}) \\ 1/L(v_L) \end{bmatrix} = \begin{bmatrix} 3(i_{c1}) \\ 8(i_{c2}) \\ 1(v_L) \end{bmatrix} = \begin{bmatrix} 3(i_{c1}|_{v_{c1}} + i_{c1}|_{v_{c2}} + i_{c1}|_{i_L} + i_{c1}|_w) \\ 8(i_{c2}|_{v_{c1}} + i_{c2}|_{v_{c2}} + i_{c2}|_{i_L} + i_{c2}|_w) \\ 1(v_L|_{v_{c1}} + v_L|_{v_{c2}} + v_L|_{i_L} + v_L|_w) \end{bmatrix} = \begin{bmatrix} 3(-2v_{c1} + 1v_{c2} + 0i_L + 1w) \\ 8(1v_{c1} - 1v_{c2} - 1i_L + 0w) \\ 1(0v_{c1} + v_{c2} + 0i_L + 0w) \end{bmatrix}$$

$$\text{or } \dot{x} = \begin{bmatrix} -6 & 3 & 0 \\ 8 & -8 & -8 \\ 0 & 1 & 0 \end{bmatrix} x + \begin{bmatrix} 3 \\ 0 \\ 0 \end{bmatrix} w$$

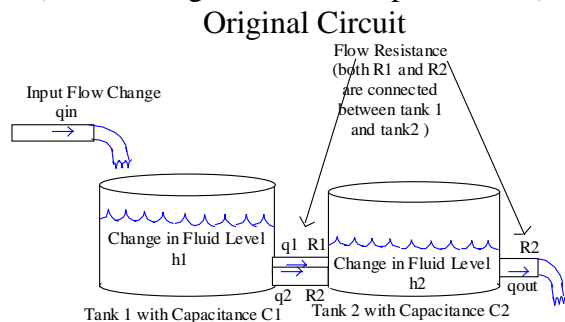1b) The analogous circuit for problem 1b) is:



Analogous Circuit

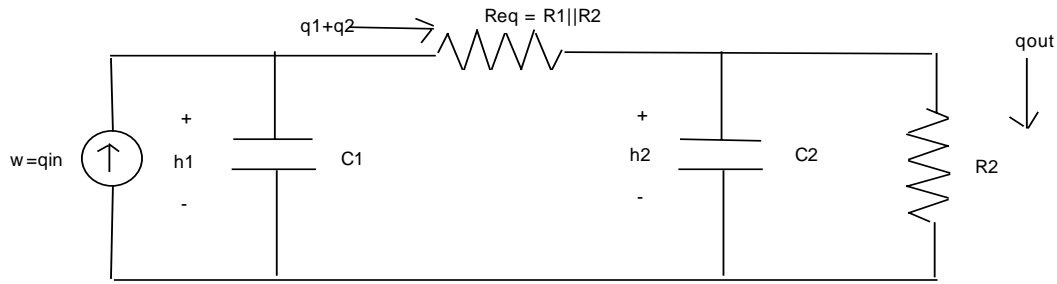

The state variable of the analogous electrical circuit is $x = [h_1 \ h_2]^T$. Thus:

$$\dot{x} = \begin{bmatrix} \dot{h}_1 \\ \dot{h}_2 \end{bmatrix} = \begin{bmatrix} 1/C_1 (i_{c1}) \\ 1/C_2 (i_{c2}) \end{bmatrix} = \begin{bmatrix} 1/C_1 (i_{c1}|_{h_1} + i_{c1}|_{h_2} + i_{c1}|_w) \\ 1/C_2 (i_{c2}|_{h_1} + i_{c2}|_{h_2} + i_{c2}|_w) \end{bmatrix} = \begin{bmatrix} 1/C_1 (-h_1/R_{eq} + h_2/R_2 + w) \\ 1/C_2 (h_1/R_1 - h_2(1/R_{eq} + 1/R_2) + 0w) \end{bmatrix}$$

$$\text{or } \dot{x} = \begin{bmatrix} \frac{-1}{R_{eq} C_1} & \frac{1}{R_{eq} C_1} \\ 1 & -R_{eq} R_2 \end{bmatrix} x + \begin{bmatrix} 1/C_1 \\ 0 \end{bmatrix} w \text{ where } R_{eq} = R_1 R_2 / (R_1 + R_2)$$

2a) i) First let's find the eigenvalues of A:

$$A = \begin{bmatrix} 2 & 1 \\ 1 & 2 \end{bmatrix} \Rightarrow |sI - A| = \begin{vmatrix} s-2 & -1 \\ -1 & s-2 \end{vmatrix} = s^2 - 4s + 3 = (s-1)(s-3) = 0 \therefore s_1 = 1 \text{ and } s_2 = 3$$

Next, let's find the eigenvectors of A:

$$[s_1 I - A] \underline{p}_1 = \begin{bmatrix} 1-2 & -1 \\ -1 & 1-2 \end{bmatrix} \begin{bmatrix} p_1 \\ p_2 \end{bmatrix} = \begin{bmatrix} -1 & -1 \\ -1 & -1 \end{bmatrix} \begin{bmatrix} p_{11} \\ p_{12} \end{bmatrix} = 0 \therefore \underline{p}_1 = \begin{bmatrix} p_{11} \\ p_{12} \end{bmatrix} = \begin{bmatrix} 1 \\ -1 \end{bmatrix}$$

$$[s_2 I - A] \underline{p}_2 = \begin{bmatrix} 3-2 & -1 \\ -1 & 3-2 \end{bmatrix} \begin{bmatrix} p_1 \\ p_2 \end{bmatrix} = \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} \begin{bmatrix} p_{21} \\ p_{22} \end{bmatrix} = 0 \therefore \underline{p}_2 = \begin{bmatrix} p_{21} \\ p_{22} \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

ii) First let's find the eigenvalues of A:

$$A = \begin{bmatrix} 0 & 2 \\ 12 & 2 \end{bmatrix} \Rightarrow |sI - A| = \begin{vmatrix} s & -2 \\ -12 & s-2 \end{vmatrix} = s^2 - 2s - 12 = (s-6)(s+4) = 0 \therefore s_1 = 6 \text{ and } s_2 = -4$$

Next, let's find the eigenvectors of A:

$$[s_1 I - A] \underline{p}_1 = \begin{bmatrix} 6 & -2 \\ -12 & 6-2 \end{bmatrix} \begin{bmatrix} p_1 \\ p_2 \end{bmatrix} = \begin{bmatrix} 6 & -2 \\ -12 & 4 \end{bmatrix} \begin{bmatrix} p_{11} \\ p_{12} \end{bmatrix} = 0 \therefore \underline{p}_1 = \begin{bmatrix} p_{11} \\ p_{12} \end{bmatrix} = \begin{bmatrix} 1 \\ 3 \end{bmatrix}$$

$$[s_2 I - A] \underline{p}_2 = \begin{bmatrix} -4 & -2 \\ -12 & -4-2 \end{bmatrix} \begin{bmatrix} p_1 \\ p_2 \end{bmatrix} = \begin{bmatrix} -4 & -2 \\ -12 & -6 \end{bmatrix} \begin{bmatrix} p_{21} \\ p_{22} \end{bmatrix} = 0 \therefore \underline{p}_2 = \begin{bmatrix} p_{21} \\ p_{22} \end{bmatrix} = \begin{bmatrix} 1 \\ -2 \end{bmatrix}$$

iii) First let's find the eigenvalues of A:

$$A = \begin{bmatrix} 0 & 2 \\ -16 & -8 \end{bmatrix} \Rightarrow |sI - A| = \begin{vmatrix} s & -2 \\ 16 & s+8 \end{vmatrix} = s^2 + 8s + 16 = (s+4+j4)(s+4-j4) = 0 \therefore s_1 = -4-j4 \text{ and } s_2 = -4+j4$$

Next, let's find the eigenvectors of A:

$$[s_1 I - A] \underline{P}_1 = \begin{bmatrix} -4-j4 & -2 \\ 16 & -4-j4+8 \end{bmatrix} \begin{bmatrix} p_1 \\ p_2 \end{bmatrix} = \begin{bmatrix} -4-j4 & -2 \\ 16 & 4-j4 \end{bmatrix} \begin{bmatrix} p_{11} \\ p_{12} \end{bmatrix} = 0 \therefore \underline{P}_1 = \begin{bmatrix} p_{11} \\ p_{12} \end{bmatrix} = \begin{bmatrix} 1 \\ -2-j2 \end{bmatrix}$$

$$[s_2 I - A] \underline{P}_2 = \begin{bmatrix} -4+j4 & -2 \\ 16 & -4+j4+8 \end{bmatrix} \begin{bmatrix} p_1 \\ p_2 \end{bmatrix} = \begin{bmatrix} -4-j4 & -2 \\ 16 & 4+j4 \end{bmatrix} \begin{bmatrix} p_{21} \\ p_{22} \end{bmatrix} = 0 \therefore \underline{P}_2 = \begin{bmatrix} p_{21} \\ p_{22} \end{bmatrix} = \begin{bmatrix} 1 \\ -2+j2 \end{bmatrix}$$