

## Homework 7

Due: Thursday, 10/19/00

**Problem 1:** Derive an expression for the input resistance of a common-gate amplifier connected to a load with resistance  $R_L$ . Your final answer should be in terms of  $g_m$ ,  $r_o$ , and  $R_L$ , and in the final step of this derivation you should assume that  $g_m \gg g_{mb}$  and  $g_{ds}$  (where  $g_{ds} = 1/r_o$ ).

**Problem 2:** Problem 3.11 from the textbook.

**Problem 3:** Problem 3.12 from the textbook. Assume  $\mu C_{OX} = 90\mu A/V^2$ .

**Problem 4: Common-Source Amplifier**

If we attach a pMOS transistor to the current mirror of Homework 6 Problem 5, we can create the common-source amplifier shown below with a pMOS amplifier transistor.

a) Using SPICE, determine the small signal gain of this amplifier if the pMOS device is  $W=18\mu m$  and  $L=2\mu m$ . Attach a 1pF capacitor to the output to create a defined high frequency roll-off. Be sure to use the Homework 6 Problem 5 circuit with a reference current close to 100 $\mu A$ . See circuit below.

\*Set  $V_{in}$  to 3.0V DC and click on Use AC.


\*You may want to use the .OP and .SHOW analysis to check if your circuit is biased correctly.

\*Perform a .AC analysis (start=10, stop=10Meg) and plot the gain (use  $\text{mag}(V(\text{out})/V(\text{in}))$  where mag = magnitude and 'out' and 'in' are the output and input node numbers).

\*Set the x-axis to log scale.

b) How could we increase the gain of this circuit? (Look back at HW6 Problem 1).

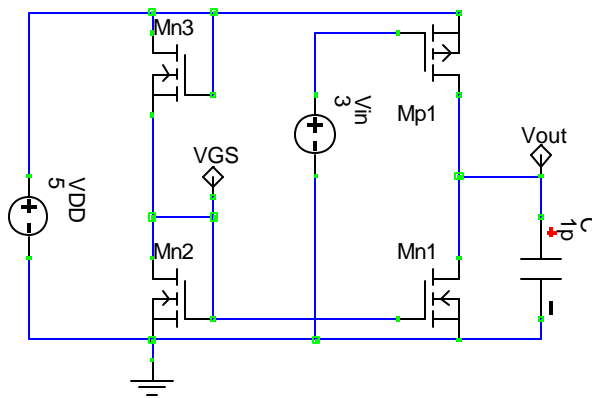c) Describe what you would expect to happen to the gain if we set the pMOS input transistor to  $W=40\mu m$  and  $L=2\mu m$ . Try this in SPICE and comment on the results.



**SPICE MOS Model Statements** for  $L=2\mu m$  transistors.

```
.model cmosn nmos level = 1 vto = 0.77 kp = 7.7e-5 gamma = 0.71 phi = 0.73
lambda = 0.0625 tox = 3e-8 ld = 2e-7 u0 = 670 nsub = 2e16
```

```
.model cmosp pmos level = 1 vto = -1.1 kp = 2.1e-5 gamma = 0.355 phi = 0.66
lambda = 0.053 tox = 3e-8 ld = 5e-8 u0 = 180 nsub = 5e15
```