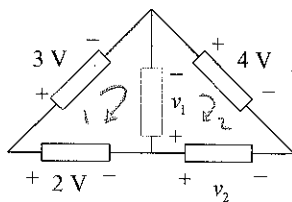


Instructions: There are a total of 13 questions on this exam. Read each question carefully before answering. Show all work on the final. If more room is needed, write on the back page, or request an additional sheet of paper from the proctor. As necessary, indicate units when writing an answer. Circle your final answers in each problem. If an answer is not circled, it is assumed that no final answer was derived.

P1	P2	P3	P4	P5	P6	P7
7 7 points	8 8 points	8 8 points	7 7 points	7 7 points	8 8 points	8 8 points
P8	P9	P10	P11	P12	P13	Total
8 8 points	7 7 points	8 8 points	8 8 points	8 8 points	8 8 points	100 100 points

P1. Basic Laws:

a) Given the network below, determine the branch voltages v_1 and v_2 .




use KVL

$$\text{Loop 1: } +3V - v_1 - 2V = 0 \Rightarrow v_1 = 1V$$

$$\text{Loop 2: } 4V - v_2 + v_1 = 0$$

$$v_2 = 5V$$

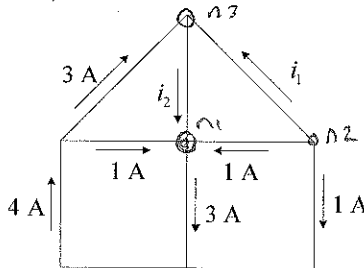b) Given the network below, determine the branch currents i_1 and i_2 .



$$\text{KCL: } n1: i_2 + 1A + 1A = 3A$$


$$i_2 = 1A$$

$$n2: i_1 + 1A + 1A = 0 \Rightarrow i_1 = -2A$$

$$\text{Check: } n3: 3A + i_1 = i_2$$

$$3A - 2A = 1A \checkmark$$

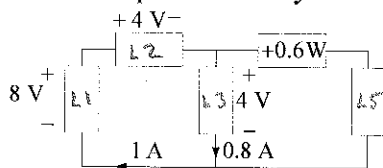c) For the network below, determine the power dissipated (or delivered) by each branch element. Write the power in the box representing each branch element. The power of 1 branch element is provided for you.



Power:

$$L1: P1 = 8V \times (-1A) = -8W$$

$$L2: P2 = 4V \times (+1A) = +4W$$

$$L3: P3 = 4V \times (0.8A) = +3.2W$$

Power Conservation:

$$P1 = P2 + P3 + 0.6W + P5 = 0$$

$$-8W + 4W + 3.2W + 0.6W + P5 = 0$$


$$\Rightarrow P5 = 0.2W$$

Final Exam

May 3, 2007, 1 - 3 pm

P2. Nodal Analysis

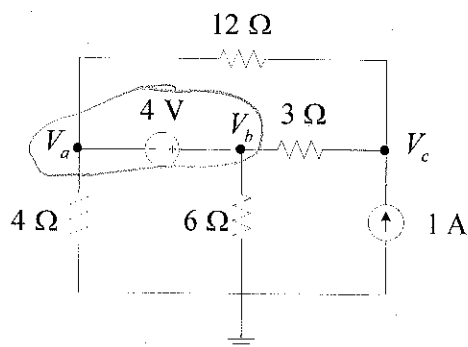You are to analyze the circuit below via a nodal analysis. Write down the equations necessary to solve for the node voltages using a nodal analysis. Express these in a matrix form. **Do not solve the equations.**



① Voltage constraint

$$V_b - V_a = 4V$$

② KCL

node c:
$$\frac{V_c - V_b}{3\Omega} + \frac{V_c - V_a}{12\Omega} - 1A = 0$$

$$\Rightarrow -\frac{V_a}{12} + \frac{5V_c}{12} - \frac{V_b}{3} = 1A$$

Super node:
$$\frac{V_a - 0}{4} + \frac{V_a - V_c}{12} + \frac{V_b - 0}{6} + \frac{V_b - V_c}{3} = 0$$


$$\Rightarrow \frac{1}{3}V_a + \frac{1}{2}V_b - \frac{5}{12}V_c = 0$$

Answer:

$$\begin{pmatrix} -1 & 1 & 0 \\ -1/12 & -1/3 & 5/12 \\ 1/3 & 1/2 & -5/12 \end{pmatrix} \begin{pmatrix} V_a \\ V_b \\ V_c \end{pmatrix} = \begin{pmatrix} 4 \\ 1 \\ 0 \end{pmatrix}$$

P3. Mesh Analysis

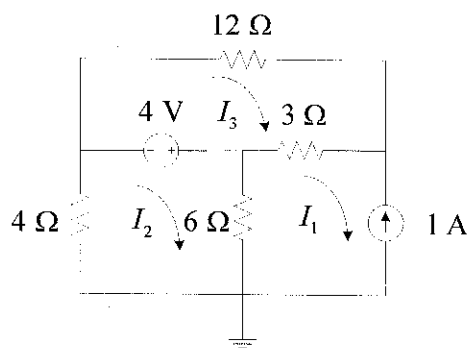You are to analyze the circuit below via a mesh analysis. Write down the equations necessary to solve for the mesh currents using a mesh. Express these in a matrix form. **Do not solve the equations.**



Current Constraint

$$I_1 = -1 \text{ A}$$

KVL:

$$\text{Loop 2: } 4\Omega (I_2) = 4\text{V} + 6\Omega (I_2 - I_1) = 0$$

$$\boxed{-6I_1 + 10I_2 = 4\text{V}}$$

$$\text{Loop 3: } 12I_3 + 3\Omega (I_3 - I_1) + 4\text{V} = 0$$

$$\boxed{-3I_1 + 15I_3 = -4}$$

Answer:



$$\begin{pmatrix} 1 & 0 & 0 \\ -6 & 10 & 0 \\ -3 & 0 & 15 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} -1 \\ 4 \\ -4 \end{pmatrix}$$

Final Exam


May 3, 2007, 1 - 3 pm

P4. Source Transformation

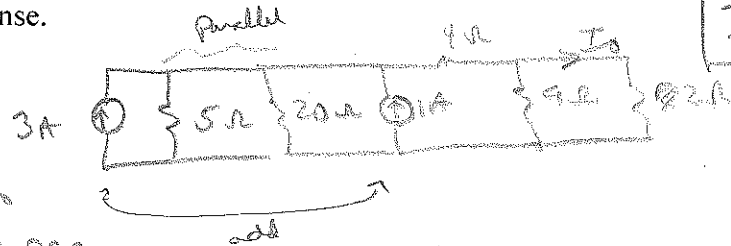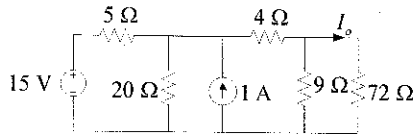Applying appropriate source transformations, determine the current I_o in the circuit below assuming a DC steady state response.




$I_o = \frac{1}{9} A$

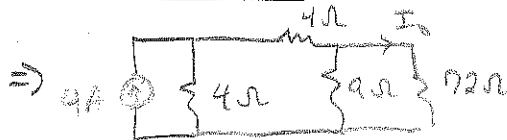

Current division


$I_o = 2A \times \frac{1}{72}$

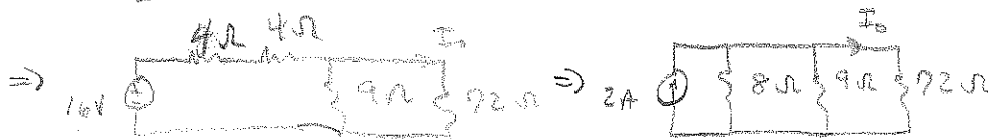$\frac{1}{8} + \frac{1}{9} + \frac{1}{72}$




P5. Thevenin/Norton Equivalence

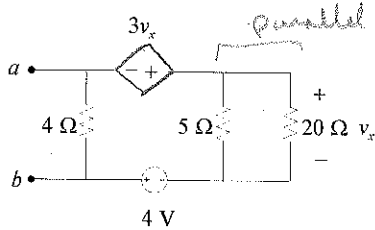Determine the Thevenin equivalent circuit relative to terminals $a-b$ in the DC circuit below. = $2A \times \frac{1}{9+8+1}$



$I_o = \frac{1}{9} A$

① Find open circuit voltage

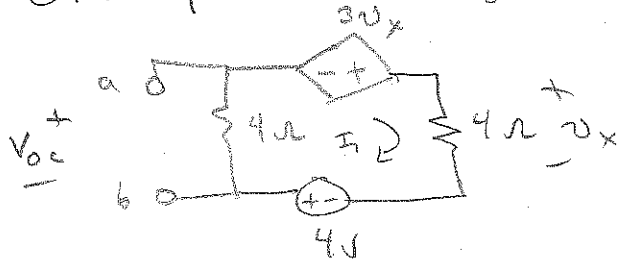

KVL: $-4V + 4I_1 - 3v_x + 4I_1 = 0$


$v_x = 4I_1$

$\Rightarrow 4V = 4I_1 - 3(4I_1) + 4I_1$

$4V = -4I_1 \Rightarrow I_1 = -1A$

$V_{oc} = -I_1 \times 4\Omega = +4V$

② Find R_{Th}

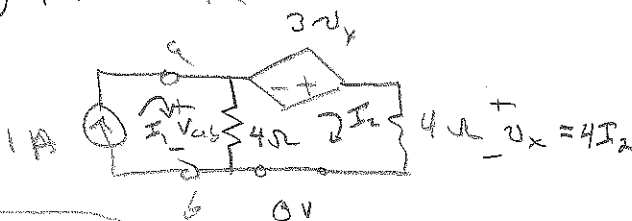


current constant $I_1 = 1A$

KVL: $4(I_2 - I_1) - 3v_x + v_x = 0$

$4(I_2 - I_1) - 2(4I_2) = 0$

$4I_2 - 4 - 8I_2 = 0$

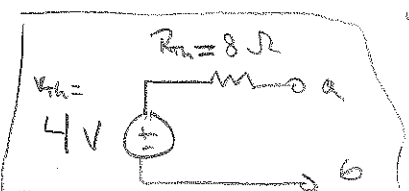$R_{Th} = \frac{V_{ob}}{I_1} = \frac{4(I_1 - I_2)}{1A} = \frac{8V}{1A} = 8\Omega \Rightarrow I_2 = -1A$




Final Exam


May 3, 2007, 1 - 3 pm

P6. Superposition

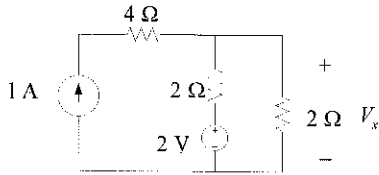Determine the voltage V_x in the network below by using *superposition*.




① open ckt 1A source

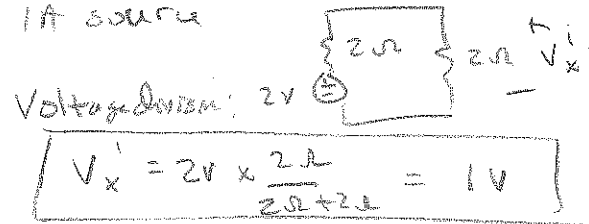

Voltage division: $2V$

$$V_x' = 2V \times \frac{2\Omega}{2\Omega + 2\Omega} = 1V$$

② short ckt 2V source ; current div:

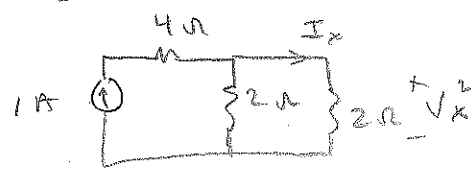

$$I_x = 1A \times \frac{1}{\frac{1}{2} + \frac{1}{2}} = \frac{1}{2} A$$


$$\therefore V_x'' = 2\Omega \times \frac{1}{2} A = 1V$$

$$V_x = V_x' + V_x'' = 2V$$

P7. Op-Amp Circuit

The network below contains an *ideal operational-amplifier*. Find the output voltage V_o .

Nodal analysis

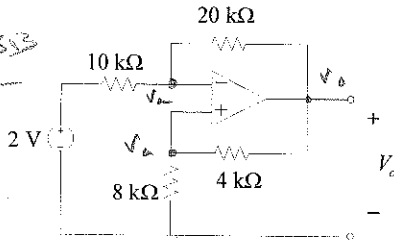

KCL at a^+ :

$$\frac{V_a}{8k\Omega} + \frac{V_a - V_o}{4k} = 0$$

$$\Rightarrow V_a \left(\frac{1}{8k} + \frac{1}{4k} \right) = \frac{V_o}{4k}$$

$$\Rightarrow \boxed{V_a = \frac{2}{3} V_o} \quad \text{or} \quad \boxed{V_o = \frac{3}{2} V_a}$$

KCL at a^- :

$$\left(\frac{V_a - 2V}{10k} + \frac{V_a - V_o}{20k} = 0 \right) \times 20k$$

$$\Rightarrow (2V_a - 4V) + V_a - V_o = 0$$

$$3V_a - V_o = 4V$$

from above,

$$V_a = \frac{2}{3} V_o \Rightarrow 3 \left(\frac{2}{3} V_o \right) - V_o = 4V$$


$$\therefore \boxed{V_o = 4V}$$

Final Exam

May 3, 2007, 1 - 3 pm

P8. Energy Storage Elements

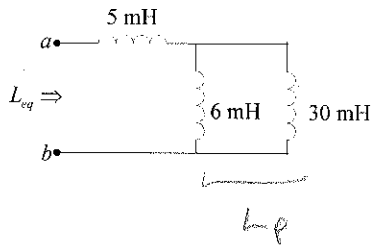
a) Given the network below, find the total network inductance.



$$L_p = \frac{1}{\frac{1}{6mH} + \frac{1}{30mH}} = \frac{30mH}{5+1} = 5mH$$

$$L_{eq} = 5mH + 5mH = 10mH = L_{eq}$$

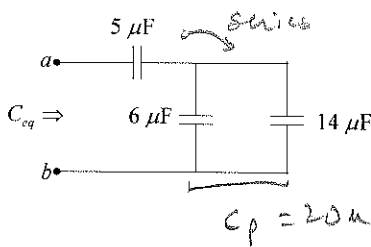
b) Given the network below, find the total network capacitance.



$$C_{eq} = \frac{1}{\frac{1}{5\mu F} + \frac{1}{20\mu F}} = \frac{20\mu F}{4+1} = 4\mu F$$

$$C_{eq} = 4\mu F$$

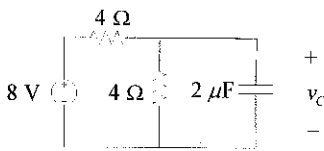c) In the circuit below, the DC source has been on for a very long time. What is the energy stored in the capacitor?




$$V_c(\infty) = \frac{4}{4+4} \times 8V = 4V$$

$$W_c = \frac{1}{2} CV^2 = \frac{1}{2} \times 2\mu F \times 4^2$$

$$W_c = 16\mu J = 16 \times 10^{-6} J$$

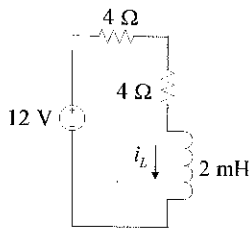c) In the circuit below, the DC source has been on for a very long time. What is the energy stored in the inductor?



$$i_L(\infty) = \frac{12V}{8\Omega} = \frac{3}{2} A$$

$$W_L = \frac{1}{2} LI^2 = \frac{1}{2} \times 2mH \times \left(\frac{3}{2}\right)^2$$


$$W_L = \frac{9}{4} mJ = \frac{9}{4} \times 10^{-3} J$$

Final Exam

May 3, 2007, 1 - 3 pm


P9. First-Order Transient Circuits

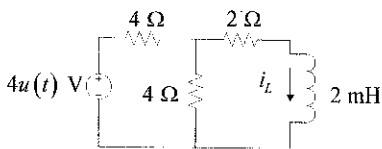The network below is driven by a transient voltage source $v_s(t) = 4u(t)$. Determine the inductor current $i_L(t)$.




Find by the Thevenin equivalent circuit

$V_{oc} = 2u(t) V$

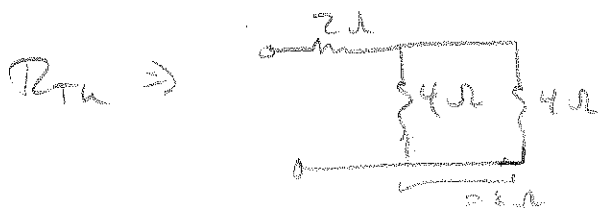

$R_{Th} = 4 \Omega$

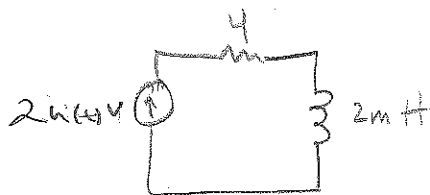

$i_L(0^-) = 0$

$i_L(\infty) = \frac{1}{2} A$

$R = 4 \Omega, \tau = \frac{L}{R} = \frac{2 mH}{4 \Omega} = \frac{1}{2} ms$

$\tau = \frac{1}{2} \times 10^{-3} s; \frac{1}{\tau} = 2000 s^{-1}$

$i_L(t) = \left[(i_L(0^-) - i_L(\infty)) e^{-t/\tau} + i_L(\infty) \right] u(t)$

$i(t) = \left[\frac{1}{2} (1 - e^{-2000t}) \right] u(t)$

$i(t) = \begin{cases} 0, & t < 0 \\ \frac{1}{2} (1 - e^{-2000t}), & t > 0 \end{cases}$


Final Exam

May 3, 2007, 1 - 3 pm

P10. Second-Order Transient Circuits

In the circuit below, the switch connecting the DC source to the network has been closed for a very long time. The switch then opens at $t = 0$, disconnecting the source.

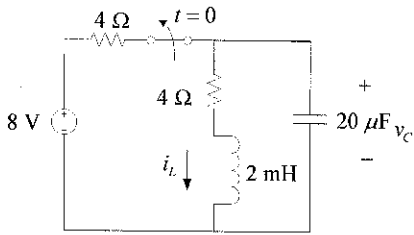- a) Determine the inductor current at time $t = 0$.
- b) Determine the capacitor voltage at time $t = 0$.
- c) Determine the derivative of the capacitor voltage at time $t = 0^+$.
- d) Determine the steady state capacitor voltage at time $t = \infty$.
- e) Is the series RLC circuit (for time $t > 0$) under-damped, critically damped, or over damped?




$(t > 0)$ Steady state w/ switch closed.

inductor = short ckt
capacitor = open ckt

a) $i_L = \frac{8V}{8\Omega} = 1A \quad \therefore \boxed{i_L(0^-) = 1A}$

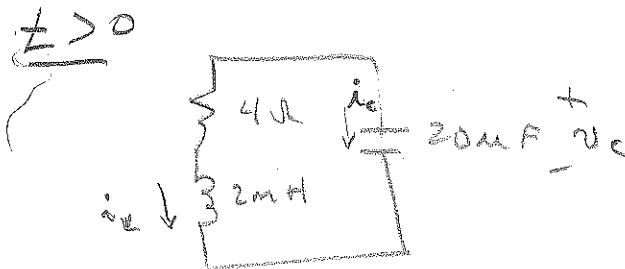b) $\boxed{v_C(0^-) = 4\Omega \times 1A = 4V}$



c) $i_C = C v_C' = -i_L$

$\therefore C v_C'(0^+) = -i_L(0^+) = -i_L(0^-)$

$v_C'(0^+) = \frac{-i_L(0^-)}{C}$

$v_C'(0^+) = \frac{-1A}{20 \times 10^{-6} F} = -50 \times 10^3$

$\boxed{v_C'(0^+) = -50 \times 10^3}$

d) $v_C(\infty) = 0$

e) $\alpha = \frac{R}{2L}$ (series RLC) $= \frac{4\Omega}{2 \times 2 \times 10^{-3}} = 1000 s^{-1}$

$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2 \times 10^{-3} \times 20 \times 10^{-6}}} = \frac{1}{\sqrt{4 \times 10^{-8}}} = \frac{1}{2} \times 10^4 = 5,000 \text{ rad/s}$

$\omega_0 > \alpha \quad \therefore \boxed{\text{Under damped}}$

Final Exam

May 3, 2007, 1 - 3 pm

P11. AC-Steady State - Phasors and Impedance

A network is driven by an AC steady state sinusoidal voltage source $v_s(t) = 4\cos(2t - \pi/3)$ V.

a) Express the time-dependent sinusoidal source voltage as a phasor:

$$\tilde{V}_s = 4 e^{-j\pi/3} = |4 \angle -60^\circ \text{ V}|$$

b) There is a 4 H inductor in the network. Determine the impedance of the inductor.

$$\omega = 2 \text{ rad/s} \quad Z_L = j\omega L = j \times 2 \text{ rad/s} \times 4 \text{ H} = | +j8 \Omega |$$

c) There is a 50 mF capacitor in the network. Determine the impedance of the capacitor.

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j \times 2 \times 50 \times 10^{-3}} = | -j10 \Omega |$$


d) A phasor voltage in the network is $\tilde{V}_x = 5 \angle 45^\circ$. Determine the actual time-dependent voltage $v_x(t)$.

$$v_x(t) = \text{Re} \{ \tilde{V}_x e^{j2t} \} = \text{Re} \{ 5 e^{j\pi/4} e^{j2t} \}$$

$$| v_x(t) = 5 \cos(2t + \pi/4) \text{ V} |$$


P12 AC-Steady State Analysis

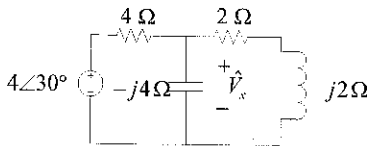The network below is expressed in the phasor domain. Determine the phasor voltage \tilde{V}_x .



series = $2 + j2 \Omega$
parallel: Z_p
 $Z_p = 4 \Omega$
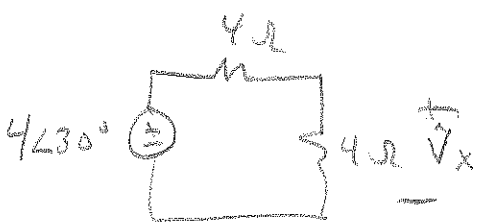
$$Z_p = \frac{1}{\frac{1}{-4j} + \frac{1}{2+j2}} = \frac{-4j}{1+j-2j} = \frac{-4j(1+j)}{1-j-2j} = \frac{4-4j(1+j)}{1-j(1+j)} = \frac{4+4j-4j+4}{1+1} = \frac{8}{2} = 4 \Omega$$



By voltage divider


$$| \tilde{V}_x = 2 \angle 30^\circ |$$

Final Exam

May 3, 2007, 1 - 3 pm

P13 AC-Steady State Analysis

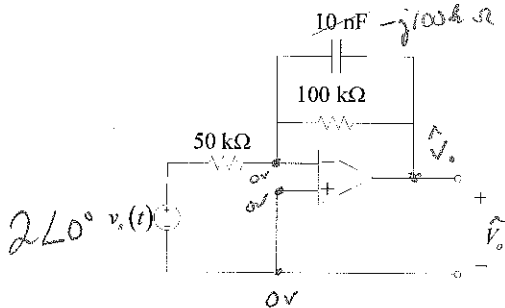The network below contains an *ideal operational-amplifier* driven by an AC steady-state sinusoidal source $v_s(t) = 2 \cos(1000t)$ V. Find the sinusoidal output voltage $v_o(t)$.



$$\omega = 1000 \text{ rad/s}$$

$$Z_c = \frac{1}{j \cdot 1000 \cdot 10 \times 10^{-9} \text{ F}} = -j100 \text{ k}\Omega$$

Nodal analysis:

$$\text{KCL at } 0^-: \left(\frac{0 - 2\angle 0^\circ}{50 \text{ k}\Omega} + \frac{0 - V_o}{100 \text{ k}\Omega} + \frac{0 - V_o}{-j100 \text{ k}\Omega} = 0 \right) \times 100 \text{ k}\Omega$$

$$-4\angle 0^\circ - V_o - \frac{V_o}{-j} = 0$$

$$V_o(-1-j) = 4\angle 0^\circ$$

$$V_o = \frac{4}{-1-j} = \frac{-4+4j}{2} = -2+2j$$

$$\frac{4(-1+j)}{(-1-j)(-1+j)} = \frac{-4+4j}{2}$$

$$V_o = 2\sqrt{2} \angle 135^\circ$$

$$v_o(t) = \text{Re} \left(2\sqrt{2} e^{j\frac{3\pi}{4}} e^{j2t} \right) \text{ V}$$

$$v_o(t) = 2\sqrt{2} \cos \left(1000t + \frac{3\pi}{4} \right) \text{ V}$$