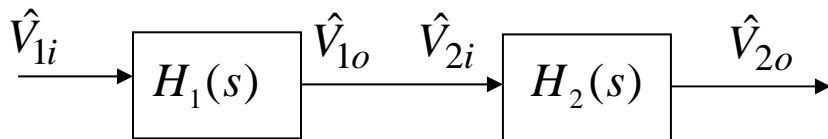


Cascading Filter Stages:

Given two active op-amp filter circuits with transfer functions $H_1(s)$ and $H_2(s)$. By definition, the op-amp circuit has a large input and output impedance.

In the limit that the input and output impedances tend to infinity, then cascading the filters yields a transfer function equal to the product of the individual circuit transfer functions:

$$H_T(s) = H_1(s)H_2(s)$$



$$H_T(s) = \frac{\hat{V}_{2o}}{\hat{V}_{1i}} = \left(\frac{\hat{V}_{1o}}{\hat{V}_{1i}} \right) \left(\frac{\hat{V}_{2o}}{\hat{V}_{2i}} \right) = H_1(s)H_2(s)$$


(If the output impedance of H_1 , or the input impedance of H_2 are not large, this relationship is no longer true)

Example: Sketch the transfer function magnitude of a first-order low-pass filter (with $A_v = 2$ and $f_c = 1$ kHz) in series with a second order band-reject filter (with $f_0 = 500$ Hz, $B = 200$ Hz, and $A_v = 1$).



Solution:

$$H_{LP}(s) = \frac{A_v}{1 + \frac{s}{\omega_c}} = \frac{2}{1 + \frac{s}{2\pi \cdot 1 \times 10^3}},$$
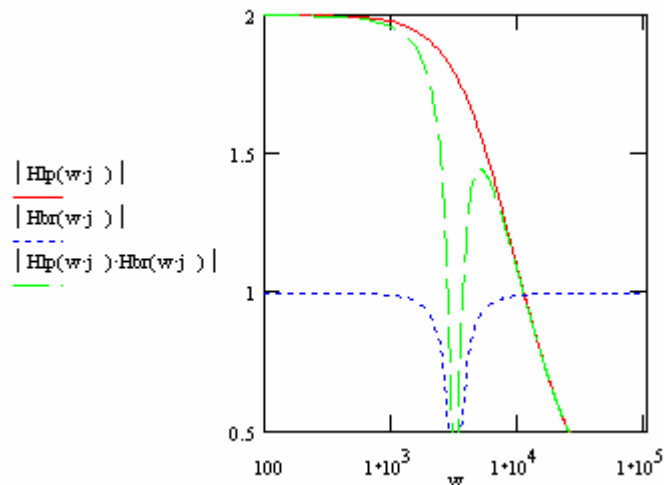
$$H_{BR}(s) = \frac{(s^2 + \omega_o^2)A_v}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2} = \frac{(s^2 + (2\pi \cdot 500)^2) \cdot 1}{s^2 + 2\pi \cdot 200s + (2\pi \cdot 500)^2}$$




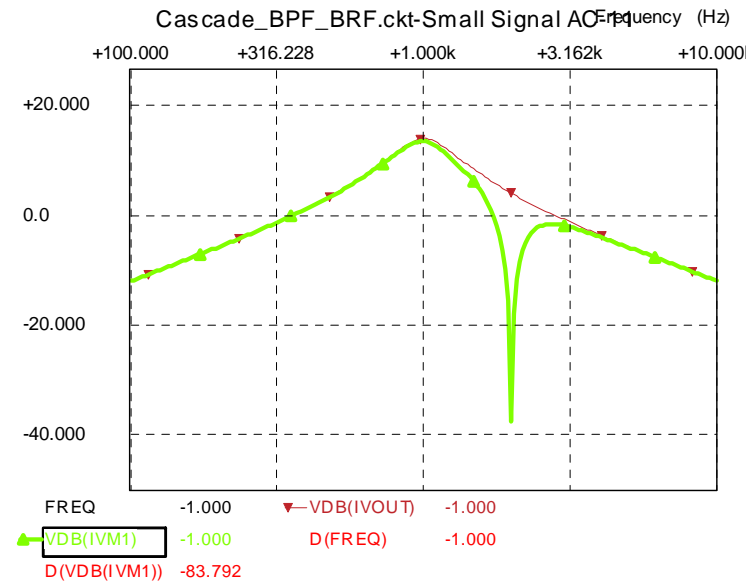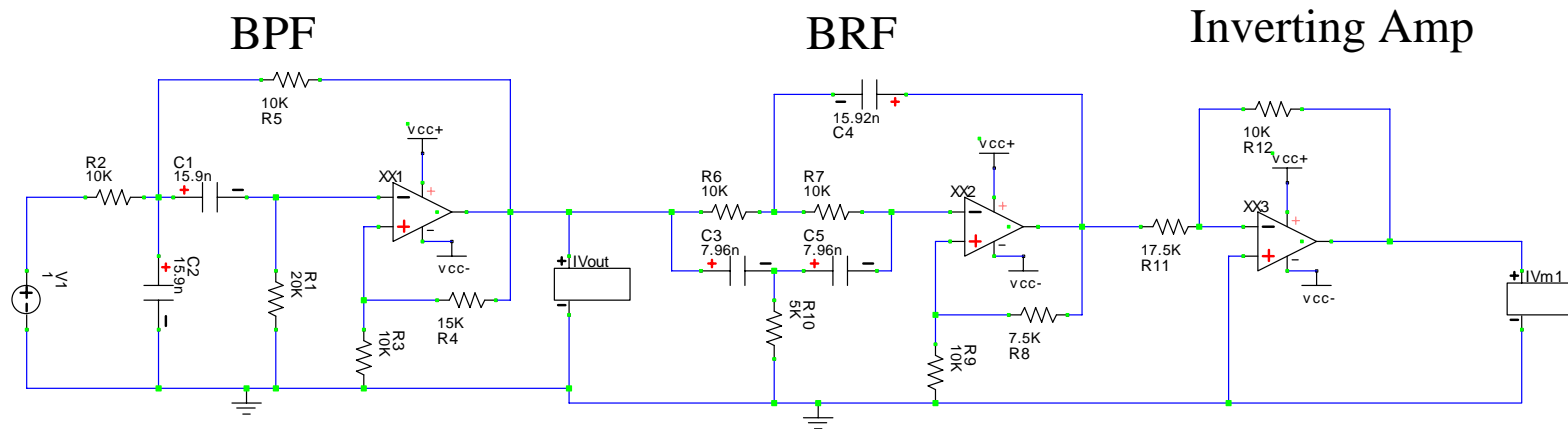Example: Cascade a Second-Order Sallen Key BPF ($f_0 = 1 \text{ kHz}$, $Q = 2$, $A_v = 14\text{dB}$) in series with a second order Sallen Key band-reject filter (with $f_0 = 2 \text{ kHz}$, $Q = 2$, and $A_v = 1.75$). The total gain is adjusted to 14 dB through an inverting amp.




Parallel Combination of Filters

Summing Amplifier:

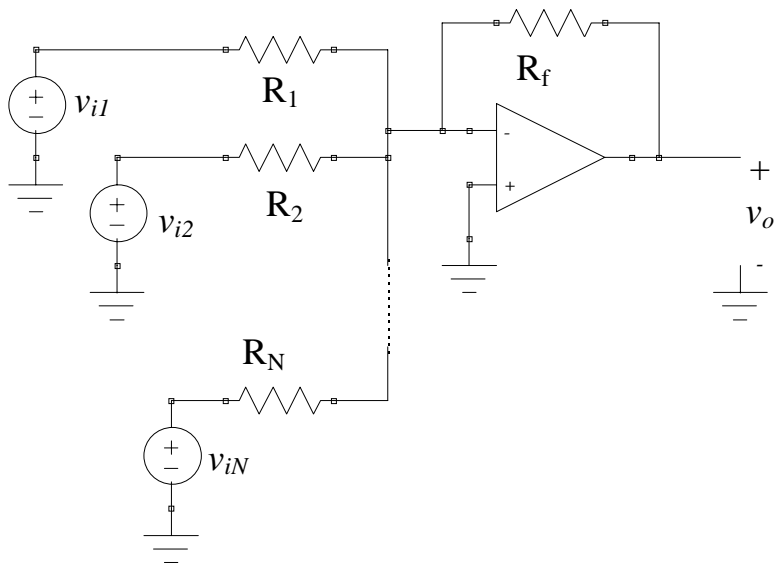

$$v_o = -\left(\frac{R_f}{R_1}v_{i1} + \frac{R_f}{R_2}v_{i2} + \dots + \frac{R_f}{R_N}v_{iN}\right)$$

Differential Amplifier:

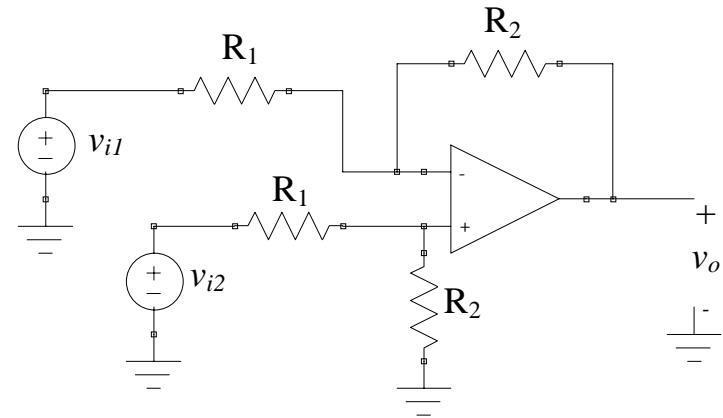


$$v_o = \frac{R_2}{R_1}(v_{i2} - v_{i1})$$

Adding Outputs of Filter Stages:

Given two filter circuits with transfer functions $H_1(s)$ and $H_2(s)$, a circuit composed of these circuits connected in parallel with a common input and their outputs summed together (through a summing amp) has a transfer function equal to the scaled sum of the individual transfer functions $H_T(s) = \alpha_1 H_1(s) + \alpha_2 H_2(s)$, provided that the connection of these circuits does not significantly alter the output resistance or input resistance of these circuits (i.e. no loading effects).
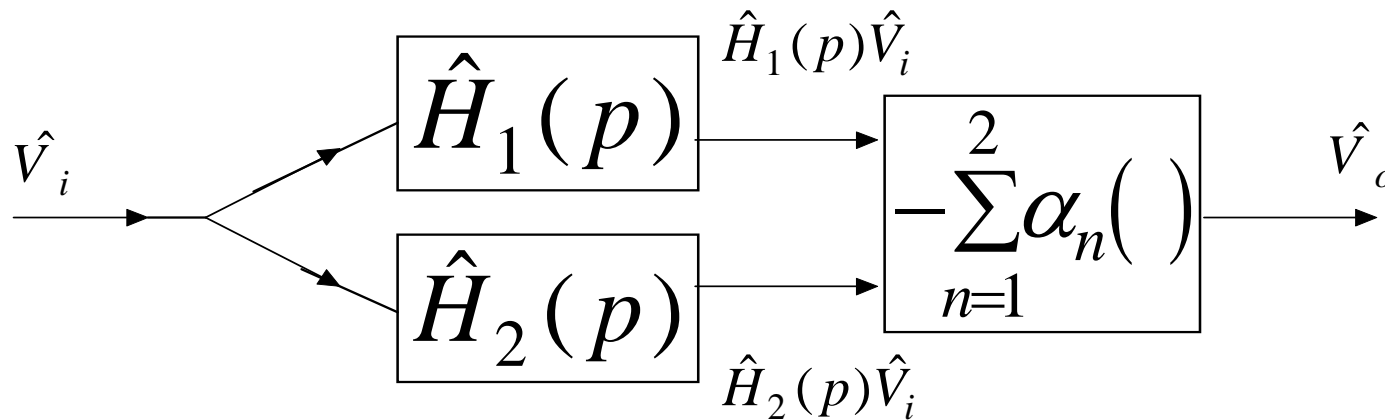
$$\hat{V}_o = -\alpha_1 H_1(s) \hat{V}_i - \alpha_2 H_2(s) \hat{V}_i$$




$$\Rightarrow H_T(s) = \frac{\hat{V}_o}{\hat{V}_i} = -\alpha_1 H_1(s) - \alpha_2 H_2(s)$$

Example:

You are to Sum three BPF's using Sallen-Key Filters

Top Level Design:


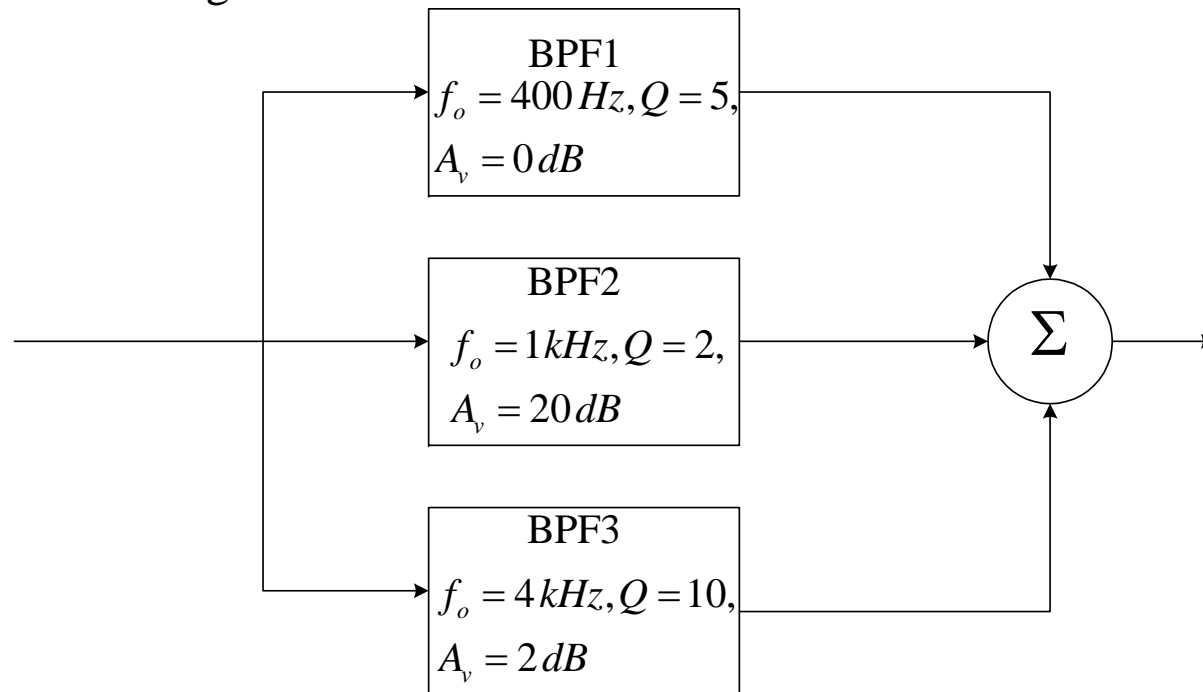


Design ($\omega_o = 1/RC$, $Q = 1/(3 - A)$, $A_v = A/(3 - A)$):


BPF1: $R = 10 \text{ K}$, $C = 39.79 \text{ nF}$, $A = 3 - 1/Q = 2.8$, $A_v = 14$. Therefore, Σ -amp needs gain $1/14$.

BPF2: $R = 10 \text{ K}$, $C = 15.92 \text{ nF}$, $A = 3 - 1/Q = 2.5$, $A_v = 5$. Therefore, Σ -amp needs gain 2

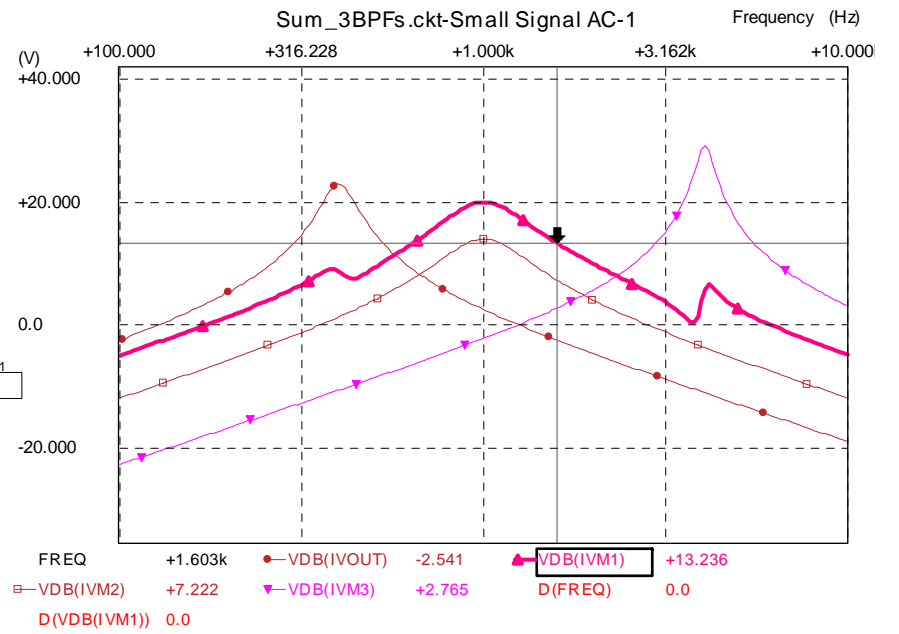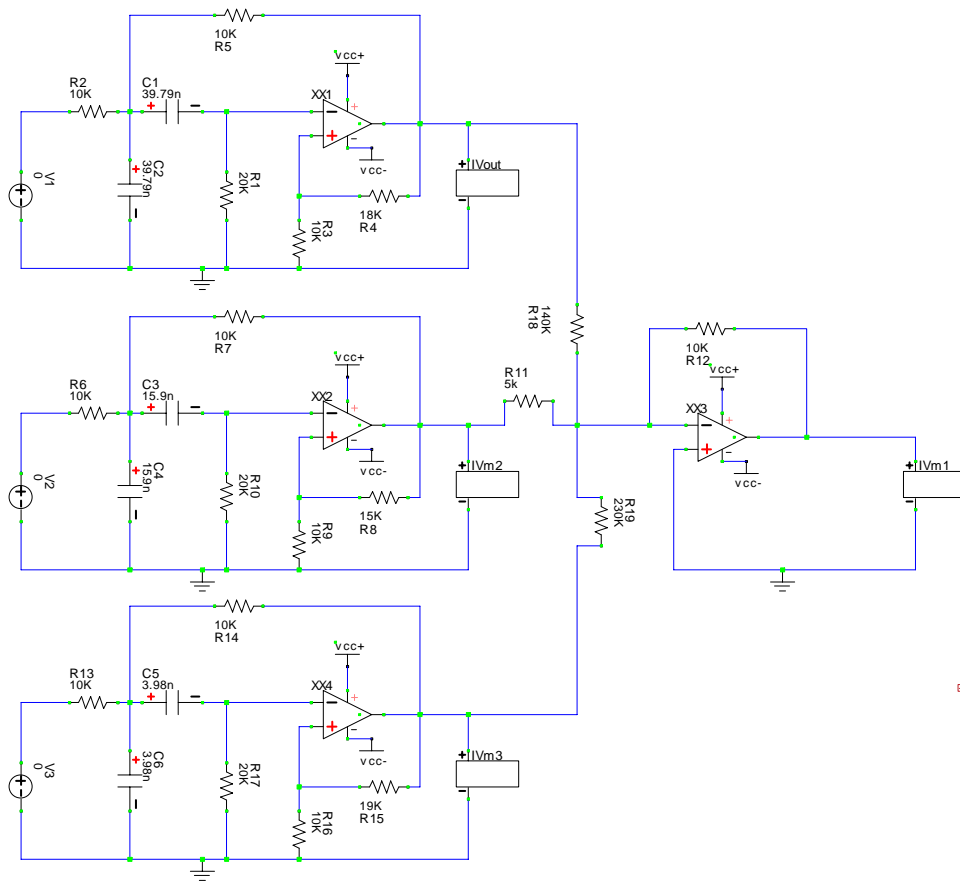BPF3: $R = 10 \text{ K}$, $C = 3.98 \text{ nF}$, $A = 3 - 1/Q = 2.9$, $A_v = 29$. Therefore, Σ -amp needs gain $1/29$



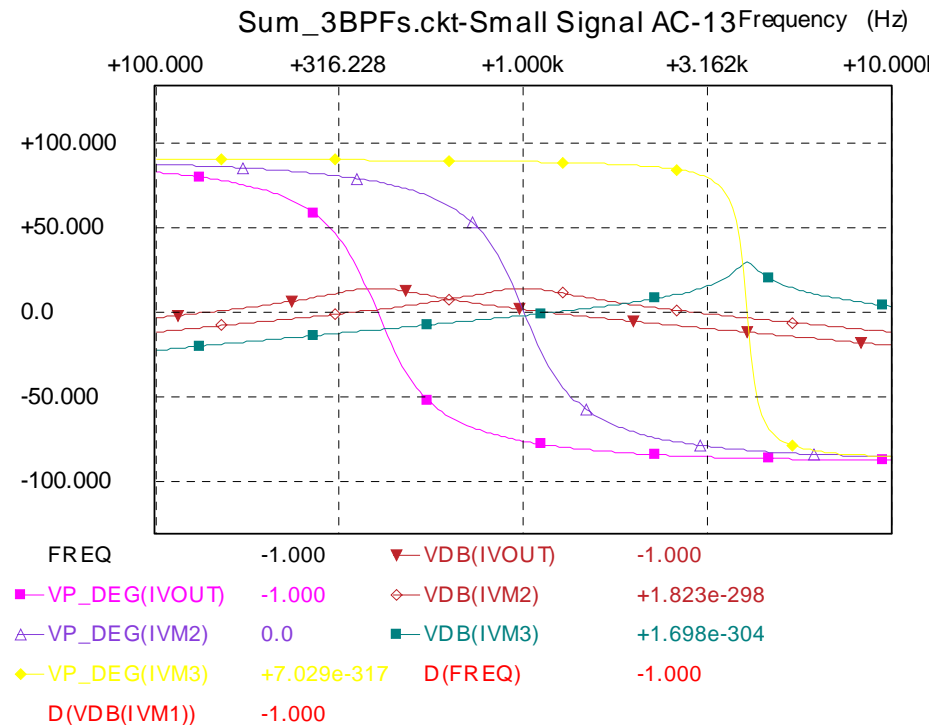Observe the phase of the Transfer functions:



Phase = 0 at resonant frequency. It is positive for $f < f_o$ (inductive) and negative for $f > f_o$ (capacitive).

The total complex signal is summed, not just the amplitudes. With phase reversal, there can be cancellation when summing in ranges of frequencies between resonances.