

MATCHING NETWORKS

- Matching networks provide a transformation of impedance to a desired value to maximize the power dissipated by a load. For example, the figure below illustrates the matching networks for a transistor amplifier. The matching networks ensure that the proper impedance is seen by the amplifier. One such matching method may be a conjugate match of the impedance.
- We will discuss many useful types of matching networks in class, including:
 - L-section matching
 - Quarter wave transformers
 - Single stub tuners


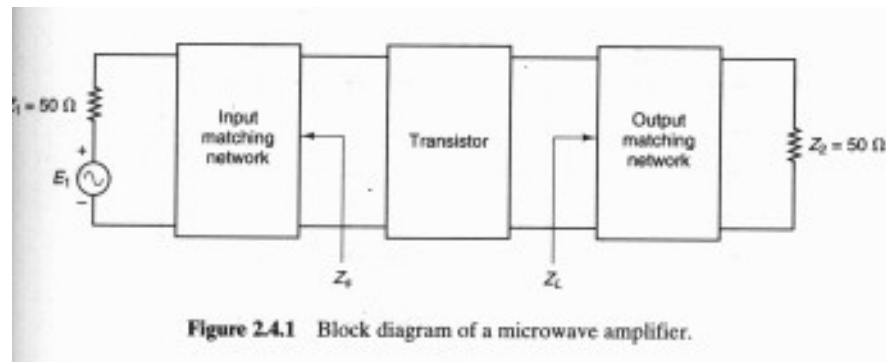


Figure 2.4.1 Block diagram of a microwave amplifier.

L-Section Matching Networks

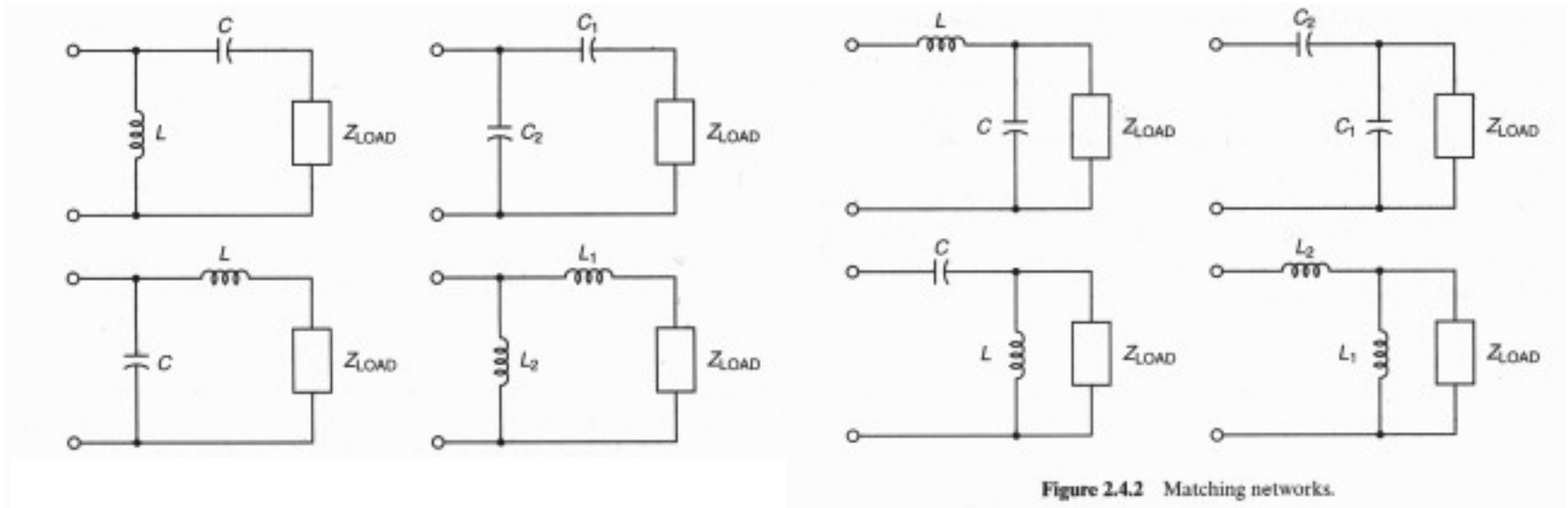- L-sections utilize purely reactive components such that no power is dissipated in the matching network
- Smith Charts are an extremely useful manner by which to design L-section matching networks



- L-section design is best performed on an Admittance/Impedance Smith chart.
- Adding series reactive loads will modify the impedance by adding negative reactance (series C), or positive reactance (series L)
- Adding shunt reactive loads will modify the admittance by adding negative susceptance (shunt C), or positive susceptance (shunt L).
- Note that a solution for a given L-section is not guaranteed. The Smith chart provides visual insight into the feasibility of design.

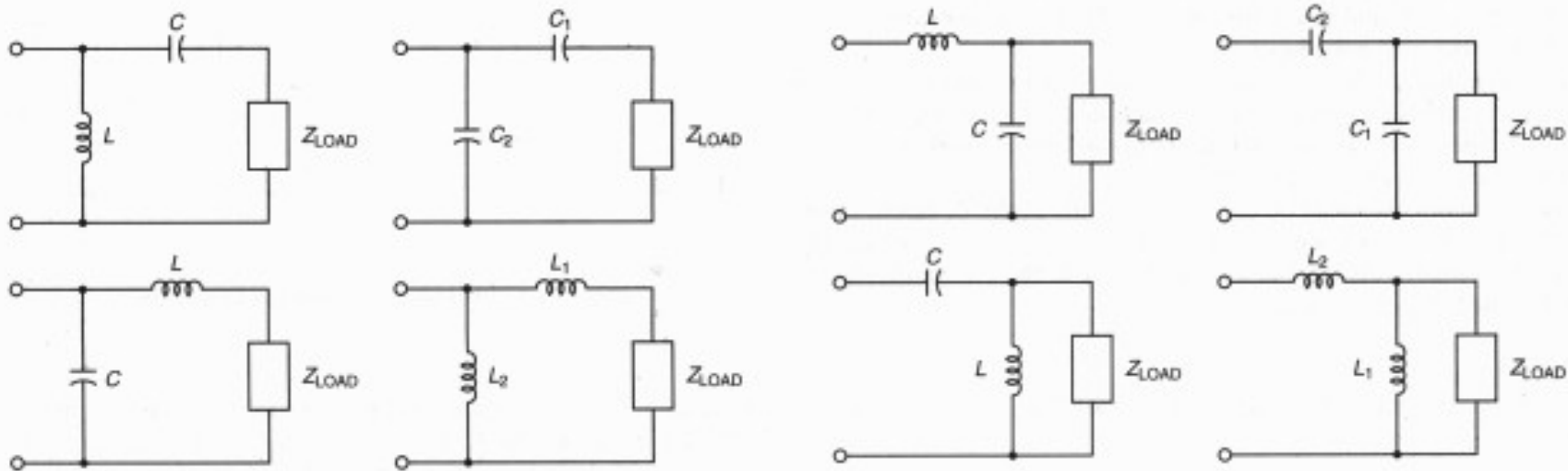


Figure 2.4.2 Matching networks.

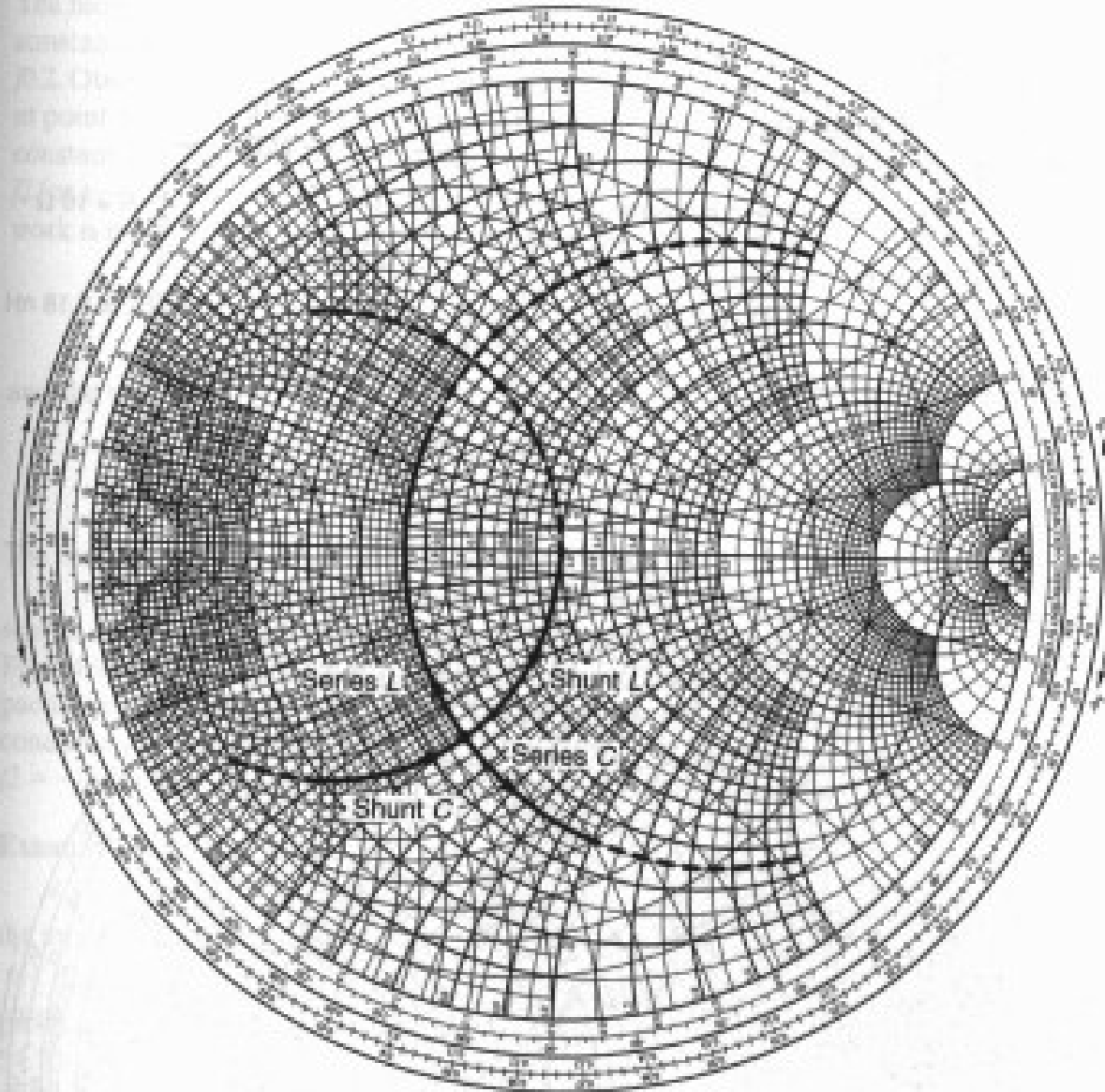


Figure 2.4.7 Effect of adding series and shunt elements in the *ZY* Smith chart.

- Example: A load $Z_L = 10 + j 10 \Omega$ is to be matched to a 50Ω line. Design L-section matching networks at 500 MHz using:
 - a) a series L, shunt C
 - b) a series C, shunt L

Solution:

- a) Given the normalized load: $0.2 + j 0.2$, move along a constant-resistance circle until the unit conductance circle is intersected. This adds $j 0.2$ normalized reactance. The normalized admittance at this point is $1 - j 2$. Thus, the normalized capacitor admittance must be $j 2$. This brings us to the origin.

Finally, the values for L and C are computed at 500 MHz:

$$L = \frac{0.2 \cdot 50}{2\pi(500 \times 10^6)} = 3.18 \text{ nH}$$


$$C = \frac{2}{50} \cdot \frac{1}{2\pi(500 \times 10^6)} = 12.74 \text{ pF}$$

- b) For the series capacitor, we move along the constant resistance circle in the opposite direction until the unit conductance circle is intersected. Thus, the normalized impedance of the capacitor is $-j 0.6$. The normalized admittance at this point is $1 + j 2$. Thus, the normalized admittance of the inductor must be $-j 2$. Thus, at 500 MHz:


$$C = \frac{1}{0.6 \cdot 50} \cdot \frac{1}{2\pi(500 \times 10^6)} = 10.6 \text{ pF} \quad L = \frac{50}{2} \cdot \frac{1}{2\pi(500 \times 10^6)} = 7.95 \text{ nH}$$

Analytical Solution for the L-Matching Network

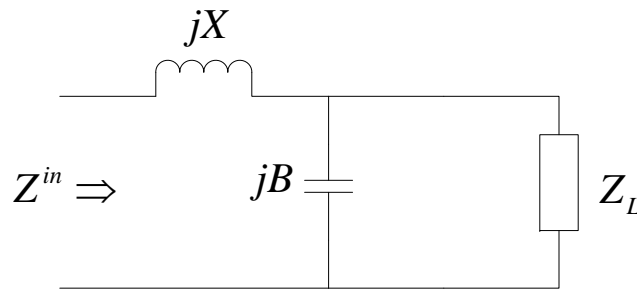- A simple matching network can be achieved with only 2 reactive elements
 - ➡ Transforms both the real and the imaginary part of the input impedance
- A common configuration of the 2 reactive elements is referred to as the L-section matching network (or “el-section”)
 - ➡ Two types:



Network #1

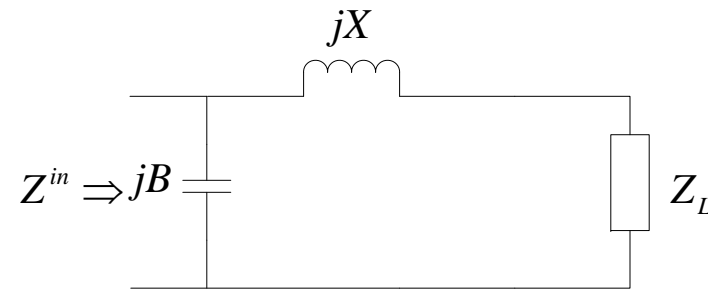

Network #2

- where, $Z_L = R_L + jX_L$

- ➡ Consider network #1:

$$Z^{in} = jX + \frac{1}{jB + \frac{1}{R_L + jX_L}} = jX + \frac{R_L + jX_L}{1 + jBR_L - BX_L}$$

- We desire that $Z^{in} = R_s$. Therefore, we can write the equation:

$$R_s = jX + \frac{R_L + jX_L}{1 + jBR_L - BX_L}$$

- We essentially have two degrees of freedom to solve for: B and X
 - Multiply both sides by the denominator:

$$(R_s + jBR_L R_s - BX_L R_s) = (jX - XBR_L - jXBX_L) + R_L + jX_L$$

- Equate the real and imaginary terms:

$$\text{Real: } B(XR_L - X_L)R_s = R_L - R_s$$

$$\text{Imag: } X(1 - BX_L) = BR_s R_L - X_L$$

- From the imaginary term, find X as a function of B :

$$X = \frac{1}{B} + \frac{X_L R_s}{R_L} - \frac{R_s}{BR_L}$$

- Plug this into the real. Then, solving for B :

$$B = \frac{X_L \pm \sqrt{\frac{R_L}{R_s}} \sqrt{R_L^2 + X_L^2 - R_s R_L}}{R_L^2 + X_L^2}$$

- We can solve for B , and then calculate X from B .

➡ Note, that there are 2 solutions available

- Choose the design that makes sense physically, and is easiest to construct
- From Network #1:

$$B = \frac{X_L \pm \sqrt{\frac{R_L}{R_s} \sqrt{R_L^2 + X_L^2 - R_s R_L}}}{R_L^2 + X_L^2}$$

- Note that in the radical term, the argument can be negative. Typically, Network #1 is only used in the case when $R_L > R_s$.
 - In this case, the argument will always be positive.
- Network #2 is used when $R_L < R_s$
- ➡ Following the same procedure of equating $Z^{in} = R_s$ for Network #2, we derive:


$$X = \pm \sqrt{R_L (R_s - R_L)} - X_L$$

$$B = \pm \frac{\sqrt{(R_s - R_L) / R_L}}{R_s}$$

The Quarter Wave Transformer

- The quarter wave transformer is another useful narrow band matching technique that allows the use of a quarter-wavelength of transmission line with controllable impedance connected to a real load
- Useful for waveguides for which one can control the dimensions and hence the characteristic line impedance (printed waveguides) when fabricating the network
- Useful Theorem:

$$Z(x \pm \lambda / 4) Z(x) = Z_o^2$$

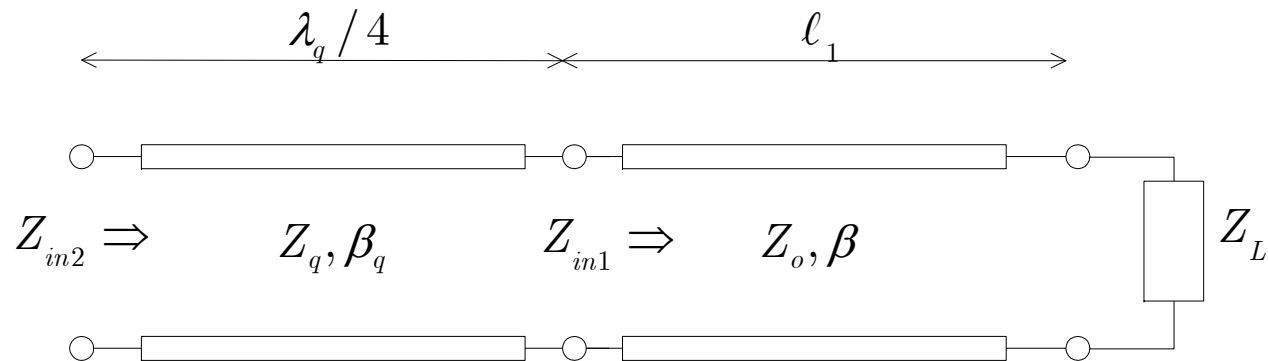

Methodology

- Given a complex load Z_L , choose ℓ_1 such that Z_{in1} is purely real, i.e., $Z_{in1} = R$
- Choose Z_q such that $Z_{in2} = Z_0$. Thus,

$$Z_o R = Z_q^2 \Rightarrow Z_q = \sqrt{Z_o R}$$

- Note that in practice, one needs to design both Z_q and ℓ_q such that $Z_q = \sqrt{Z_o R}$ and $\ell_q = \lambda_q / 4$

Example

Design a QWT to match a $100+j50$ ohm load to a 50 ohm transmission line. To design the QWT, move along the SWR circle to the nearest real axis crossing (Max or Min?).

$$\text{Determine } \Gamma_L = 0.447e^{j0.464}$$

Recall:

$$d_{\max} = \frac{\lambda}{2} \left(\frac{\phi}{2\pi} \right) = \frac{\lambda}{2} \left(\frac{0.464}{2\pi} \right) = 0.037\lambda \quad (\text{for } n = 0)$$

$$Z_{in} = Z_o \frac{Z_L + jZ_o \tan(\beta\ell)}{Z_o + jZ_L \tan(\beta\ell)} = 130.9 \Omega$$

Finally,

$$Z_q = \sqrt{Z_{in} Z_o} = 80.9 \Omega$$

Check:

$$Z_{inq} = Z_q \frac{Z_{in1} + jZ_q \tan(\pi)}{Z_q + jZ_{in1} \tan(\pi)} = 50 \Omega$$

General Design Rule

- Given a complex load Z_L , choose ℓ_1 such that Z_{in1} is purely real, i.e., $Z_{in1} = R$
- If $R < Z_o$ (typically, if $\text{Im}(Z_L) < 0$), then

$$d_{\min} = \frac{\lambda}{2} \left(\frac{1}{2} + \frac{\phi}{2\pi} \right) = \text{(for } n = 0)$$

$$Z_{q_{\min}} = \sqrt{Z_o Z_{in}} = \sqrt{Z_o^2 \left(\frac{1 - |\Gamma_L|}{1 + |\Gamma_L|} \right)}$$

- If $R > Z_o$ (typically, if $\text{Im}(Z_L) > 0$), then

$$d_{\max} = \frac{\lambda}{2} \left(\frac{\phi}{2\pi} \right) = \text{(for } n = 0)$$

$$Z_{q_{\min}} = \sqrt{Z_o Z_{in}} = \sqrt{Z_o^2 \left(\frac{1 + |\Gamma_L|}{1 - |\Gamma_L|} \right)}$$

Bandwidth

- The QWT is only truly matched at the resonant frequency. However, one can determine a frequency bandwidth over which the QWT yields a reflection coefficient below a desirable threshold.
- Assume, $Z_L = R$. Then, then input impedance to the QWT is:

$$Z_{in} = Z_q \frac{R + jZ_q \tan(\beta_q \ell_q)}{Z_q + jR \tan(\beta_q \ell_q)} = Z_q \frac{R + jZ_q t}{Z_q + jR t}$$

- This results in the reflection coefficient:

$$\Gamma = \frac{Z_{in} - Z_o}{Z_{in} + Z_o} = \frac{Z_q (R - Z_o) + jt (Z_q^2 - Z_o R)}{Z_q (R + Z_o) + jt (Z_q^2 + Z_o R)}$$

- Since, $Z_q^2 = Z_o R$, this reduces to:

$$\Gamma = \frac{(R - Z_o)}{(R + Z_o) + j2t\sqrt{Z_o R}}$$

- It can be shown that:

$$|\Gamma| = \frac{1}{\sqrt{1 + \left[\frac{4Z_o R}{(R - Z_o)^2} \right] \sec^2 \theta}}, \text{ where } \theta = \beta_q \ell_q$$

- Define a maximum allowable reflection coefficient Γ_m . Then, let $\theta_m = \theta$ for which $|\Gamma| = \Gamma_m$.
Namely,

$$\theta_m = \cos^{-1} \left\{ \frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_o R}}{|R - Z_o|} \right\}$$


- Finally, the bandwidth is defined as:

$$\Delta\theta = 2 \left(\frac{\pi}{2} - \theta_m \right)$$

- Since $\theta = \beta\ell = \frac{2\pi f}{c} \ell$, and $\theta_m = \beta_m \ell = \frac{2\pi f_m}{c} \ell$

$$\Rightarrow \frac{\Delta f}{f_o} = \frac{2(f_o - f_m)}{f_o} = 2 - 2 \frac{f_m}{f_o} = 2 - 4 \frac{\theta_m}{\pi}$$


$|\Gamma|$ vs. f / f_o for various values of Z_L / Z_o

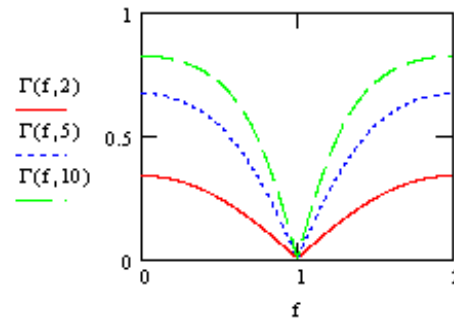

Fractional Bandwidth versus Z_L / Z_o given Γ_m

$$\theta_m(\Gamma_m, z_l) := \arccos\left(\frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \cdot \frac{2\sqrt{z_l}}{|z_l - 1|}\right)$$
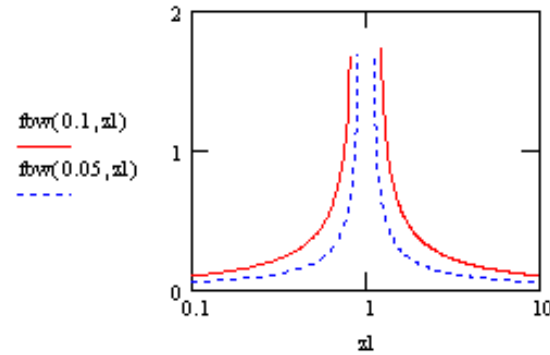
$$\text{fbw}(\Gamma_m, z_l) := 2 - 4 \cdot \frac{\theta_m(\Gamma_m, z_l)}{\pi}$$



Single Stub Tuning

- An alternate method of matching is to reactively load the line with a shunt load rendering the net line impedance equal to the characteristic impedance.
- A single stub tuner is best illustrated on a smith chart using the following procedure:
 - ❑ Plot the normalized load impedance on the smith chart
 - ❑ Draw the SWR circle and determine the line admittance
 - ❑ Move toward the load until you cross the $r = 1$ circle
 - ❑ At this point, the line admittance = $1 + jb$
 - ❑ Add in a shunt load with input admittance = $-jb$
 - ❑ Note that a purely imaginary input admittance can be achieved by a short or open circuited line with the proper line length
 - ❑ At this point, the normalized admittance = 1. Thus, the line is matched to the load
- As with the QWT, the geometry of the line is simply modified to manipulate the line impedance and reach a matched condition. No lumped loads are needed.
- In essence, the stub line cancels out the reactive power stored in the standing wave between the load and the line. Thus, all power is delivered to the load.

Analytical Solution

- A Smith chart will solve the SST approximately. Simple analytic solutions can also be derived.
- Assume a load impedance (admittance):

$$Z_L = R_L + jX_L; Y_L = 1/Z_L$$

- A distance d from the load, the line admittance is given as:

$$Y = G + jB = \frac{1}{Z_o} \frac{Z_o + j(R_L + jX_L)t}{(R_L + jX_L) + jZ_o t}$$

where $t = \tan \beta d$

- Evaluating the real and imaginary parts:

$$G = \frac{R_L(1+t^2)}{R_L^2 + (X_L + Z_o t)^2}, \quad B = \frac{R_L^2 t - (Z_o - X_L t)(X_L + Z_o t)}{Z_o [R_L^2 + (X_L + Z_o t)^2]}$$

- Solving for d such that $G/Y_o = 1$

$$t = \begin{cases} \frac{X_L \pm \sqrt{R_L [(Z_o - R_L)^2 + X_L^2]} / Z_o}{R_L - Z_o}, & \text{if } R_L \neq Z_o \\ -\frac{X_L}{2Z_o}, & \text{if } R_L = Z_o \end{cases}$$

- Finally, there are two solutions for d :

$$\frac{d}{\lambda} = \begin{cases} \frac{1}{2\pi} \tan^{-1} t, & (t \geq 0) \\ \frac{1}{2\pi} (\pi + \tan^{-1} t), & (t < 0) \end{cases}$$

- At this point, the normalized line admittance = $1 + jB / Y_o$
- Thus, we need to add in a shunt stub tuner to cancel out the reactive part.
- Assume that the stub is terminated by a short circuit. Then:

$$Z_{in_{sc}} = jZ_o \tan(\beta \ell_{sc}) \Rightarrow Y_{in_{sc}} = -j \frac{1}{Z_o} \cot(\beta \ell_{sc})$$

- It is desired that: $Y_{in_{sc}} = -jB$

- Therefore:

$$-jB = -j \frac{1}{Z_o} \cot(\beta \ell_{sc}) \Rightarrow \frac{\ell_{sc}}{\lambda} = \frac{1}{2\pi} \tan^{-1} \left(\frac{1}{Z_o B} \right)$$

- Similarly, for an open circuit stub:

$$Z_{in_{oc}} = -jZ_o \cot(\beta \ell_{oc}) \Rightarrow Y_{in_{oc}} = j \frac{1}{Z_o} \tan(\beta \ell_{oc})$$

- Hence

$$\frac{\ell_{oc}}{\lambda} = -\frac{1}{2\pi} \tan^{-1} (BZ_o)$$

Example:

Design a QWT and an open-circuit single stub tuner to match a parallel resistor capacitor load to a $50\ \Omega$ TEM transmission line ($\epsilon_r = 1$) at 1 GHz, given $R = 100\ \Omega$, $C = 1\ \text{pF}$.

Solution (QWT):

$$f := 1 \cdot 10^9 \quad c := 3 \cdot 10^8 \quad Z_0 := 50 \quad R := 100 \quad C := 1 \cdot 10^{-12}$$

$$\lambda := \frac{c}{f} \quad \lambda = 0.3 \quad X_c := \frac{1}{j \cdot 2 \cdot \pi \cdot f \cdot C} \quad X_c = -159.155i$$

$$Z_L := \frac{R \cdot X_c}{R + X_c} \quad R_L := \text{Re}(Z_L) \quad X_L := \text{Im}(Z_L) \quad R_L = 71.696 \quad X_L = -45.048$$

Quarter Wave Transformer Design:

$$\Gamma := \frac{Z_L - Z_0}{Z_L + Z_0} \quad \Gamma = 0.277 - 0.268i$$

Note that due to the negative reactance, we first expect a Voltage Minimum:

$$d_{\min} := 0.5 \cdot \left[\frac{1}{2} + \frac{(\arg(\Gamma))}{2 \cdot \pi} \right] \quad d_{\min} = 0.189$$

$$Z_{\text{in}} := Z_0 \cdot \frac{(Z_L + j \cdot Z_0 \cdot \tan(2 \cdot \pi \cdot d_{\min}))}{Z_0 + j \cdot Z_L \cdot \tan(2 \cdot \pi \cdot d_{\min})} \quad Z_{\text{in}} = 22.186$$

$$Z_q := \sqrt{Z_{\text{in}} \cdot Z_0}$$

$$Z_q = 33.306 \ \Omega \quad d_{\min} \cdot \lambda = 0.057 \ \text{m}$$

If instead, we move to the first voltage maximum:

$$d_{\max} := 0.5 \cdot \left[1 + \frac{(\arg(\Gamma))}{2 \cdot \pi} \right] \quad d_{\max} = 0.439$$

$$Z_{\text{in}} := Z_0 \cdot \frac{(Z_L + j \cdot Z_0 \cdot \tan(2 \cdot \pi \cdot d_{\max}))}{Z_0 + j \cdot Z_L \cdot \tan(2 \cdot \pi \cdot d_{\max})} \quad Z_{\text{in}} = 112.684$$

$$Z_q := \sqrt{Z_{\text{in}} \cdot Z_0}$$

$$Z_q = 75.061 \ \Omega \quad d_{\max} \cdot \lambda = 0.132 \ \text{m}$$

Solution (SST):

$$f := 1 \cdot 10^9 \quad c := 3 \cdot 10^8 \quad Z_0 := 50 \quad R := 100 \quad C := 1 \cdot 10^{-12}$$

$$\lambda := \frac{c}{f} \quad \lambda = 0.3 \quad X_c := \frac{1}{j \cdot 2 \cdot \pi \cdot f \cdot C} \quad X_c = -159.155i$$

$$Z_L := \frac{R \cdot X_c}{R + X_c} \quad R_L := \text{Re}(Z_L) \quad X_L := \text{Im}(Z_L) \quad R_L = 71.696 \quad X_L = -45.048$$

Single Stub Tuner Design (RL ≠ Zo):

Solution 1:

$$t_1 := \frac{X_L + \sqrt{R_L \cdot \left[(Z_0 - R_L)^2 + X_L^2 \right]}}{R_L - Z_0} \quad t_1 = 0.683$$

$$d_1 := \frac{1}{2 \cdot \pi} \cdot \text{atan}(t_1) \cdot \lambda \quad d_1 = 0.029 \text{ m}$$

$$B_1 := \frac{R_L^2 \cdot t_1 - (Z_0 - X_L \cdot t_1) \cdot (X_L + Z_0 \cdot t_1)}{Z_0 \cdot [R_L^2 + (X_L + Z_0 \cdot t_1)^2]} \quad B_1 = 0.017$$

$$l_{s1} := \frac{1}{2 \cdot \pi} \cdot \text{atan}\left(\frac{1}{Z_0 \cdot B_1}\right) \cdot \lambda \quad l_{s1} = 0.042 \text{ m}$$

+

Solution 2:

$$t_2 := \frac{X_L - \sqrt{R_L \cdot \left[(Z_0 - R_L)^2 + X_L^2 \right]}}{R_L - Z_0} \quad t_2 = -4.836$$

$$d_2 := \frac{1}{2 \cdot \pi} (\pi + \text{atan}(t_2)) \cdot \lambda \quad d_2 = 0.085 \text{ m}$$

$$B_2 := \frac{R_L^2 \cdot t_2 - (Z_0 - X_L \cdot t_2) \cdot (X_L + Z_0 \cdot t_2)}{Z_0 \cdot [R_L^2 + (X_L + Z_0 \cdot t_2)^2]} \quad B_2 = -0.017$$

$$l_{s2} := \frac{1}{2 \cdot \pi} \cdot \text{atan}\left(\frac{1}{Z_0 \cdot B_2}\right) \cdot \lambda \quad l_{s2} = -0.042 \text{ m}$$

Note that since l_{s2} is negative, we need to add $\lambda/2$ to get a positive result:

$$l_{s2} := l_{s2} + \frac{\lambda}{2} \quad l_{s2} = 0.108 \text{ m}$$

ee523_prj QWT (Schematic):1

File Edit Select View Draw Component Options Tools Layout Simulate Window Help

Lumped-Components

Basic linear frequency domain S-parameter template.
 Steps: 1. Connect circuit between ports 1 and 2.
 2. Set frequency range of simulation under S PARAMETERS block.
 3. Click simulation icon to run.
 4. Open Window > Open Plot Display

S. PARAMETERS

S:Port=1
 SP1
 SStart=0.5 GHz
 SStop=2 GHz
 SStep=0.05 GHz

Copy: Enter reference location 0 items wire -6.250, -2.000 -6.500, 0.000

$|\Gamma|$ in dB

