

General 2nd order filter expression

$$H(s) = \frac{n_2 s^2 + n_1 s + n_0}{s^2 + \left(\frac{\omega_0}{Q}\right) s + \omega_0^2} \quad (1)$$

$$H(s) = \underbrace{\frac{n_2 s^2}{s^2 + \left(\frac{\omega_0}{Q}\right) s + \omega_0^2}}_{\text{HPF}} + \underbrace{\frac{n_1 s}{s^2 + \left(\frac{\omega_0}{Q}\right) s + \omega_0^2}}_{\text{BPF}} + \underbrace{\frac{n_0}{s^2 + \left(\frac{\omega_0}{Q}\right) s + \omega_0^2}}_{\text{LPF}}$$

n_0, n_1 and n_2 determine zeros in Eq.(1)

and determine filter type.




The denominator: $s^2 + \left(\frac{\omega_0}{Q}\right) s + \omega_0^2$ determines poles

② - 09

$$p_1, p_2 = -\frac{\omega_0}{2Q} \pm \sqrt{\left(\frac{\omega_0}{2Q}\right)^2 - \omega_0^2}$$

for $Q > 0.5$ $p_1, p_2 = -\frac{\omega_0}{2Q} \pm j \sqrt{\omega_0^2 - \left(\frac{\omega_0}{2Q}\right)^2}$

Equivalent LPF

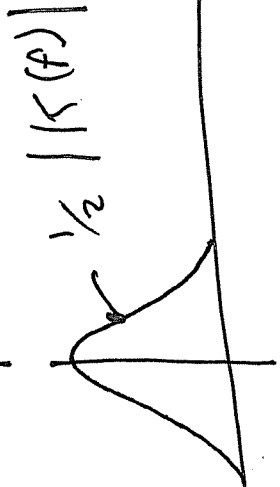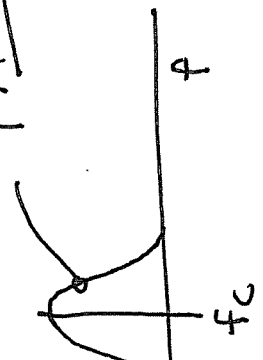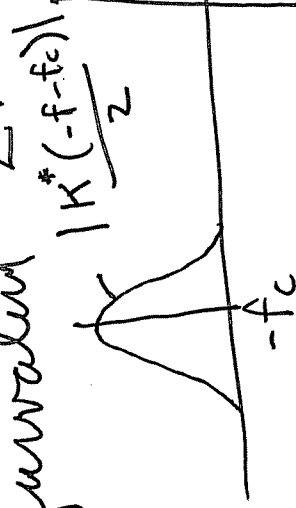

For example: Given a BPF $H(s) = \frac{n_1 s}{s^2 + \left(\frac{\omega_0}{Q}\right)s + \omega_0^2}$

3-09

$$\text{so } H(s) = \frac{n, s}{(s-p_1)(s-p_2)} = \frac{A}{(s-p_1)} + \frac{B}{(s-p_2)}$$

Use partial fraction expansion (PFE)

Solve for A by mult. by $(s-p_1)$

$$\frac{n, s}{s-p_2} = A + \frac{B(s-p_1)}{(s-p_2)}$$

$$\text{let } s = p_1 \text{ so } A = \frac{n, p_1}{p_1 - p_2}, \text{ likewise } B = \frac{n, p_2}{p_2 - p_1}$$

let $s = j\omega$


$$H(\omega) = \frac{A}{j(\omega - \omega_0) + C} + \frac{B}{j(\omega + \omega_0) + C}$$

$\underbrace{\hspace{10em}}_{\frac{1}{2} K(\omega - \omega_0)} \quad \underbrace{\hspace{10em}}_{\frac{1}{2} K(\omega + \omega_0)}$

$$H_{LP}(\omega) = \frac{1}{2} K(\omega) = \frac{A}{j\omega + C}$$


Active Filter Designs (ie. contain an ideal op-amp) 4-09

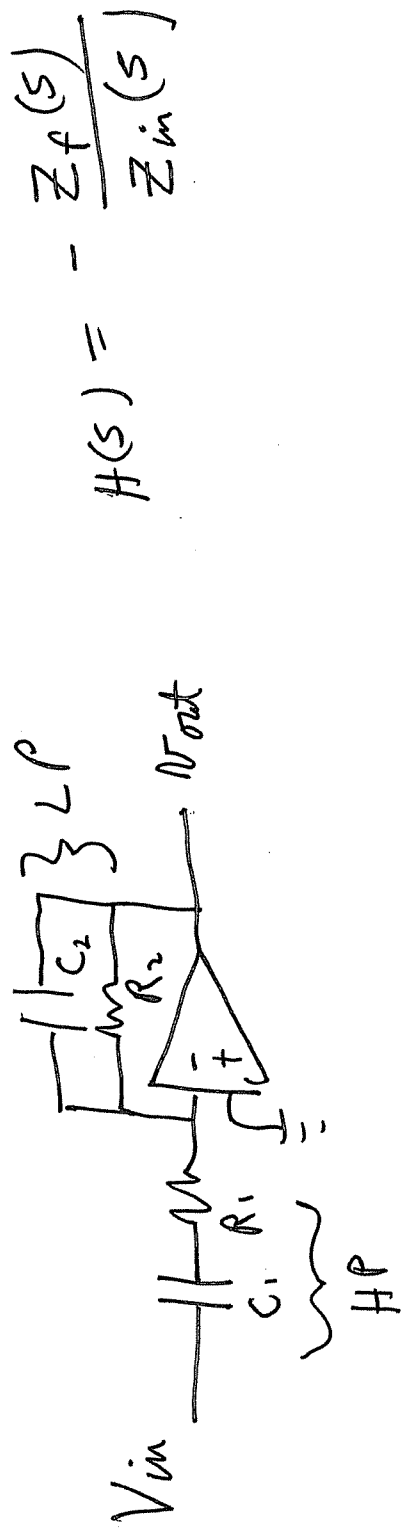Broad Band (no resonance) low Q, inverting




$$H(s) = - \frac{Z_f(s)}{Z_{in}(s)}$$

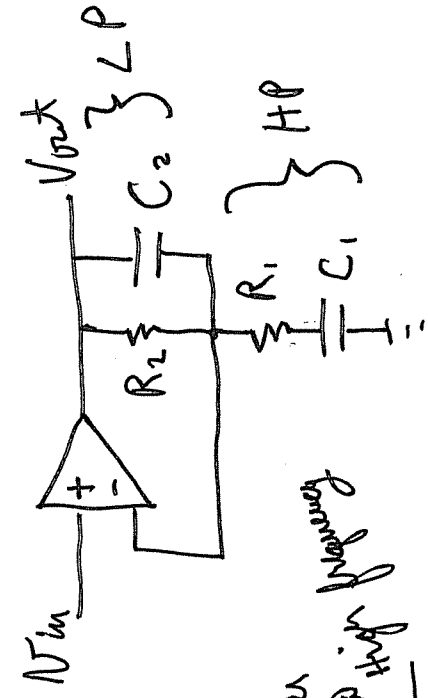
Non-inverting (Technically an all pass) low Q



Note: may not be practical

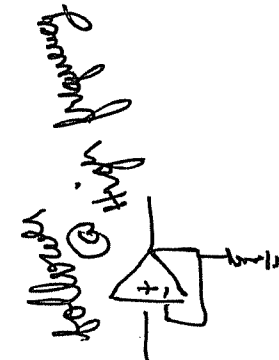


Bandpass (high Q)

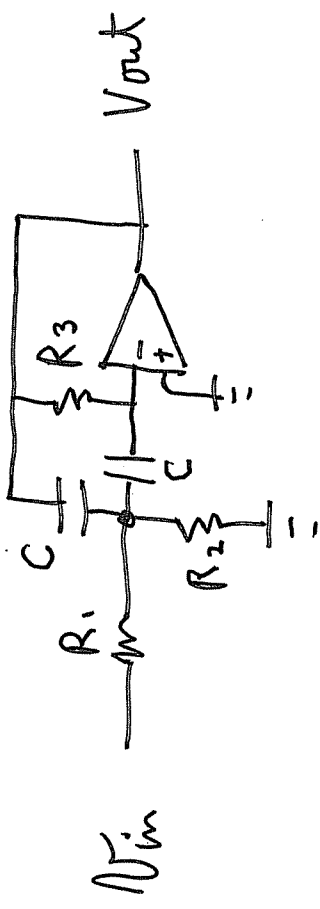


very practical

High Pass (High Q)

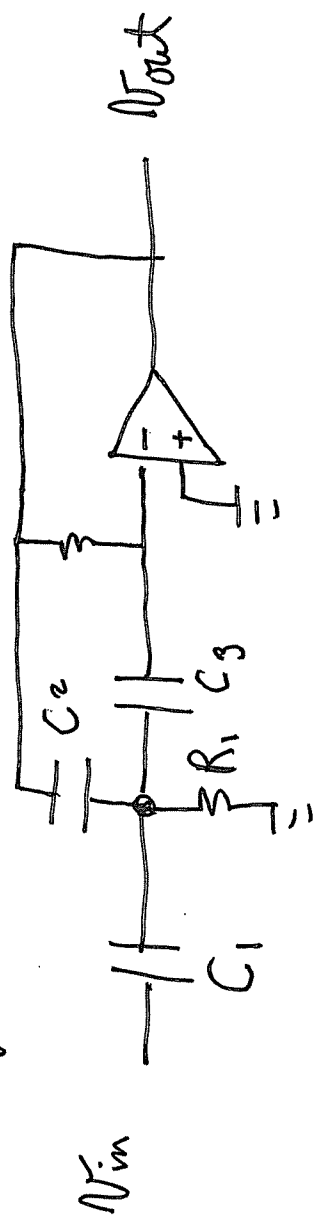

Low Pass (High Q)

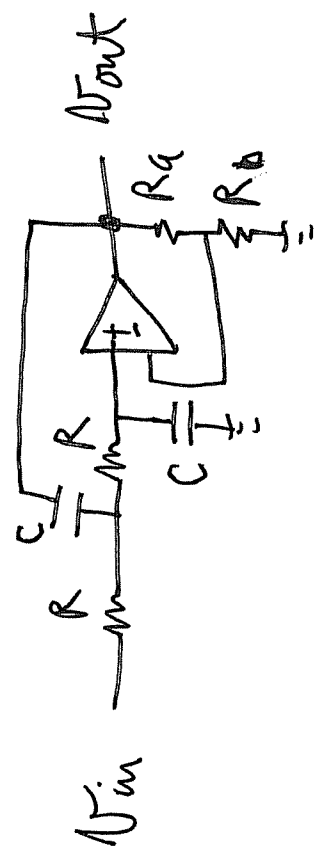


$$H(j\omega) = \frac{K\omega_0^2}{-\omega^2 + j\omega_0(b-K) + \omega_0^2}$$

where $K = \frac{R_a + R_b}{R_b}$

$$\omega_0 = \frac{1}{RC}$$


6-09

All pass Linear Phase Delay

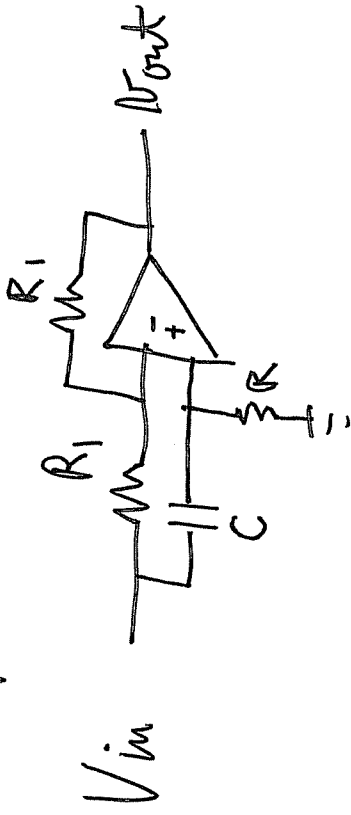

Ex: 1 Consider cascaded 1st order LP filters
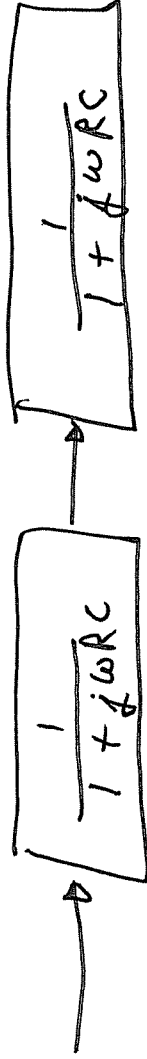
$$H(\omega) = \frac{1}{1 + j2\omega RC - (\omega RC)^2}$$



$$H(\omega) = \frac{-1/RC)^2}{\omega^2 - 2j\omega/RC - 1/RC)^2} = \frac{1/RC)^2}{s^2 + 5/RC/2 + 1/RC)^2} \quad \text{for } s=j\omega$$

7-09

$$H(s) = \frac{\omega_0^2}{s^2 + s\left(\frac{\omega_0}{Q}\right) + \omega_0^2}$$

so $s/RC/2 = s\omega_0/Q$ and $\omega_0^2 = 1/RC^2$

then $Q = 1/2$, $\omega_0 = 1/RC$