

Integrate and Amp

Consider an analog integrator



$$\frac{V_{out}}{V_{in}} = -\frac{Z_f}{Z_i} = -\frac{1/sC}{R_1} = -\frac{1}{sR_1C}$$

Practical integrator or low pass filter




$$H(s) = -\frac{R_2/sC}{R_1 + 1/sC}$$

$$= -\frac{R_2/R_1}{1 + j\omega R_2C}$$


If  $R_2 \gg R_1$  then  $H(\omega) \approx -\frac{1}{j\omega R_2C}$

2-09

# Integrate and Dump

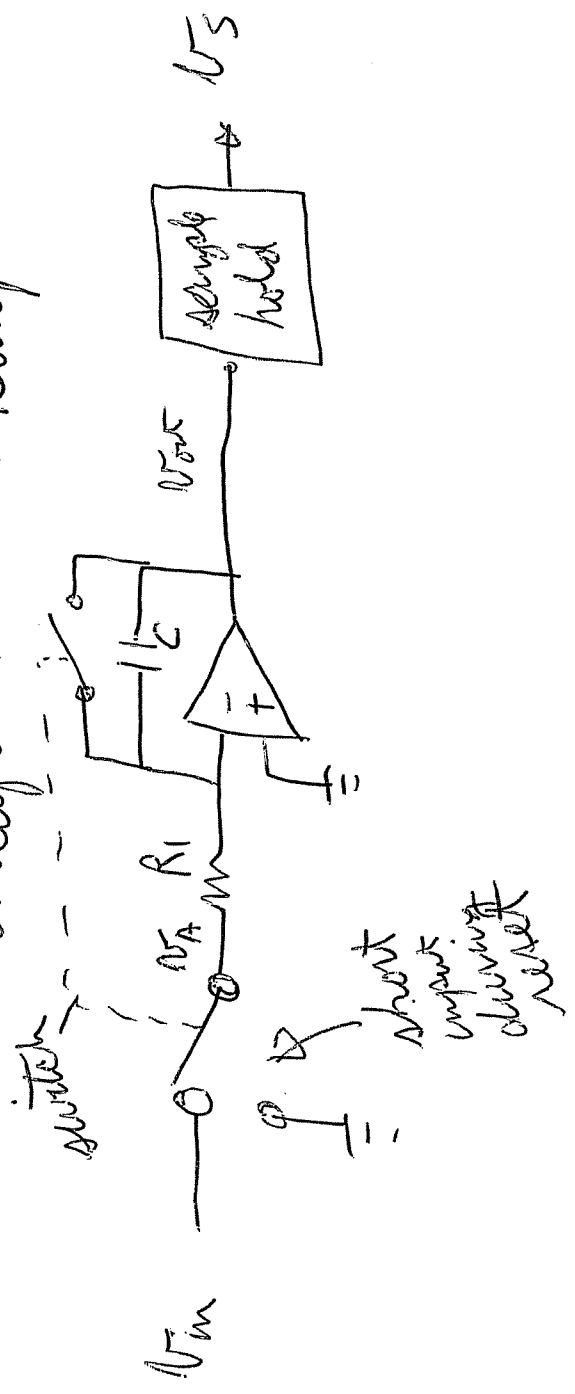

short input circuit reset

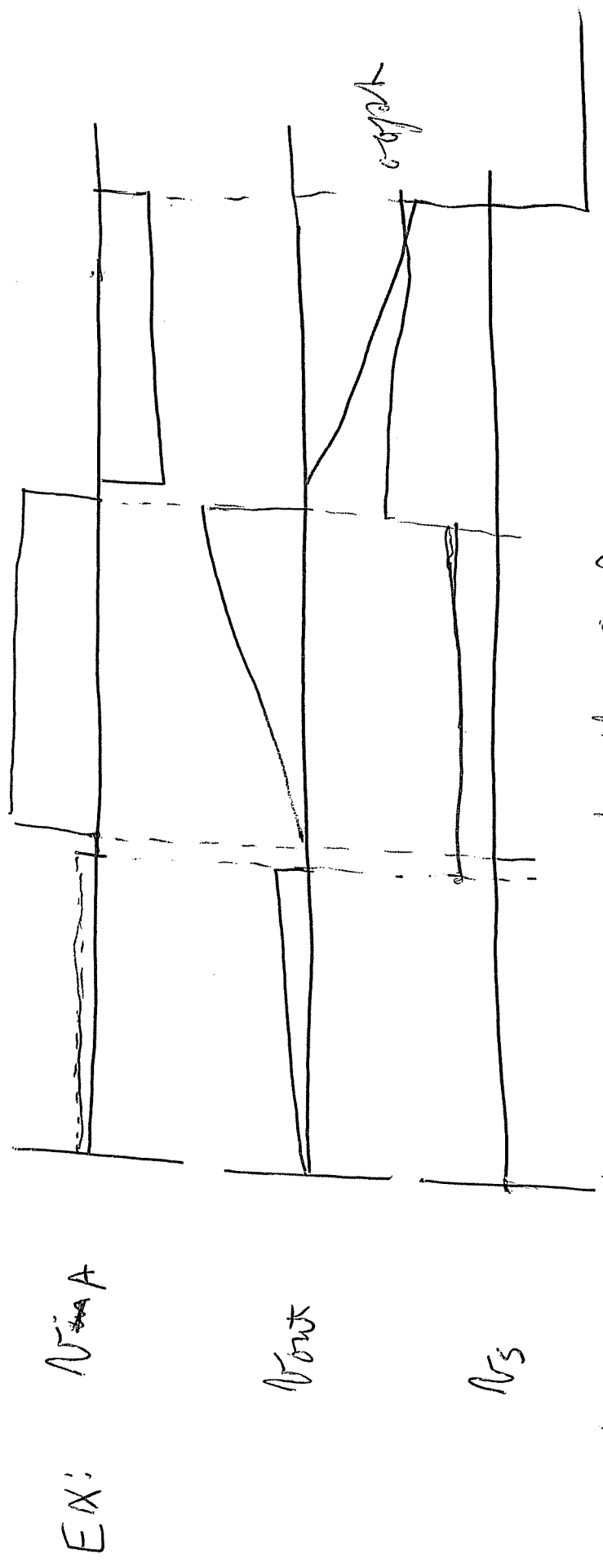

The longer we integrate, the higher the SNR