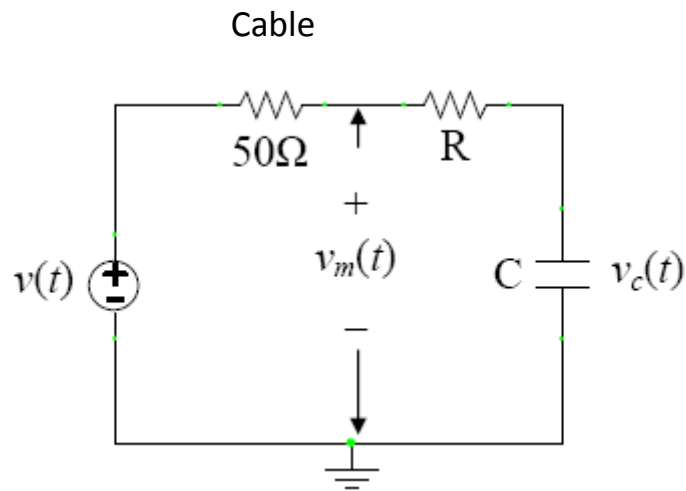


**Example: Cable issue.** Consider the following RC circuit, where a  $50\ \Omega$  -cable is used. The voltage source  $v(t)$  is connected to the RC circuit through the  $50\ \Omega$  -cable. The real voltage applied to RC is  $v_m(t)$ .



We can solve the differential equation to find  $v_c(t) = A \left( 1 - e^{-\frac{t}{\tau}} \right) u(t)$  and

$v_m(t) = A \left( 1 - e^{-\frac{t}{\tau}} + \frac{RC}{\tau} e^{-\frac{t}{\tau}} \right) u(t)$  and  $\tau = (R+50)C$ . Therefore,  $V_m(t)$  is no longer an ideal step function.

How to make  $V_m(t)$  close to an ideal step function?

- (1) qualitatively should  $R$  be large or small?
- (2) If  $R \gg 50\ \Omega$ , what is  $V_m(t)$ ?