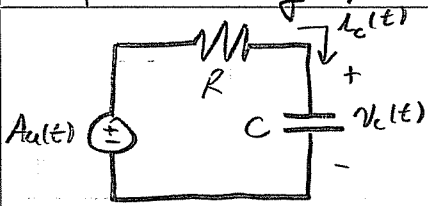


22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



1.



KVL - Time Domain

$$-A u(t) + i_c R + v_c = 0$$

$$i_c = C \frac{dv_c}{dt}$$

$$RC \frac{dv_c}{dt} + v_c = A u(t)$$

$$\frac{dv_c}{dt} + \frac{v_c}{RC} = \frac{A}{RC} u(t)$$

$$e^{t/RC} \left[\frac{dv_c}{dt} + \frac{v_c}{RC} \right] = \frac{A}{RC} e^{t/RC} u(t)$$


$$\frac{d}{dt} \left[e^{t/RC} v_c \right] = \frac{A}{RC} e^{t/RC} u(t)$$

$$e^{t/RC} v_c = \frac{A}{RC} \int_0^t e^{t/RC} dt$$


$$e^{t/RC} v_c = \frac{A}{RC} (RC) \left[e^{t/RC} \right]_0^t$$

$$e^{t/RC} v_c = A (e^{t/RC} - 1)$$

$$v_c(t) = A (1 - e^{-t/RC}) u(t)$$

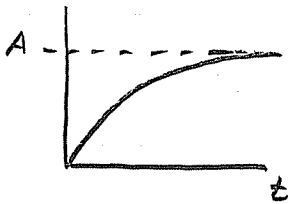

2.


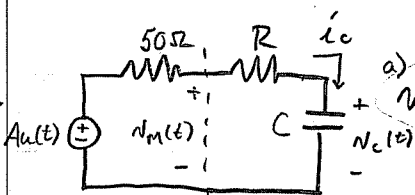


$$v_c(t) = A (1 - e^{-t/(R+50)C}) u(t) \quad \tau = (R+50)C$$

$$b) v_m(t) = R i_c(t) + v_c(t) = RC \frac{dv_c}{dt} + v_c(t)$$

$$v_m(t) = \frac{ARC}{\tau} e^{-t/\tau} + A (1 - e^{-t/\tau})$$
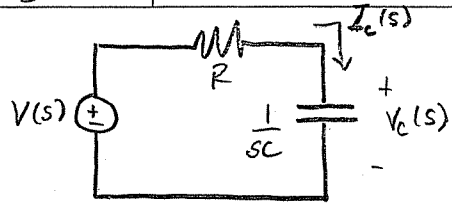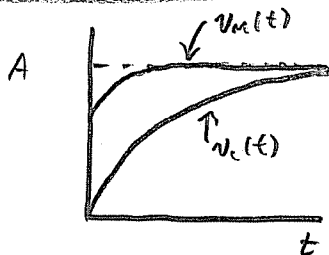
$$v_m(t) = A \left[1 - e^{-t/\tau} + \frac{RC}{\tau} e^{-t/\tau} \right]$$



Voltage Division - s Domain

$$V_c(s) = \frac{V(s) \frac{1}{sC}}{\frac{1}{sC} + R} = \frac{V(s)}{1 + sRC}$$

$$V_c(s) = \mathcal{L}(A u(t)) = \int_{-\infty}^{\infty} A u(t) e^{-st} dt$$

$$V_c(s) = A \int_0^{\infty} e^{-st} dt = -\frac{A}{s} \left[e^{-st} \right]_0^{\infty}$$

$$V_c(s) = \frac{A}{s}$$

$$V_c(s) = \frac{A}{s(1 + sRC)} = \frac{A/RC}{s(\frac{1}{RC} + s)}$$

$$A/RC \left[\frac{1}{s(\frac{1}{RC} + s)} \right] = \frac{A}{RC} \left[\frac{D}{s} + \frac{E}{\frac{1}{RC} + s} \right]$$

$$D = \frac{1}{\frac{1}{RC} + s} \Big|_{s=0} = RC$$

$$E = \frac{1}{s} \Big|_{s=-\frac{1}{RC}} = -RC$$

$$D = RC$$

$$E = -RC$$

$$V_c(s) = \frac{A}{RC} \left(\frac{RC}{s} - \frac{RC}{\frac{1}{RC} + s} \right)$$

$$V_c(s) = \frac{A}{s} - \frac{A}{\frac{1}{RC} + s}$$

$$v_c(t) = A u(t) - A e^{-t/RC} u(t)$$

$$v_c(t) = A (1 - e^{-t/RC}) u(t)$$



$$\frac{dv_c}{dt} = (-A e^{-t/\tau}) \left(-\frac{1}{\tau} \right)$$

$$\frac{dv_c}{dt} = \frac{A}{\tau} e^{-t/\tau}$$


22-141 50 SHEETS
22-142 100 SHEETS
22-143 200 SHEETS
22-144 200 SHEETS
GAMPAD

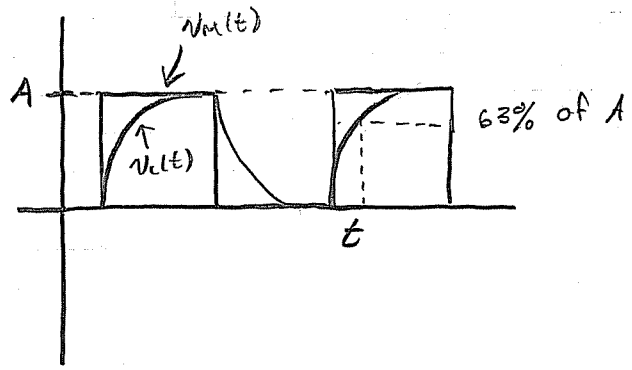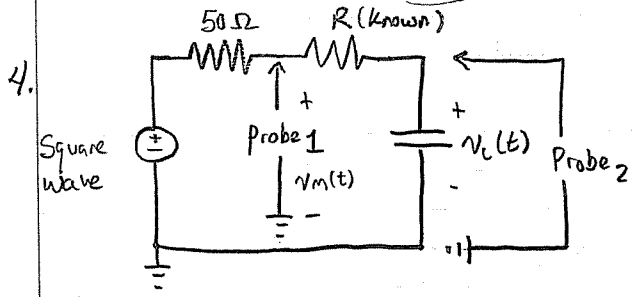3. $V_c(t) = A(1 - e^{-t/RC})u(t)$
 $3.2 = 5(1 - e^{-(10ms)/RC})$
 $.64 = 1 - e^{-5 \times 10^{-5}/C}$
 $.36 = e^{-5 \times 10^{-5}/C}$
 $C \ln(.36) = -5 \times 10^{-5}$
 $C = 4.894 \times 10^{-5} \approx 49 \mu F$

$R = 200 \Omega, A = 5V, V_c(10ms) = 3.2V$



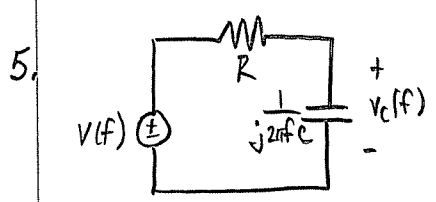- Set square wave input with offset to be positive only
- Set frequency of square wave to allow for capacitor to charge and discharge sufficiently.
- Find using cursors when cap voltage is 63% of square wave max.
- The time from start of the pulse to this time is $RC \rightarrow$ solve for C.




$$V_c(f) = \frac{V(f) \frac{1}{j2\pi fC}}{R + \frac{1}{j2\pi fC}} = \frac{V(f)}{1 + j2\pi fRC}$$

$$H(f) = \frac{1}{1 + j2\pi fRC} = \frac{V_c(f)}{V(f)} = \frac{\text{out}}{\text{in}}$$

$$|H(f)| = \frac{1}{|1 + j2\pi fRC|} = \frac{1}{\sqrt{1^2 + (2\pi fRC)^2}} = \frac{1}{(1 + (2\pi fRC)^2)^{1/2}}$$

$$\angle H(f) = \frac{\angle 1}{\angle 1 + j2\pi fRC} = \angle 1 - \angle 1 + j2\pi fRC$$
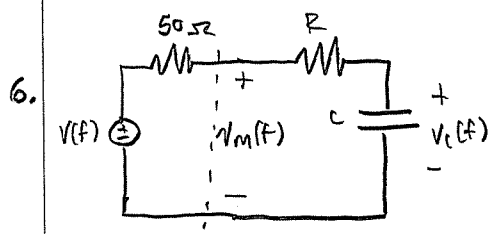
$$\angle H(f) = -\tan^{-1}\left(\frac{2\pi fRC}{1}\right) = -\tan^{-1}(2\pi fRC)$$



If $V_m(f)$ is reference, we have the circuit of #5, and thus the same TF.



$$7. |V_c| = \frac{|V|}{(1 + (2\pi fRC)^2)^{1/2}}$$

$$|V_c|^2 = \frac{|V|^2}{1 + (2\pi fRC)^2}$$

$$1 + (2\pi fRC)^2 = \frac{|V|^2}{|V_c|^2} - 1$$

$$2\pi fRC = \frac{\sqrt{\frac{|V|^2}{|V_c|^2} - 1}}{2\pi fR}$$


$$C = \frac{\sqrt{\frac{|V|^2}{|V_c|^2} - 1}}{2\pi fR} = 5.412 \times 10^{-7} \text{ F} \approx .54 \mu\text{F}$$

$$8. \angle H(f) = -\tan^{-1}(2\pi fRC)$$

$$\tan(\angle H(f)) = C$$

$$C = -\frac{\tan(\angle V_c - \angle V)}{2\pi fR}$$
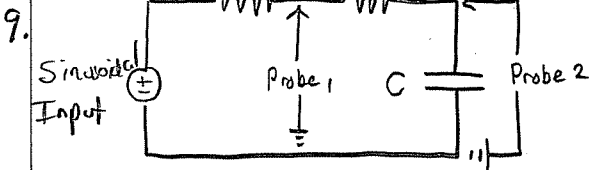
$$C = -\frac{\tan(-45^\circ)}{2\pi f(6k)} = 6.63 \text{ nF}$$



Magnitude

Measure input/output as shown above; the peak/peak measurements can be used in the formula:

$$C = \frac{\sqrt{\left(\frac{V_s(pp)}{V_c(pp)}\right)^2 - 1}}{j2\pi fR}$$

Phase

Run a frequency sweep and find where the phase difference is 45° .

$$\angle H(f) = -\tan^{-1}(2\pi fRC)$$

$$\angle V_s \text{ reference} = 0^\circ$$

$$\angle V_c - \angle V_s = -\tan^{-1}(2\pi fRC)$$

$$-\tan(\angle V_c) = 2\pi fRC$$

$$C = \frac{-\tan(\angle V_c)}{2\pi fR} = -\tan(-45^\circ) = \frac{1}{2\pi fR} = C$$

$$\text{At } 45^\circ, C = \frac{1}{2\pi fR}$$