
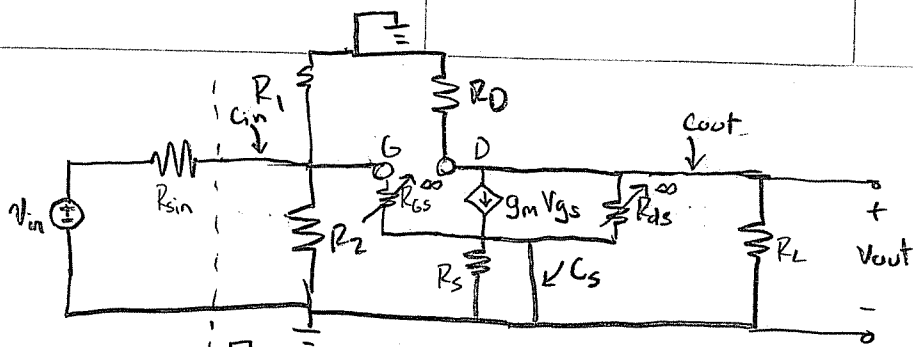


2.

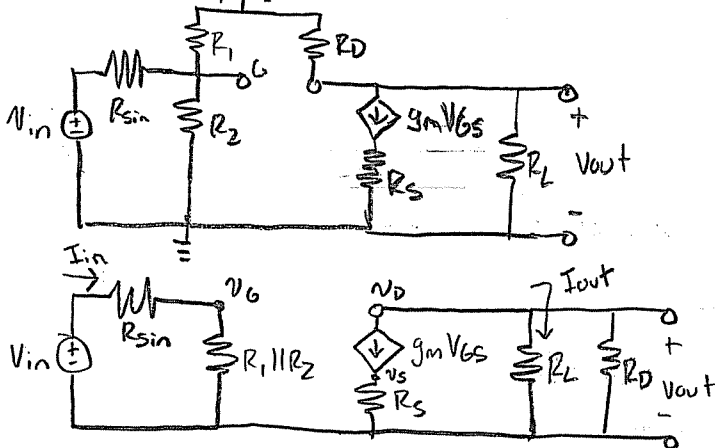

3.



$$V_{out} = -g_m V_{GS} (R_L \parallel R_D)$$

$$V_G = \frac{V_{in} (R_1 \parallel R_2)}{(R_1 \parallel R_2) + R_{sin}}$$

$$V_S = g_m V_{GS} R_S = g_m (V_G - V_S) R_S$$

$$V_S = g_m R_S V_G - g_m R_S V_S$$

$$V_S (1 + g_m R_S) = g_m R_S V_G$$

$$V_S = \frac{g_m R_S V_G}{1 + g_m R_S}$$

$$V_{GS} = V_G - V_S = V_G - V_G \left(\frac{g_m R_S}{1 + g_m R_S} \right)$$

$$= V_G \left(1 - \frac{g_m R_S}{1 + g_m R_S} \right)$$

$$V_{GS} = \frac{V_{in} (R_1 \parallel R_2)}{(R_1 \parallel R_2) + R_{sin}} \left(1 - \frac{g_m R_S}{1 + g_m R_S} \right)$$

$$\therefore \left[\frac{V_{out}}{V_{in}} = \frac{-g_m (R_L \parallel R_D) (R_1 \parallel R_2)}{(R_1 \parallel R_2) + R_{sin}} \left(1 - \frac{g_m R_S}{1 + g_m R_S} \right) \right]$$

$R_{sin} = 0, R_L = \infty, R_D = 1k\Omega, R_S = 470\Omega, V_{GS} = 2V, k_p = .1233, R_1 = 200k\Omega, R_2 = 90k\Omega$

$$\frac{V_{out}}{V_{in}} = \frac{-g_m R_D (R_1 \parallel R_2)}{(R_1 \parallel R_2)} \left(1 - \frac{g_m R_S}{1 + g_m R_S} \right) = -g_m R_D + \frac{g_m^2 R_D R_S}{1 + g_m R_S}$$

$$g_m = \frac{2I_D}{2V_{GS}} \Big|_{V_{GS} = V_{GSQ}} = k_p (V_{GS} - V_{TR}) \approx .02466$$

$$\frac{V_{out}}{V_{in}} \Big|_{R_{sin}=0, R_L=\infty} \approx -2$$

$$\frac{V_{out}}{V_{in}} \Big|_{R_{sin}=50\Omega, R_L=1k\Omega} = \frac{-g_m (500\Omega) (62069)}{(62069) + 50} \left(1 - \frac{g_m (470)}{1 + g_m (470)} \right) \approx -1$$

Source and load resistance reduce gain.

$$\frac{I_{out}}{I_{in}} \Big|_{R_L = \infty} = 0$$

$$I_{out} \Big|_{R_{sin} = 50\Omega, R_L = 1k\Omega} = \frac{V_{out}}{R_L} = \frac{-1 V_{in}}{R_L} = -0.001 V_{in}$$


$$I_{in} = \frac{V_{in}}{R_{sin} + (R_1 || R_2)}$$

$$\frac{I_{out}}{I_{in}} \Big|_{R_{sin} = 50\Omega, R_L = 1k\Omega} \approx -62.119$$

4. $\frac{1}{2\pi f R_{sin}} \lll C$

$$1.5915 \times 10^{-6} \lll C$$

16 μF to 160 μF will work.

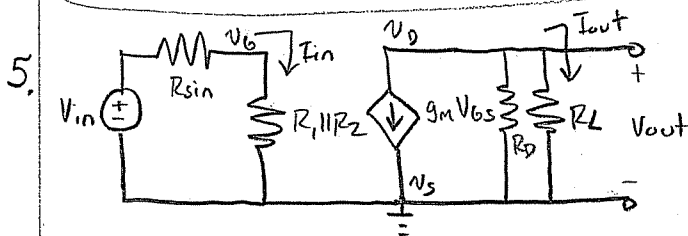

$$V_{out} = -g_m V_{GS} (R_L || R_D)$$

$$\frac{V_{in} (R_1 || R_2)}{(R_1 || R_2) + R_{sin}} = V_G$$

$$V_S = 0$$

$$\left[\frac{V_{out}}{V_{in}} = \frac{-g_m (R_L || R_D) (R_1 || R_2)}{(R_1 || R_2) + R_{sin}} \right] \therefore V_{GS} = V_G$$

$$\frac{V_{out}}{V_{in}} \Big|_{R_L = \infty, R_{sin} = 0} = -g_m R_D \approx -25$$

$$\frac{V_{out}}{V_{in}} \Big|_{R_{sin} = 50\Omega, R_L = 1k\Omega} \approx -12.3$$


$$\frac{I_{out}}{I_{in}} \Big|_{R_L = \infty} = 0 \quad (\text{No Load} = \text{No output current})$$

$$I_{out} \Big|_{R_{sin} = 50\Omega, R_L = 1k\Omega} = \frac{V_{out}}{R_L} = \frac{-12.3 V_{in}}{R_L} = -0.0123 V_{in}$$

$$I_{in} = \frac{V_{in}}{R_{sin} + (R_1 || R_2)} = 1.609 \times 10^{-5} V_{in}$$

$$\frac{I_{out}}{I_{in}} \Big|_{R_{sin} = 50\Omega, R_L = 1k\Omega} \approx -764$$

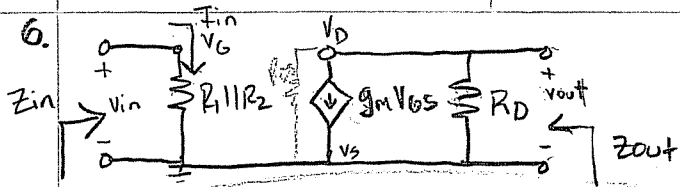R_S greatly reduces current and voltage gain!



$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{V_{in}}{\frac{V_{in}}{R_1 || R_2}} = R_1 || R_2 \approx 62069 \Omega$$


$$Z_{out} = \frac{V_{open}}{I_{short}} = \frac{-g_m V_{GS} R_D}{-g_m V_{GS}} = R_D = 1 k\Omega$$

CAMPAD

7.

$$Z_{in} = R_1 || R_2 = 62069 \Omega$$
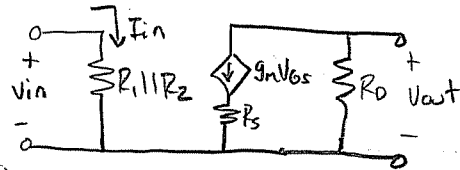
$$Z_{out} = \frac{V_{open}}{I_{short}} = \frac{-g_m V_{GS} R_D}{-g_m V_{GS}} = R_D = 1 k\Omega$$



$$V_{out} = -g_m V_{GS} R_D$$

R_s does not effect output or input impedances (in the small signal model with these assumptions)